 


# Unit 6: Testing

---

- Course contents
  - Fault Modeling
  - Fault Simulation
  - Test Generation
  - Design For Testability
- Reading
  - Supplementary readings





# Outline

---



- Introduction
- Fault Modeling
- Fault Simulation
- Test Generation
- Design For Testability

# Chip Design & Manufacturing Flow

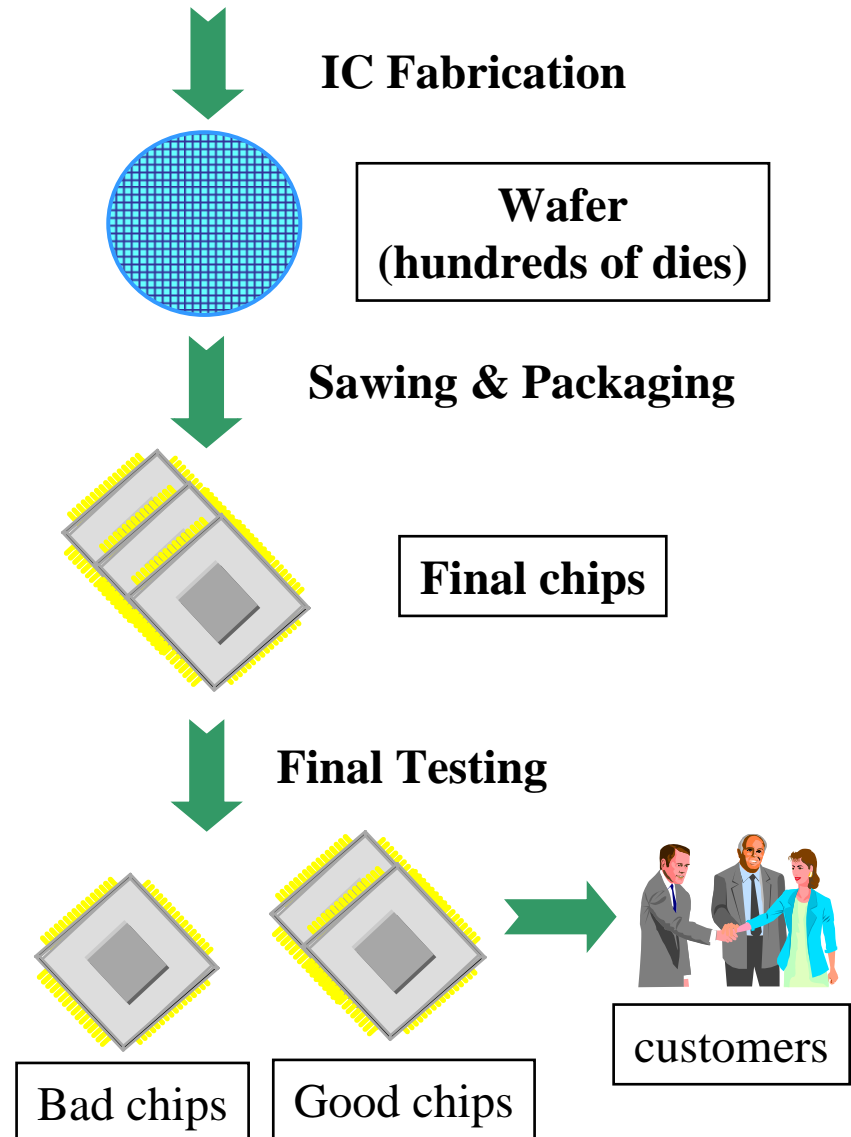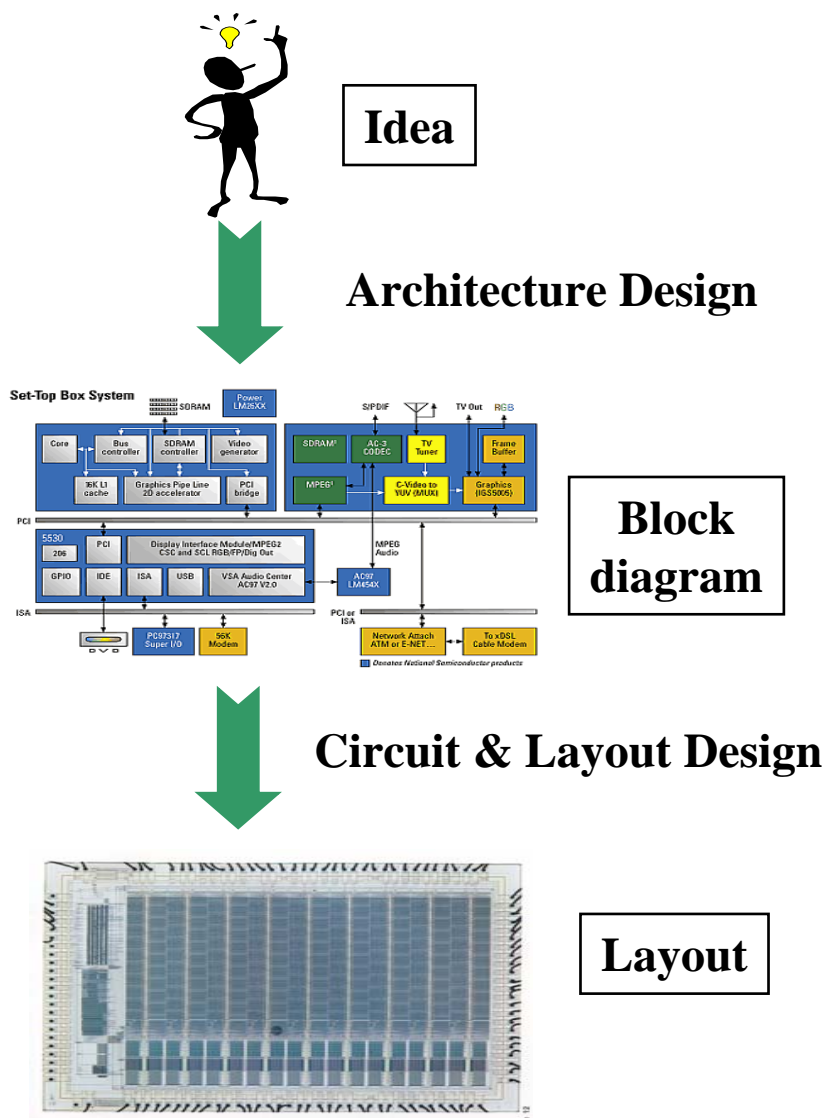

# Design Verification, Testing and Diagnosis

---

- Design Verification:
  - Ascertain the design perform its specified behavior
- Testing:
  - Exercise the system and analyze the response to ascertain whether it behaves correctly **after manufacturing**
- Diagnosis:
  - To locate the **cause(s)** of misbehavior after the incorrect behavior is detected

# Manufacturing Defects

---

- Processing Faults
  - missing contact windows
  - parasitic transistors
  - oxide breakdown
- Material Defects
  - bulk defects (cracks, crystal imperfections)
  - surface impurities
- Time-Dependent Failures
  - dielectric breakdown
  - electro-migration
- Packaging Failures
  - contact degradation
  - seal leaks


# Faults, Errors and Failures

---

- Fault:
  - A physical defect within a circuit or a system
  - May or may not cause a system failure
- Error:
  - Manifestation of a fault that results in incorrect circuit (system) outputs or states
  - Caused by faults
- Failure:
  - Deviation of a circuit or system from its specified behavior
  - Fails to do what it should do
  - Caused by an error
- Fault ---> Error ---> Failure

# Scenario of Manufacturing Test

---

 

# Tester: Advantest T6682


---





 
# Purpose of Testing

- Verify Manufacturing of Circuit
  - Improve System Reliability
  - Diminish System Cost
- Cost of repair
  - goes up by an order of magnitude each step away from the fab. line



# Testing and Quality

---

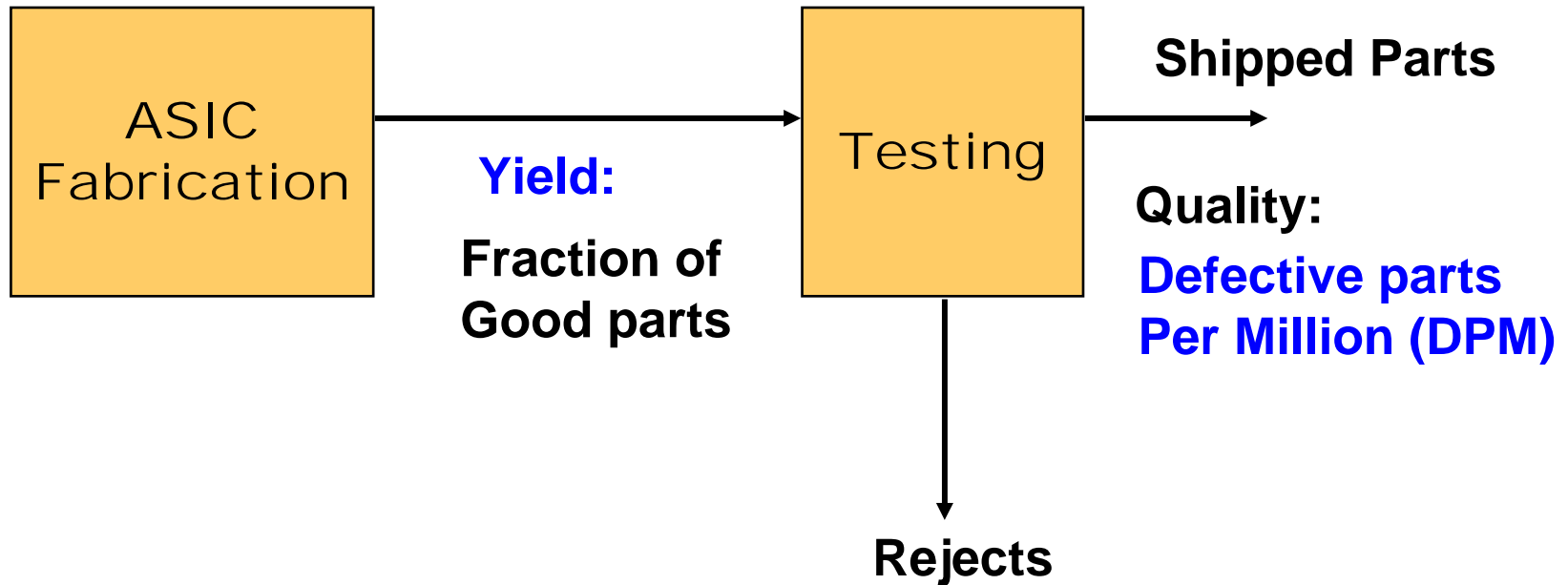

**Quality of shipped part is a function of yield  $Y$  and the test (fault) coverage  $T$ .**

# Fault Coverage

---

- Fault Coverage T
  - Is the measure of the ability of a set of tests to detect a given class of faults that may occur on the device under test (DUT)

$$T = \frac{\text{No. of detected faults}}{\text{No. of all possible faults}}$$

# Defect Level

---


- Defect Level
  - Is the fraction of the shipped parts that are defective

$$DL = 1 - Y^{(1-T)}$$

Y: yield

T: fault coverage

# Defect Level v.s. Fault Coverage

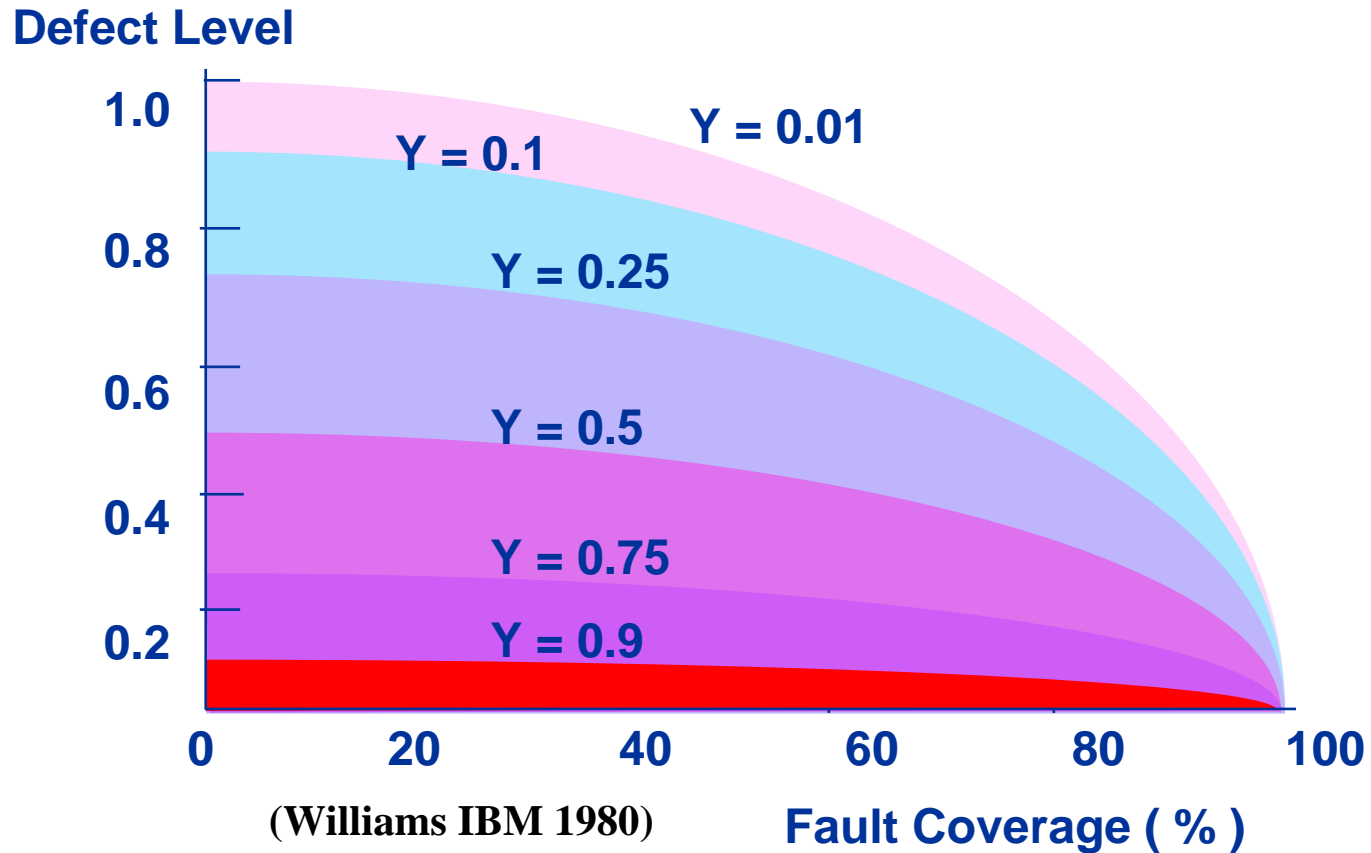

High fault coverage  $\longrightarrow$  Low defect level

## DPM v.s. Yield and Coverage

---

Yield	Fault Coverage	DPM
<b>50%</b>	<b>90%</b>	<b>67,000</b>
<b>75%</b>	<b>90%</b>	<b>28,000</b>
<b>90%</b>	<b>90%</b>	<b>10,000</b>
<b>95%</b>	<b>90%</b>	<b>5,000</b>
<b>99%</b>	<b>90%</b>	<b>1,000</b>
<b>90%</b>	<b>90%</b>	<b>10,000</b>
<b>90%</b>	<b>95%</b>	<b>5,000</b>
<b>90%</b>	<b>99%</b>	<b>1,000</b>
<b>90%</b>	<b>99.9%</b>	<b>100</b>

# Why Testing Is Difficult ?


---

- Test application time can be exploded for exhaustive testing of VLSI
  - For a combinational circuit with 50 inputs, we need  $2^{50} = 1.126 \times 10^{15}$  test patterns.
  - Assume one test per  $10^{-7}$ sec, it takes  $1.125 \times 10^8$ sec = 3.57yrs. to test such a circuit.
  - Test generation for sequential circuits are even more difficult due to the lack of controllability and observability at flip-flops (latches)
- Functional testing
  - may NOT be able to detect the physical faults
 
# The Infamous Design/Test Wall


---

**30 years of experience proves that  
test after design does not work!**






# Old Design & Test Flow

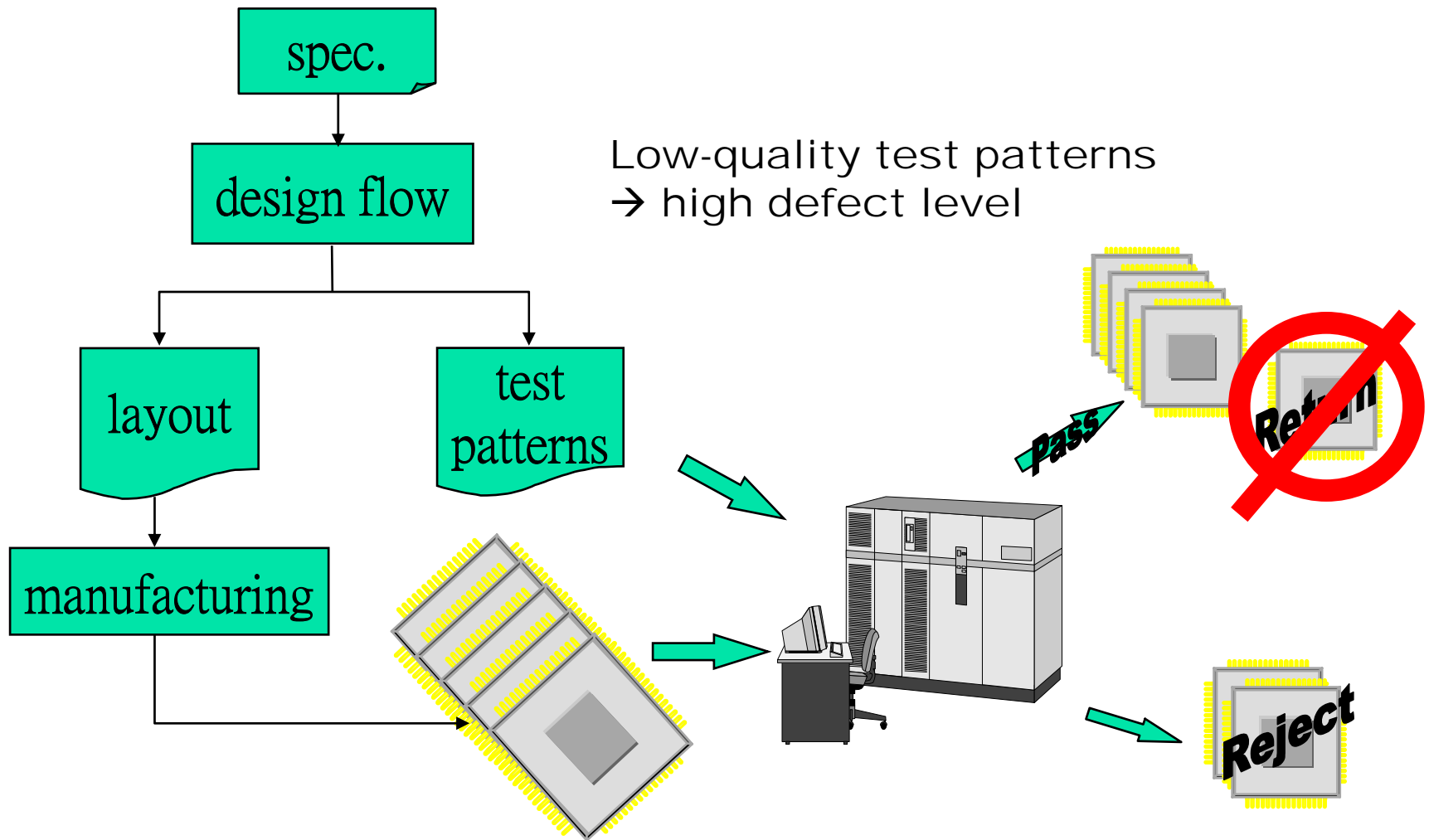


# New Design and Test Flow

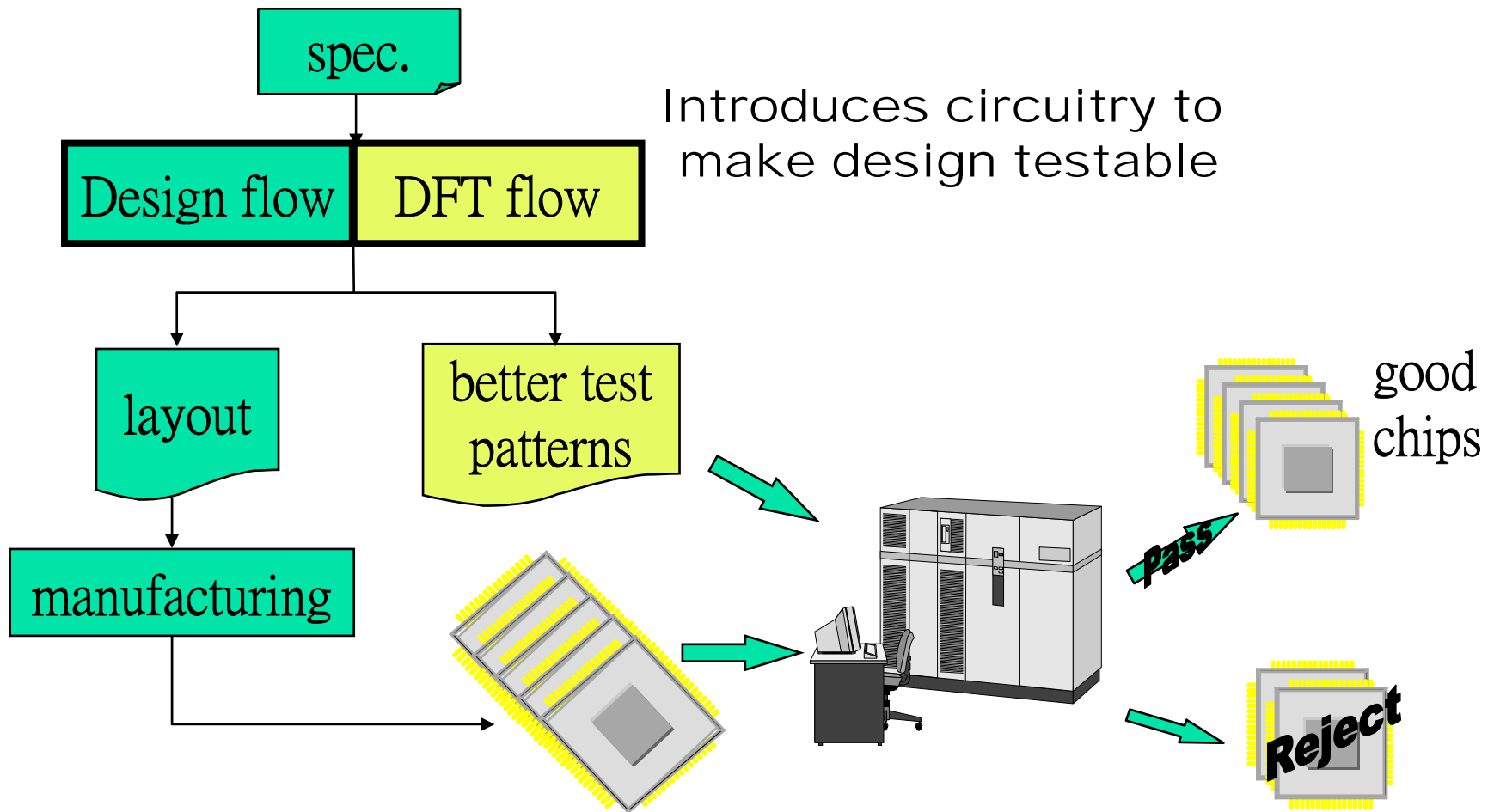

# Outline

---

- Introduction
-  • Fault Modeling
- Fault Simulation
- Test Generation
- Design For Testability

# Functional v.s. Structural Testing

---

- I/O function tests inadequate for manufacturing
  - Functionality vs. component & interconnection testing
- Exhaustive testing is Prohibitively expensive

# Why Fault Model ?

---

- Fault model identifies target faults
  - Model faults most likely to occur
- Fault model limits the scope of test generation
  - Create tests only for the modeled faults
- Fault model makes effectiveness measurable by experiments
  - Fault coverage can be computed for specific test patterns to reflect its effectiveness
- Fault model makes analysis possible
  - Associate specific defects with specific test patterns

# Fault Modeling

---

- Fault Modeling
  - Model the effects of physical defects on the logic function and timing
- Physical Defects
  - Silicon Defects
  - Photolithographic Defects
  - Mask Contamination
  - Process Variation
  - Defective Oxides

# Fault Modeling (cont'd)

---

- **Electrical Effects**
  - Shorts (Bridging Faults)
  - Opens
  - Transistor Stuck-On/Open
  - Resistive Shorts/Opens
  - Change in Threshold Voltages
- **Logical Effects**
  - Logical Stuck-at 0/1
  - Slower Transition (Delay Faults)
  - AND-bridging, OR-bridging


# Fault Types Commonly Used To Guide Test Generation

---

- Stuck-at Faults
- Bridging Faults
- Transistor Stuck-On/Open Faults
- Delay Faults
- IDDQ Faults
- State Transition Faults (for FSM)
- Memory Faults
- PLA Faults



# Single Stuck-At Fault

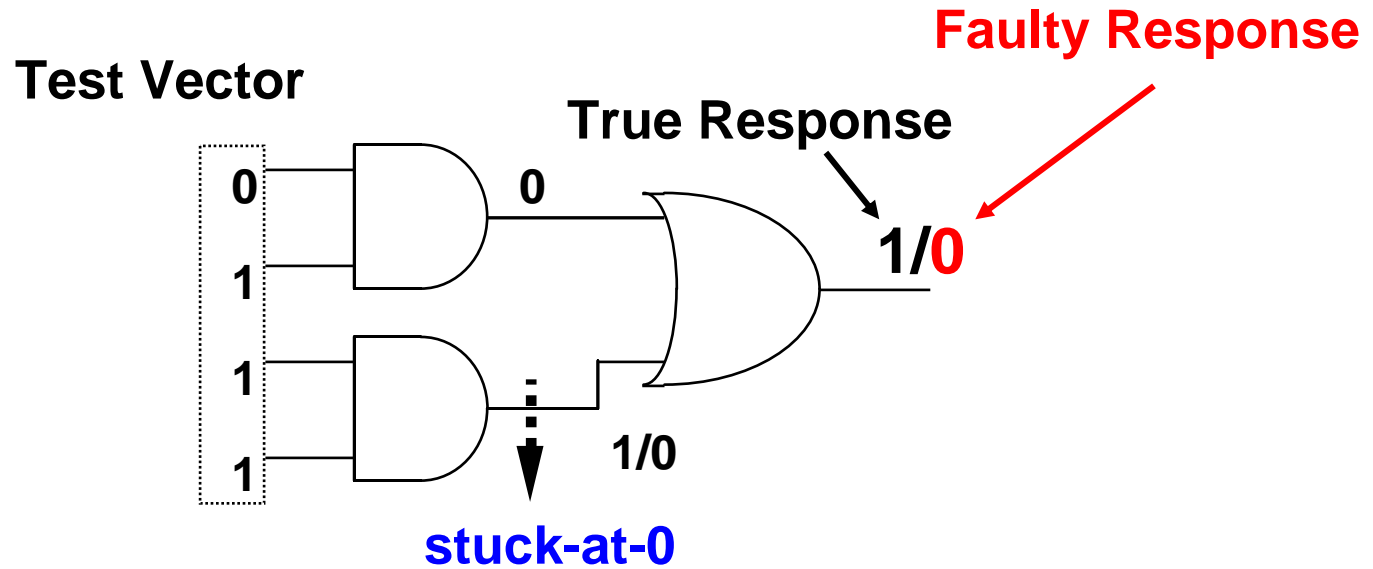

Assumptions:

- Only One line is faulty
- Faulty line permanently set to 0 or 1
- Fault can be at an input or output of a gate

# Multiple Stuck-At Faults

---

- Several stuck-at faults occur at the same time
  - Important in high density circuits
- For a circuit with  $k$  lines
  - there are  $2k$  single stuck-at faults
  - there are  $3^k - 1$  multiple stuck-at faults
    - A line could be stuck-at-0, stuck-at-1, or fault-free
    - One out of  $3^k$  resulting circuits is fault-free

# Why Single Stuck-At Fault Model

---

- Complexity is greatly reduced
  - Many different physical defects may be modeled by the same logical single stuck-at fault
- Stuck-at fault is technology independent
  - Can be applied to TTL, ECL, CMOS, BiCMOS etc.
- Design style independent
  - Gate array, standard cell, custom VLSI
- Detection capability of un-modeled defects
  - Empirically many defects accidentally detected by test derived based on single stuck-at fault
- Cover a large percentage of multiple stuck-at faults


# Multiple Faults

---


- Multiple stuck-fault coverage by single-fault tests of combinational circuit:
  - 4-bit ALU (Hughes & McCluskey, ITC-84)  
All double and most triple-faults covered.
  - Large circuits (Jacob & Biswas, ITC-87)  
Almost 100% multiple faults covered for circuits with 3 or more outputs.
- No results available for sequential circuits.
 
# Bridging Faults

- Two or more normally distinct points (lines) are shorted together
  - Logic effect depends on technology
  - Wired-AND for TTL




- Wired-OR for ECL

 

- CMOS ?
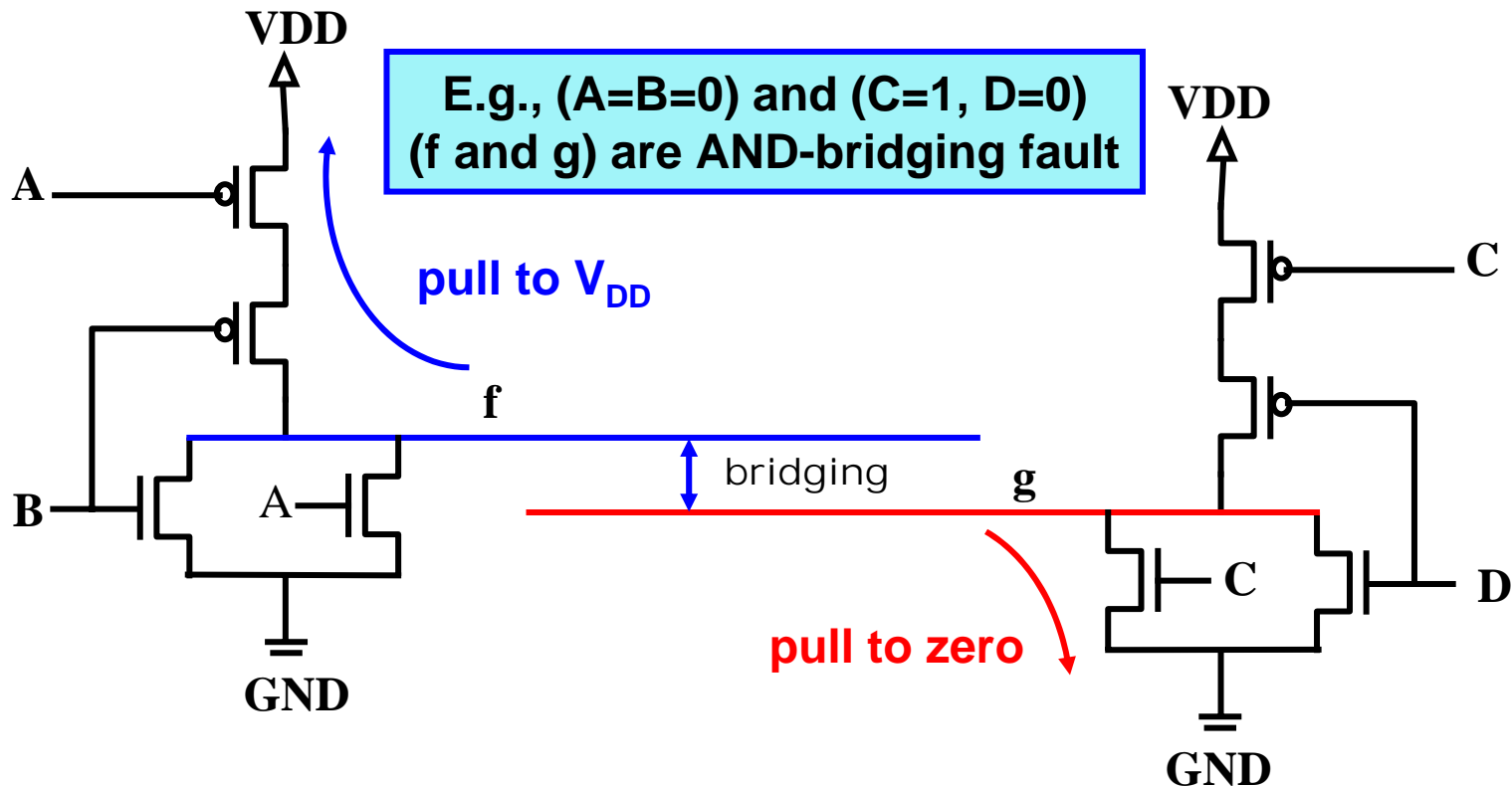
# Bridging Faults For CMOS Logic


- The result
  - could be AND-bridging or OR-bridging
  - depends on the the inputs



# CMOS Transistor Stuck-On

Example:


N transistor  
is always ON

 

- Transistor Stuck-On
  - May cause ambiguous logic level
  - Depends on the relative impedances of the pull-up and pull-down networks
- When Input Is Low
  - Both P and N transistors are conducting, causing increased quiescent current, called  $I_{DDQ}$  fault
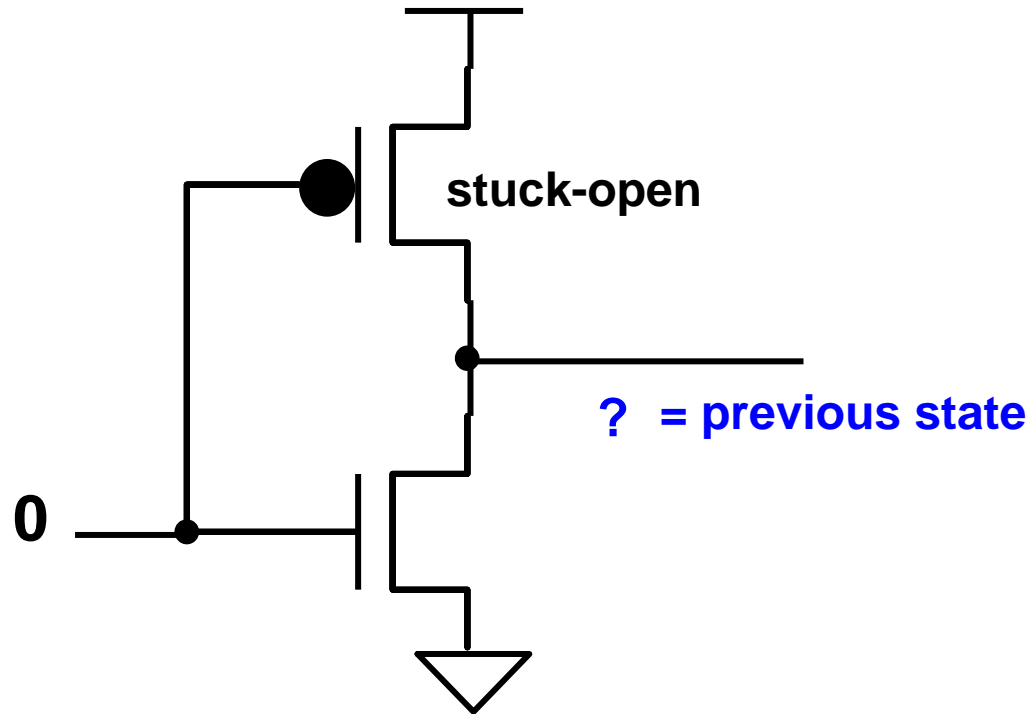
# CMOS Transistor Stuck-Open (I)


- Transistor stuck-open
  - May cause the output to be **floating**
  - The faulty becomes exhibits **sequential behavior**





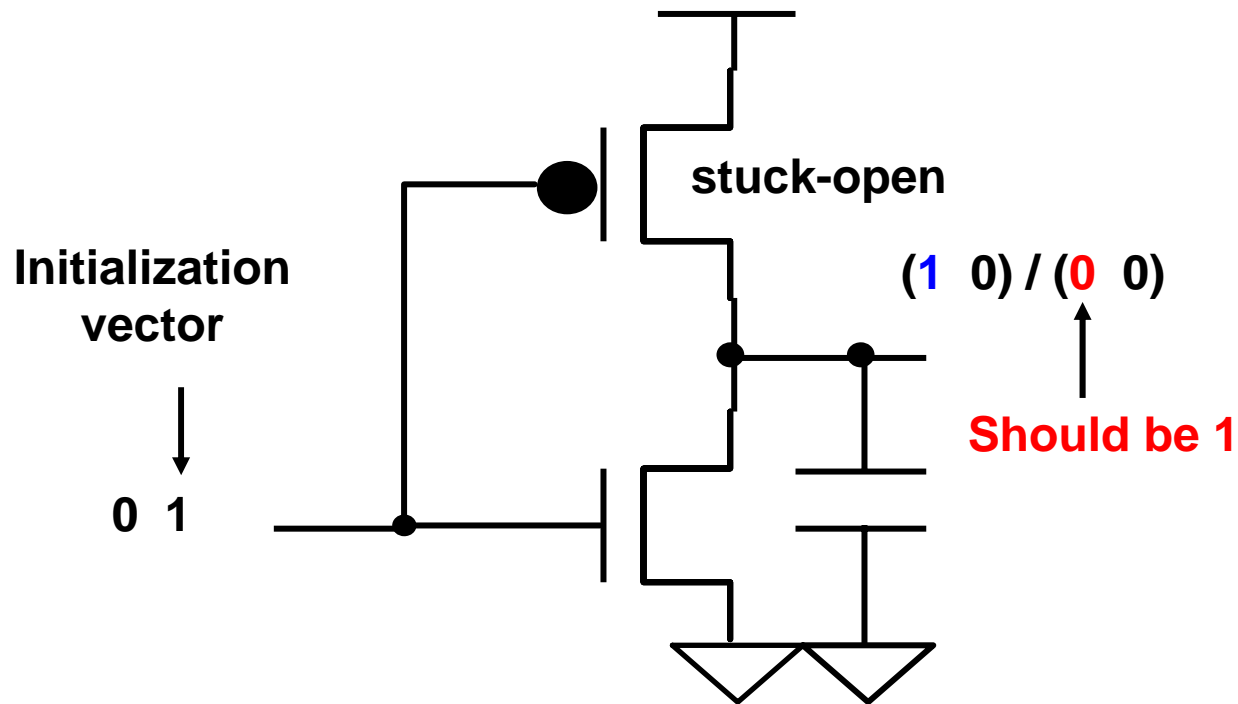
# CMOS Transistor Stuck-Open (II)

- The circuit may turn into a **sequential** one
- Stuck-open requires **two vector tests**



# Fault Coverage in a CMOS Chip

 

# Summary of Stuck-Open Faults

---

- First Report:
  - Wadsack, Bell System Technology, J., 1978
- Recent Results
  - Woodhall et. al, ITC-87 (1-micron CMOS chips)
  - 4552 chips passed parametric test
  - 1255 chips (27.57%) failed tests for stuck-at faults
  - 44 chips (0.97%) failed tests for stuck-open faults
  - 4 chips with stuck-open faults passed tests for stuck-at faults
- Conclusion
  - Stuck-at faults are about 20 times more frequent than stuck-open faults
  - About 91% of chips with stuck-open faults may also have stuck-at faults
  - Faulty chips escaping tests for stuck-at faults = 0.121%

# Memory Faults

---

- Parametric Faults
  - Output Levels
  - Power Consumption
  - Noise Margin
  - Data Retention Time
- Functional Faults
  - Stuck Faults in Address Register, Data Register, and Address Decoder
  - Cell Stuck Faults
  - Adjacent Cell Coupling Faults
  - Pattern-Sensitive Faults


# Delay Testing

---

- Chip with timing defects
  - may pass the DC stuck-fault testing, but fail when operated at the system speed
  - For example, a chip may pass testing under 10 MHz operation, but fail under 100 MHz
- Delay Fault Models
  - Gate-Delay Fault
  - Path-Delay Fault

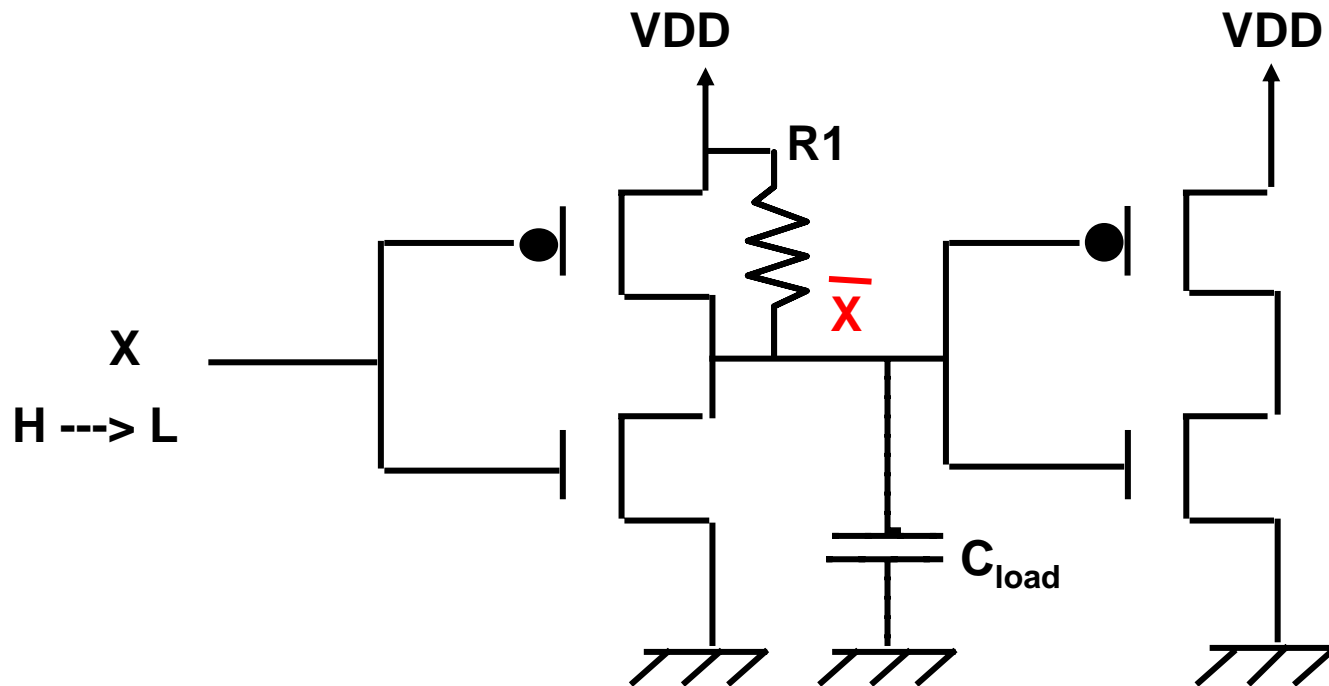
# Gate-Delay Fault

- Slow to rise, slow to fall
  - $\bar{x}$  is slow to rise when channel resistance R1 is abnormally high



## Gate-Delay Fault (cont'd)


---

 

- Test Based on Gate-Delay Fault
  - May not detect those delay faults that result from the **accumulation** of a number of small **incremental delay defects** along a path !! (Disadvantage)
 
# Path-Delay Fault

- Associated with a Path (e.g. **A-B-C-Z**)
  - Whose delay exceeds the clock interval
- More complicated than gate-delay fault
  - Because the number of paths grows exponentially






# Why Logical Fault Modeling ?

---

- Fault analysis on logic rather than physical problem
  - Complexity is reduced
- Technology independent
  - Same fault model is applicable to many technologies
  - Testing and diagnosis methods remain valid despite changes in technology
- Tests derived
  - may be used for physical faults whose effect on circuit behavior is not completely understood or too complex to be analyzed
- Stuck-at fault is
  - The most popular logical fault model
 
# Definition Of Fault Detection

- A test (vector)  $t$  detects a fault  $f$  iff
  - $t$  detects  $f \Leftrightarrow \mathbf{z}(t) \neq \mathbf{z}_f(t)$
- Example




The test  $(x_1, x_2, x_3) = (100)$  detects  $f$  because  $z_1(100)=0$  while  $z_{1f}(100)=1$

# Fault Detection Requirement

---

- A test  $t$  that detects a fault  $f$ 
  - **Activates**  $f$  (or generate a fault effect) by creating different  $v$  and  $v_f$  values at the site of the fault
  - **Propagates** the error to a primary output  $w$  by making all the lines along at least one path between the fault site and  $w$  have different  $v$  and  $v_f$  values
- Sensitized Line:
  - A line whose **value in response to the test changes** in the presence of the fault  $f$  is said to be **sensitized by the test** in the faulty circuit
- Sensitized Path:
  - A path composed of sensitized lines is called a sensitized path

# Fault Sensitization

 

$$z(1011)=0$$

$$z_f(1011)=1$$

**1011 detects the fault  $f$  ( $G_2$  stuck-at 1)**

**$v/v_f$  :  $v$  = signal value in the fault free circuit**


**$v_f$  = signal value in the faulty circuit**

# Detectability

---

- A fault  $f$  is said to be detectable
  - if there exists a test  $t$  that detects  $f$ ; otherwise,  $f$  is an undetectable fault
- For an undetectable fault  $f$ 
  - No test can **simultaneously** activate  $f$  and create a sensitized path to a primary output

# Undetectable Fault

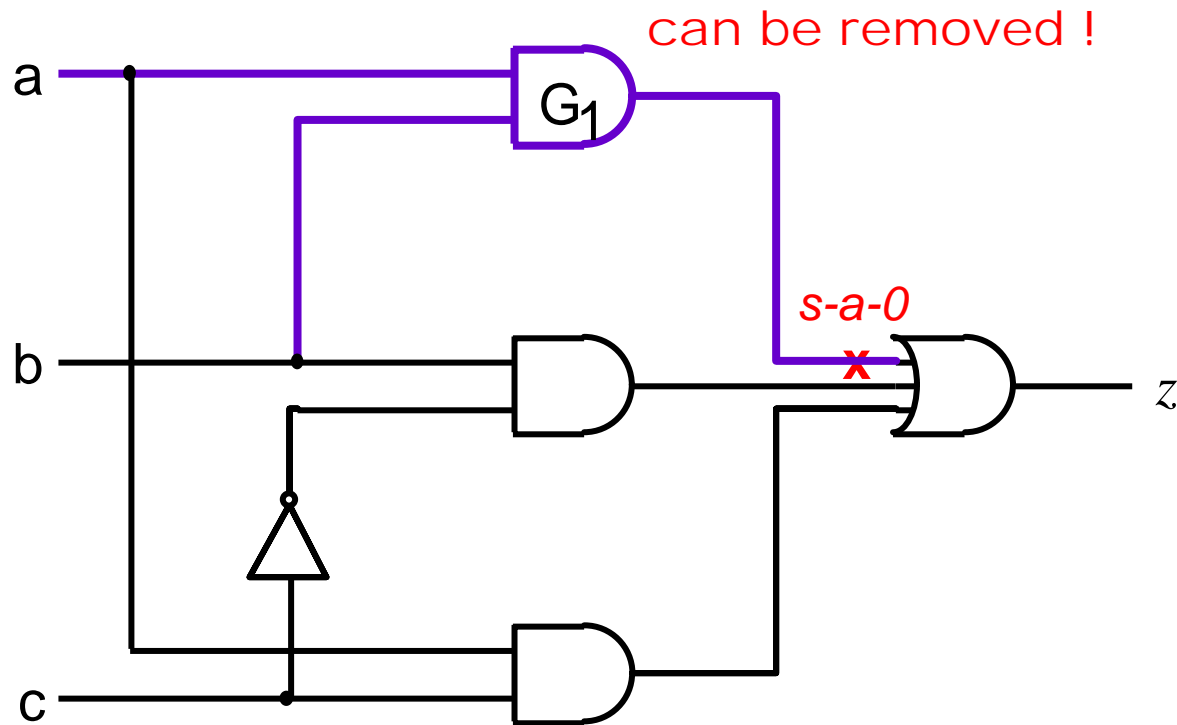

- $G_1$  output stuck-at-0 fault is undetectable
  - Undetectable faults do not change the function of the circuit
  - The related circuit can be deleted to simplify the circuit


# Test Set

---

- Complete detection test set:
  - A set of tests that detect any detectable faults in a class of faults
- The quality of a test set
  - is measured by fault coverage
- Fault coverage:
  - Fraction of faults that are detected by a test set
- The fault coverage
  - can be determined by fault simulation
  - >95% is typically required for single stuck-at fault model
  - >99.9% in IBM

# Typical Test Generation Flow

---

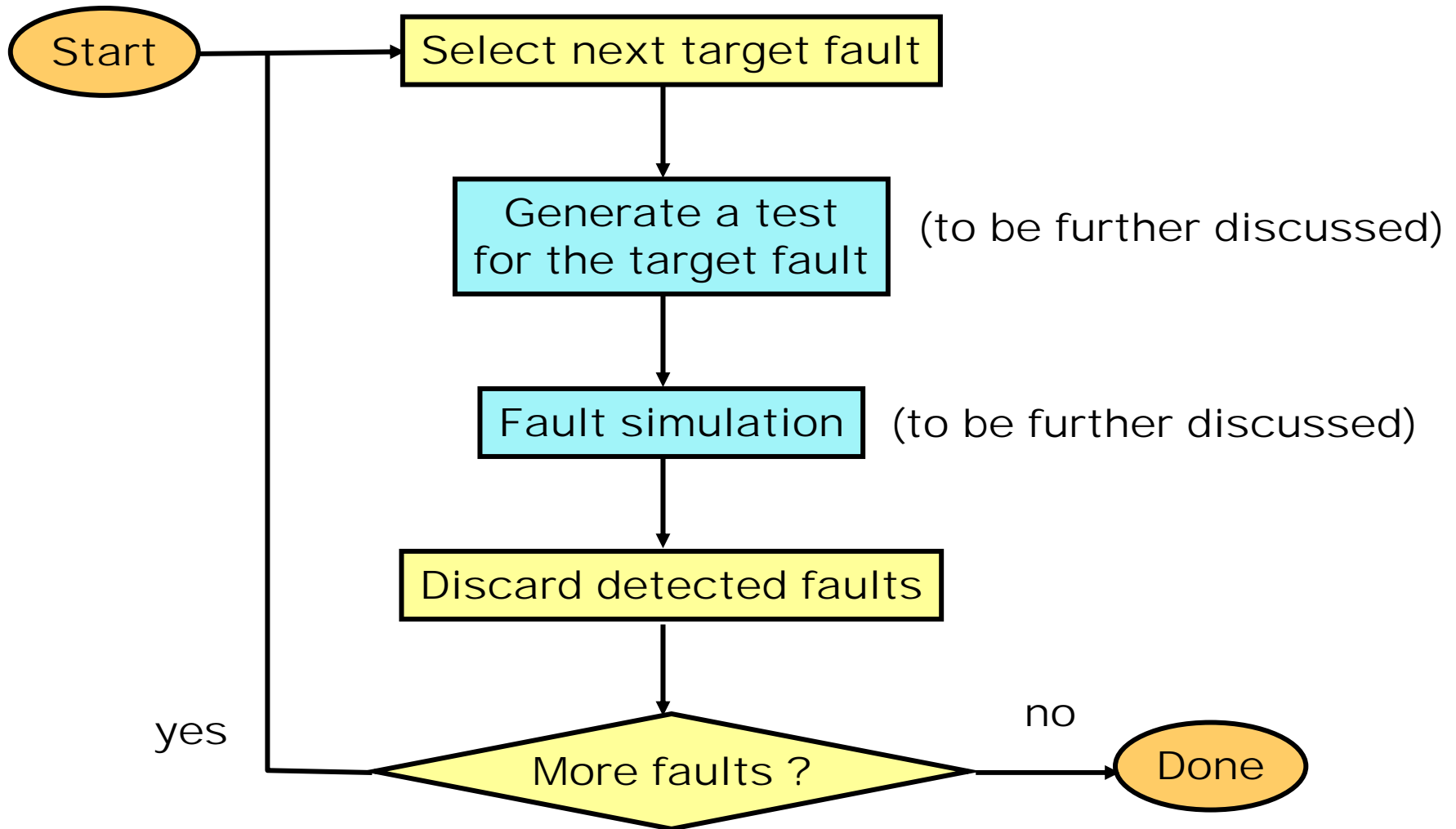



# Fault Equivalence

---

- Distinguishing test

- A test  $t$  distinguishes faults  $\alpha$  and  $\beta$  if


$$Z_{\alpha}(t) \oplus Z_{\beta}(t) = 1$$

- Equivalent Faults

- Two faults,  $\alpha$  &  $\beta$  are said to be equivalent in a circuit, iff the function under  $\alpha$  is equal to the function under  $\beta$  for **any input combination** (sequence) of the circuit.
- No test can distinguish between  $\alpha$  and  $\beta$
- In other words, **test-set( $\alpha$ ) = test-set( $\beta$ )**




 
# Fault Equivalence

- AND gate:
  - all *s-a-0* faults are equivalent
- OR gate:
  - all *s-a-1* faults are equivalent
- NAND gate:
  - all the input *s-a-0* faults and the output *s-a-1* faults are equivalent
- NOR gate:
  - all input *s-a-1* faults and the output *s-a-0* faults are equivalent
- Inverter:
  - input *s-a-1* and output *s-a-0* are equivalent
  - input *s-a-0* and output *s-a-1* are equivalent



    
# Equivalence Fault Collapsing

- $n+2$  instead of  $2(n+1)$  faults need to be considered for  $n$ -input gates


 
# Equivalent Fault Group

- In a combinational circuit
  - Many faults may form an equivalent group
  - These equivalent faults can be found by sweeping the circuit from the primary outputs to the primary inputs




Three faults shown are equivalent !
 
# Fault Dominance


- Dominance Relation

- A fault  $\beta$  is said to *dominate* another fault  $\alpha$  in an irredundant circuit, iff every test (sequence) for  $\alpha$  is also a test (sequence) for  $\beta$ .
- I.e.,  $\text{test-set}(\beta) > \text{test-set}(\alpha)$
- No need to consider fault  $\beta$  for fault detection



 
# Fault Dominance

- AND gate:
  - Output *s-a-1* dominates any input *s-a-1*
- NAND gate:
  - Output *s-a-0* dominates any input *s-a-1*
- OR gate:
  - Output *s-a-0* dominates any input *s-a-0*
- NOR gate:
  - Output *s-a-1* dominates any input *s-a-0*
- Dominance fault collapsing:
  - The reduction of the set of faults to be analyzed based on dominance relation


 
# Stem v.s. Branch Faults

C: **stem** of a multiple fanout  
A & B: **branches**



- Detect A sa1:

$$z(t) \oplus z_f(t) = (\mathbf{CD} \oplus \mathbf{CE}) \oplus (\mathbf{D} \oplus \mathbf{CE}) = \mathbf{D} \oplus \mathbf{CD} = 1$$

$$\Rightarrow (\mathbf{C} = 0, \mathbf{D} = 1)$$

- Detect C sa1:

$$z(t) \oplus z_f(t) = (\mathbf{CD} \oplus \mathbf{CE}) \oplus (\mathbf{D} \oplus \mathbf{E}) = 1$$

$$\Rightarrow (\mathbf{C} = 0, \mathbf{D} = 1) \text{ or } (\mathbf{C} = 0, \mathbf{E} = 1)$$


- Hence, C sa1 dominates A sa1

- Similarly

- C sa1 dominates B sa1
- C sa0 dominates A sa0
- C sa0 dominates B sa0

- In general, there might be no equivalence or dominance relations between stem and branch faults

# Analysis of a Single Gate

 





AB	C	A sa1	B sa1	C sa1	A sa0	B sa0	C sa0
00	0			1			
01	0	1		1			
10	0		1	1			
11	1				0	0	0

- Fault Equivalence Class
  - (A s-a-0, B s-a-0, C s-a-0)
- Fault Dominance Relations
  - (C s-a-1 > A s-a-1) and (C s-a-1 > B s-a-1)
- Faults that can be ignored:
  - A s-a-0, B s-a-0, and C s-a-1



    
# Fault Collapsing

- Equivalence + Dominance
  - For each  $n$ -input gate, we only need to consider  $n+1$  faults during test generation



 
# Dominance Graph

- Rule
  - When fault  $\alpha$  dominates fault  $\beta$ , then an arrow is pointing from  $\alpha$  to  $\beta$
- Application
  - Find out the transitive dominance relations among faults



# Fault Collapsing Flow

---

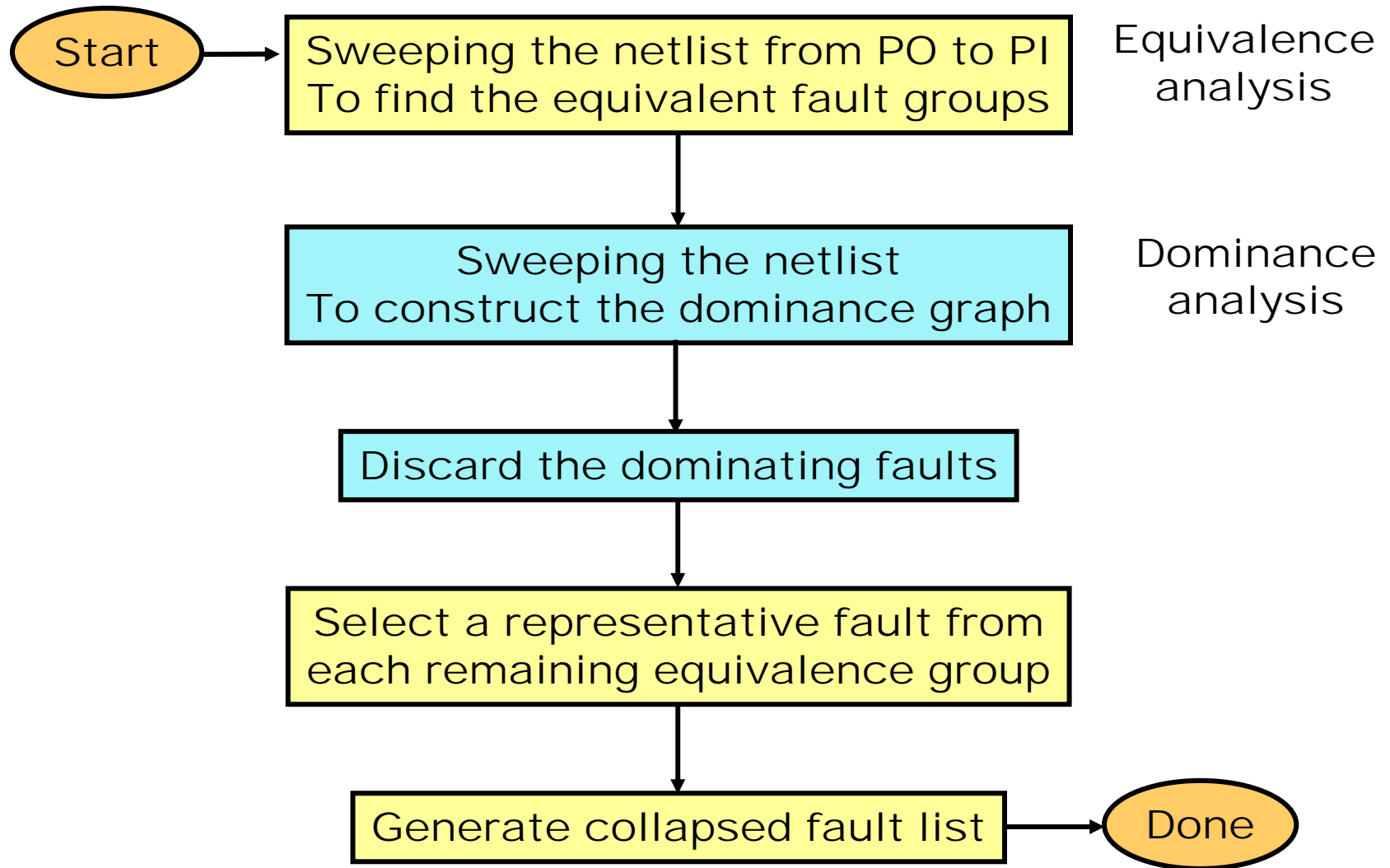


# Prime Fault

---

- $\alpha$  is a prime fault if every fault that is dominated by  $\alpha$  is also equivalent to  $\alpha$
- Representative Set of Prime Fault (RSPF)
  - A set that consists of exactly one prime fault from each equivalence class of prime faults
  - True minimal RSPF is difficult to find
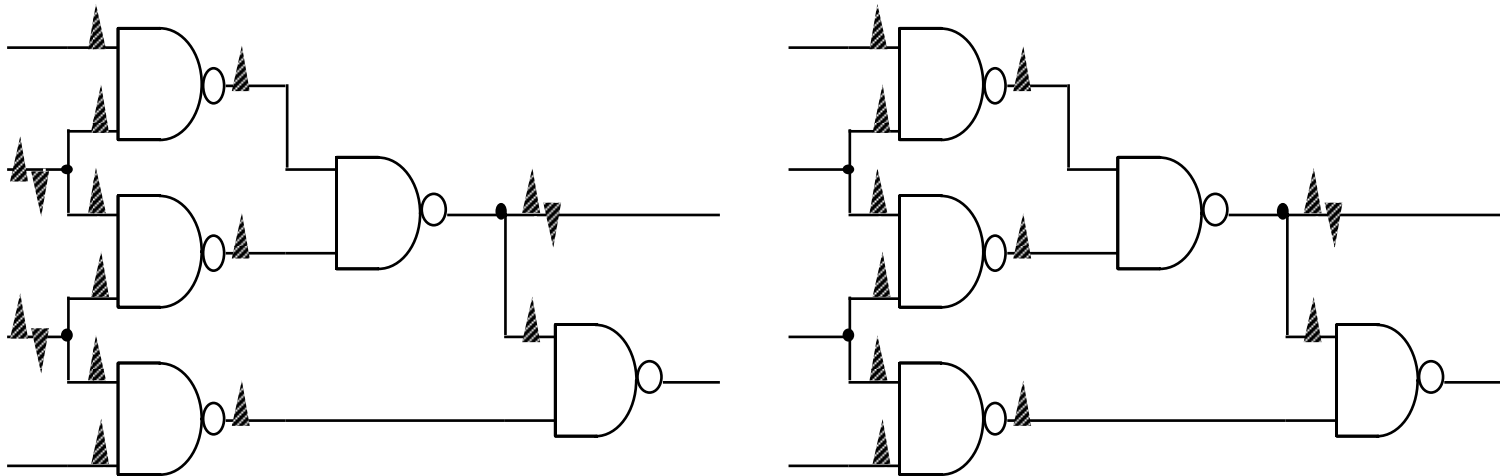
# Why Fault Collapsing ?

- Memory and CPU-time saving
- Ease testing generation and fault simulation




**\* 30 total faults    →    12 prime faults**
 
# Checkpoint Theorem

---


- Checkpoints for test generation
  - A test set detects every fault on the **primary inputs** and **fanout branches** is complete
  - I.e., this test set detects all other faults too
  - Therefore, **primary inputs** and **fanout branches** form a *sufficient* set of checkpoints in test generation
  - In fanout-free combinational circuits, primary inputs are the checkpoints



Stem is not a checkpoint !


# Why Inputs + Branches Are Enough ?

 - Example
  - Checkpoints are marked in blue
  - Sweeping the circuit from PI to PO to examine every gate, e.g., based on an order of (A->B->C->D->E)
  - For each gate,  
output faults are detected if every input fault is detected



# Fault Collapsing + Checkpoint

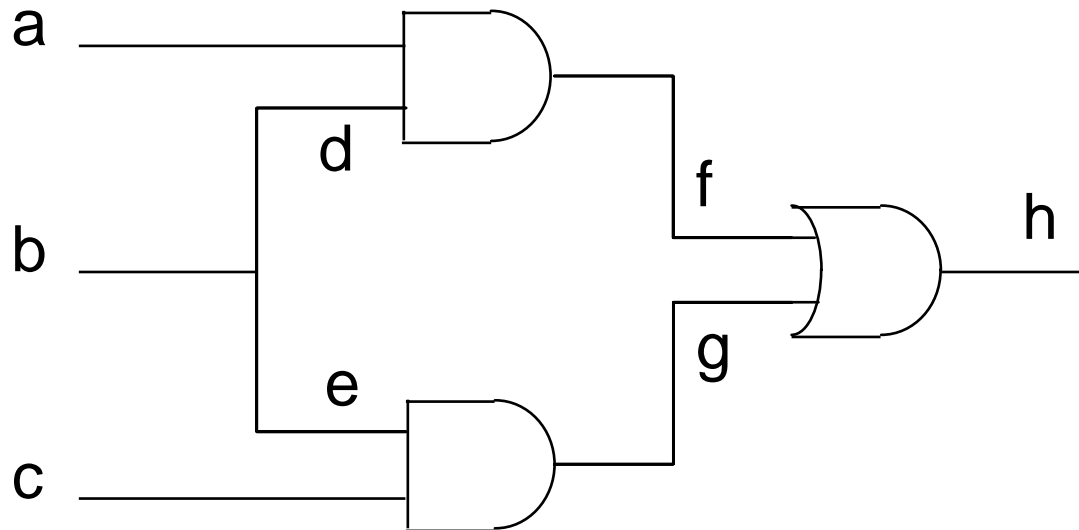- Example:
  - 10 checkpoint faults
  - $a \text{ s-a-0} \Leftrightarrow d \text{ s-a-0}$  ,  $c \text{ s-a-0} \Leftrightarrow e \text{ s-a-0}$   
 $b \text{ s-a-0} > d \text{ s-a-0}$  ,  $b \text{ s-a-1} > d \text{ s-a-1}$
  - 6 tests are enough





# Outline

---

- Introduction
- Fault Modeling
- **Fault Simulation**
- Test Generation
- Design For Testability




# Why Fault Simulation ?

---

- To evaluate the quality of a test set
  - I.e., to compute its fault coverage
- Part of an ATPG program
  - A vector usually detected multiple faults
  - Fault simulation is used to compute the faults accidentally detected by a particular vector
- To construct fault-dictionary
  - For post-testing diagnosis

# Conceptual Fault Simulation

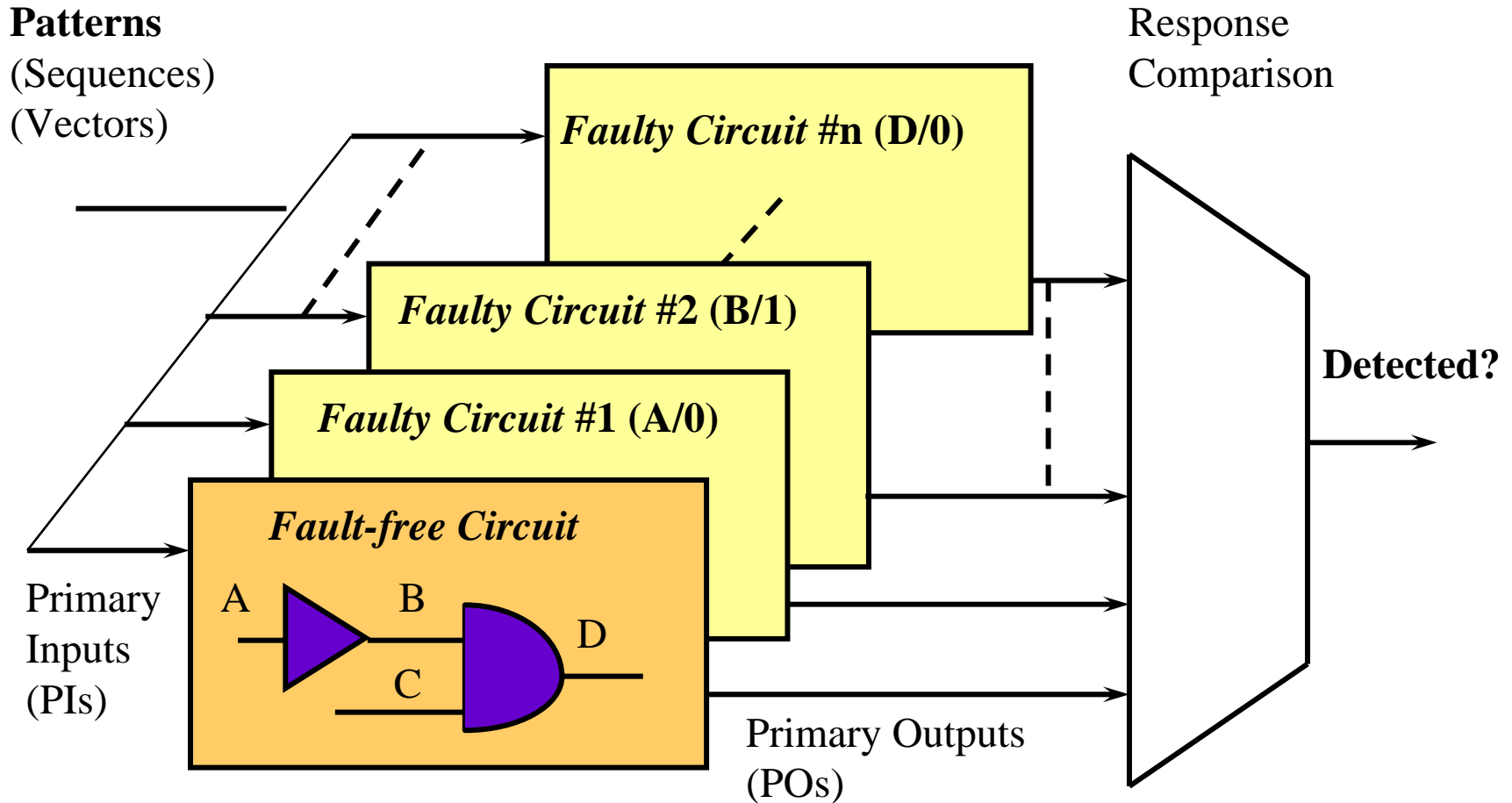

Logic simulation on both good (fault-free) and faulty circuits


# Some Basics for Logic Simulation

---

- For fault simulation purpose,
  - mostly the **gate delay is assumed to be zero** unless the delay faults are considered. Our main concern is the **functional faults**
- The logic values
  - can be either two (0, 1) or **three values (0, 1, X)**
- Two simulation mechanisms:
  - **Oblivious compiled-code:**
    - circuit is translated into a program and **all** gates are executed for each pattern. (may have **redundant computation**)
  - **Interpretive event-driven:**
    - Simulating a vector is viewed as a sequence of **value-change events** propagating from the PI's to the PO's
    - Only those logic gates affected by the events are **re-evaluated**



# Compiled-Code Simulation

---

 


- Compiled code
  - LOAD    *A*        */\* load accumulator with value of *A* \*/*
  - AND     *B*        */\* calculate *A* and *B* \*/*
  - AND     *C*        */\* calculate *E* = *AB* and *C* \*/*
  - OR      *D*        */\* calculate *Z* = *E* or *D* \*/*
  - STORE   *Z*        */\* store result of *Z* \*/*

# Event-Driven Simulation

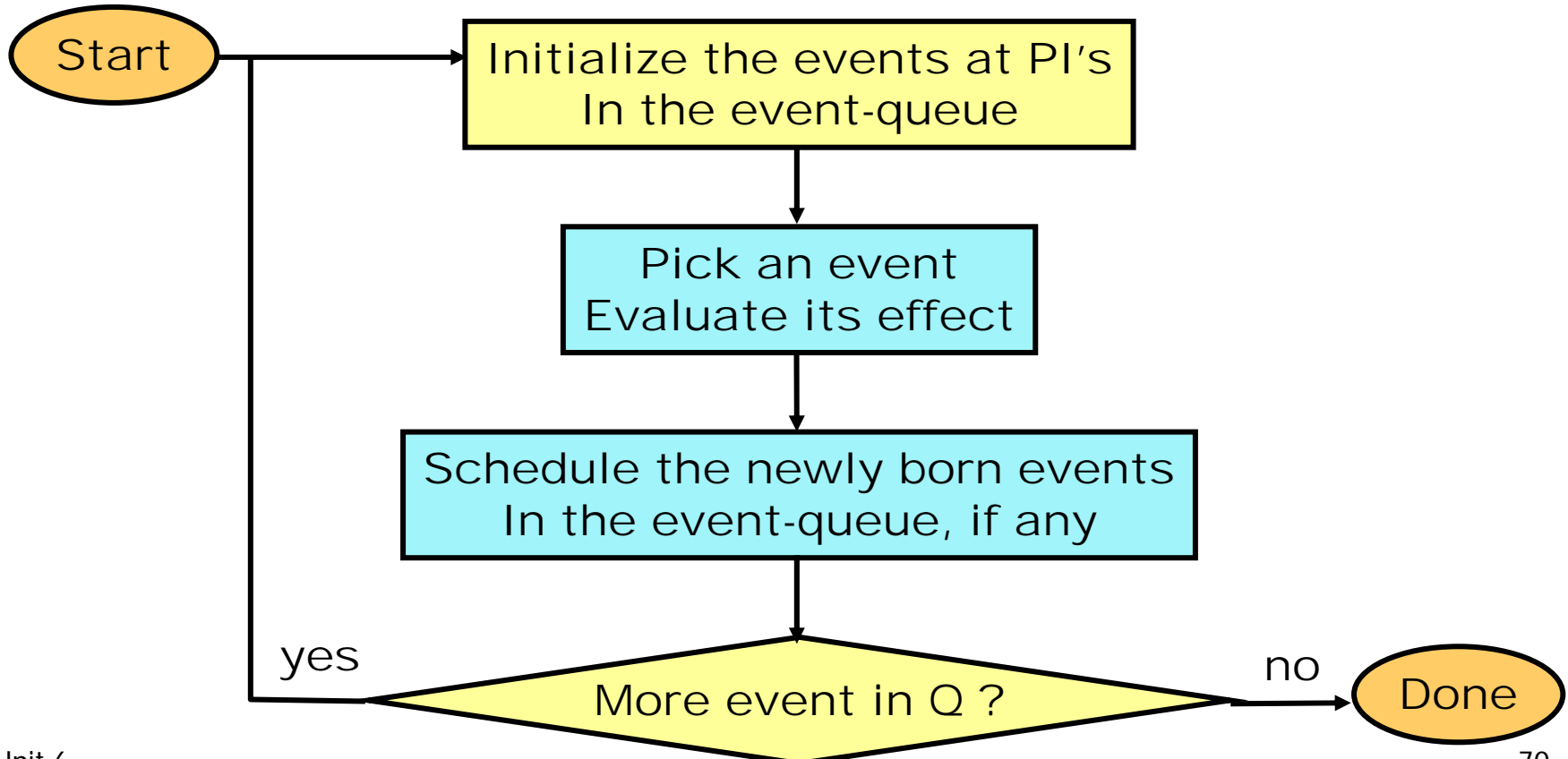 

# Complexity of Fault Simulation


---

 

- Complexity  $\sim F \cdot P \cdot G \sim O(G^3)$
- The complexity is higher than logic simulation by a factor of  $F$ , while usually is much lower than ATPG
- The complexity can be greatly reduced using
  - **Fault dropping** and other advanced techniques
 
# Characteristics of Fault Simulation

- Fault activity with respect to fault-free circuit
  - is often **sparse** both in **time** and in **space**.
- For example
  - F1 is not activated by the given pattern, while F2 affects only the lower part of this circuit.





# Fault Simulation Techniques

---

- Serial Fault Simulation
  - trivial single-fault single-pattern
- Parallel Fault Simulation
- Deductive Fault Simulation
- Concurrent Fault Simulation



# Parallel Fault Simulation

---

- Simulate multiple circuits at a time:
  - The inherent parallel operation of **computer words** to simulate faulty circuits in parallel with fault-free circuit
  - **The number of faulty circuits**, or faults, can be processed simultaneously is limited by the word length, e.g., **32** circuits for a 32-bit computer
- Extra Cost:
  - An **event**, a value-change of a single fault or fault-free circuit leads to the computation of the entire word
  - The **fault-free logic simulation** is repeated for each pass
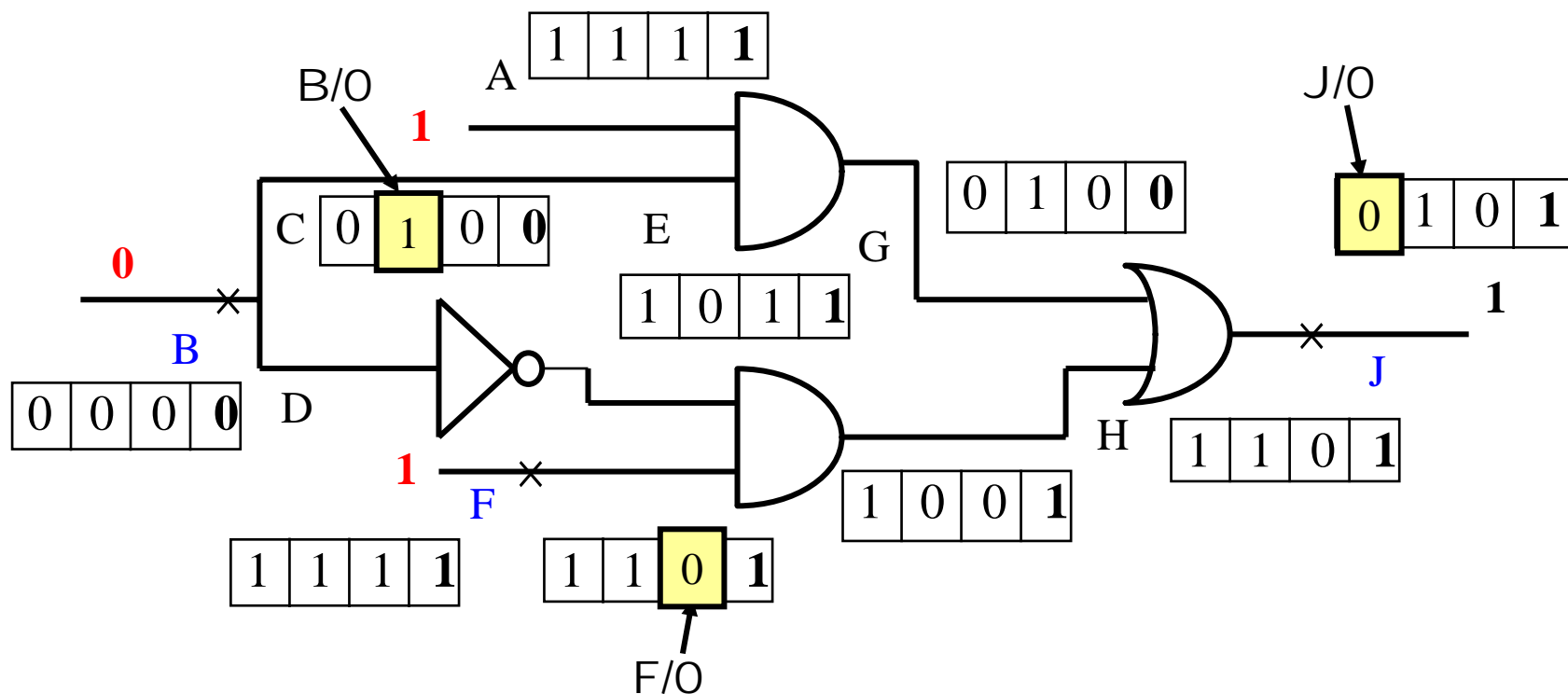 
# Example: Parallel Fault Simulation

- Consider three faults:  
(J s-a-0, B s-a-1, and F s-a-0)
- Bit-space: (FF denotes fault-free)



# Deductive Fault Simulation


---

- Simulate all faulty circuits in one pass
  - For each pattern, sweep the circuit from PI's to PO's.
  - During the process, a **list of faults** is associated with each line
  - The list contains faults that would produce a **fault effect** on this line
  - The **union fault list at every PO** contains the detected faults by the simulated input vector
- Major operation: fault list propagation
  - Related to the gate types and values
  - The size of the list may grow dynamically, leading to a potential **memory explosion problem**

# Illustration of Fault List Propagation

---

Consider a two-input AND-gate:

 

Non-controlling case: **Case 1:**  $A=1, B=1, C=1$  at fault-free,  
 $LC = LA + LB + \{C/0\}$

Controlling cases: **Case 2:**  $A=1, B=0, C=0$  at fault-free,  
 $LC = \overline{LA} * LB + \{C/1\}$

**Case 3:**  $A=0, B=0, C=0$  at fault-free,  
 $LC = LA * LB + \{C/1\}$

$\overline{LA}$  is the set of all faults not in LA

# Fault List Propagation Rule

- Notations:

- Let  $I$  be the set of inputs of a gate  $Z$  with controlling value  $c$  and inversion  $i$   
(i.e.,  $i$  is 0 for AND, OR and 1 for NAND, NOR)
- Let  $C$  be the set of inputs with value  $c$

Non-controlling case:

$$\text{if } C = \phi \text{ then } L_z = \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s-a-}(c \oplus i)\}$$


union

Controlling cases: intersection

$$\text{else } L_z = \left\{ \bigcap_{j \in C} L_j \right\} - \left\{ \bigcup_{j \in I-C} L_j \right\} \cup \{Z \text{ s-a-}(\bar{c} \oplus i)\}$$

# Example: Deductive Simulation (1)

- Consider 3 faults: B/1, F/0, and J/0

 


Fault List at PI's:

$$LB = \{B/1\}, \quad LF = \{F/0\}, \quad LA = \phi, \quad LC=LD = \{B/1\}$$

## Example: Deductive Simulation (2)

- Consider 3 faults: B/1, F/0, and J/0

 

Fault Lists at G and E:

$$\mathbf{LB} = \{\mathbf{B/1}\}, \mathbf{LF} = \{\mathbf{F/0}\}, \mathbf{LA} = \phi, \mathbf{LC=LD} = \{\mathbf{B/1}\},$$


$$\mathbf{LG} = (\overline{\mathbf{LA}} * \mathbf{LC}) = \{\mathbf{B/1}\}$$

$$\mathbf{LE} = (\mathbf{LD}) = \{\mathbf{B/1}\}$$



## Example: Deductive Simulation (3)

- Consider 3 faults: B/1, F/0, and J/0

 

Computed Fault List at H:


**$LB = \{B/1\}$ ,  $LF = \{F/0\}$ ,  $LC=LD = \{B/1\}$ ,**

**$LG = \{B/1\}$ ,  $LE = \{B/1\}$**

**$LH = (LE + LF) = \{B/1, F/0\}$**

## Example: Deductive Simulation (4)

- Consider 3 faults: B/1, F/0, and J/0

 

Final Fault List at the output J:

**LB = {B/1}, LF = {F/0}, LC=LD = {B/1},**


**LG = {B/1}, LE = {B/1}**

**LH = {B/1, F/0},**

**LJ = {F/0, J/0}**

# Example: Deductive Simulation

- When A changes from 1 to 0

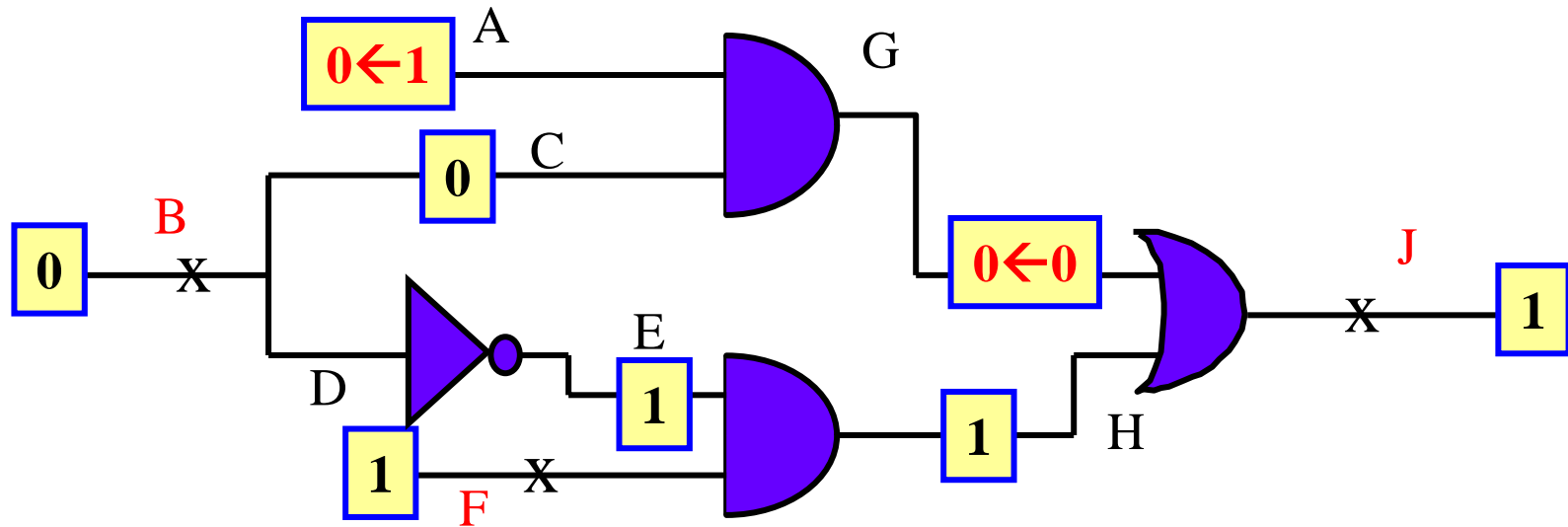

Event-driven operation:

$LB = \{B/1\}$ ,  $LF = \{F/0\}$ ,  $LA = \phi$

$LC=LD = \{B/1\}$ ,  $LG = \phi$ ,


$LE = \{B/1\}$ ,  $LH = \{B/1, F/0\}$ ,  $LJ = \{B/1, F/0, J/0\}$

# Concurrent Fault Simulation

---


- Simulate all faulty circuits in one pass:
  - Each gate retains a list of fault copies and each of them stores the status of a fault exhibiting difference from fault-free values
- Simulation mechanism
  - is similar to the conceptual fault simulation except that only the dynamical difference w.r.t. fault-free circuit is retained.
- Theoretically,
  - all faults in a circuit can be processed in one pass
- Practically,
  - memory explosion problem may restrict the number of faults that can be processed in each pass

# Concurrent Fault Simulation

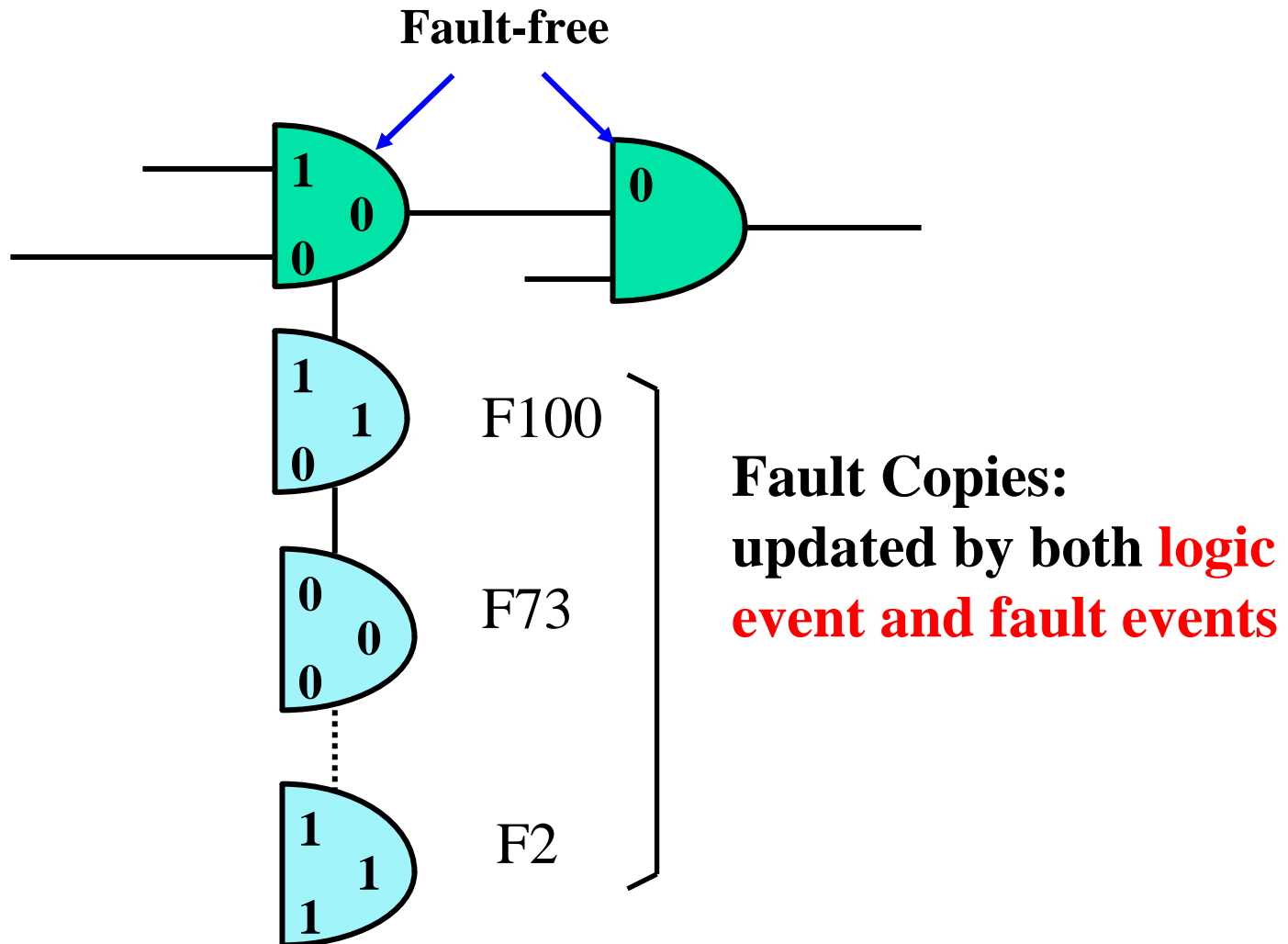

# Example: Concurrent Simulation (1)


- Consider 3 faults: B/1, F/0, and J/0

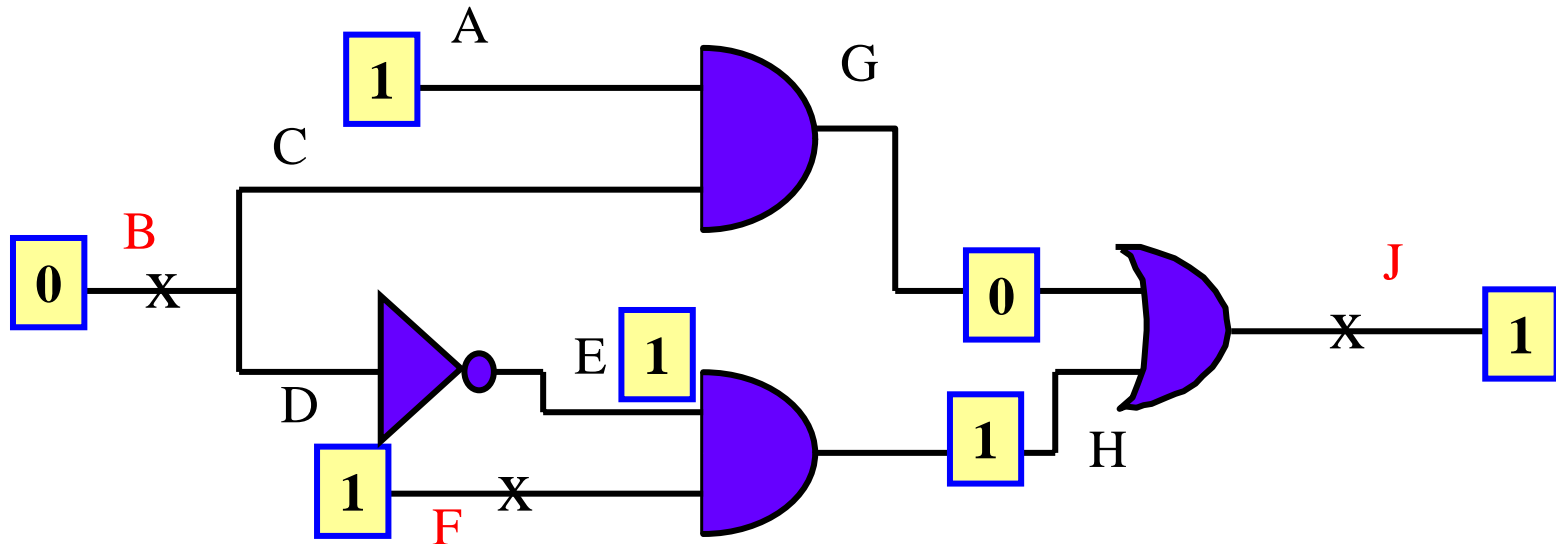

$LG = \{10\_0, B/1:11\_1\}$      $LE = \{0\_1, B/1:1\_0\}$

## Example: Concurrent Simulation (2)

- Consider 3 faults: B/1, F/0, and J/0

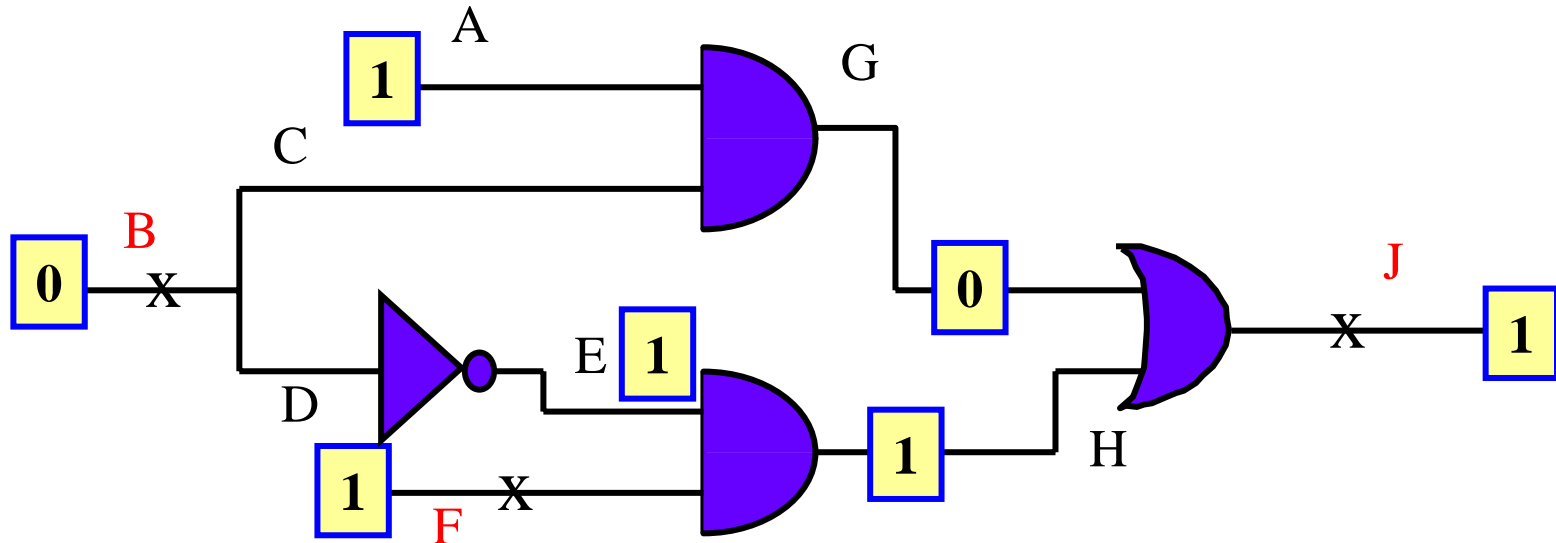


**LG = {10\_0, B/1:11\_1}    LE = {0\_1, B/1:1\_0}**

**LH = {11\_1, B/1:01\_0, F/0:10\_0}**

## Example: Concurrent Simulation (3)

- Consider 3 faults: B/1, F/0, and J/0

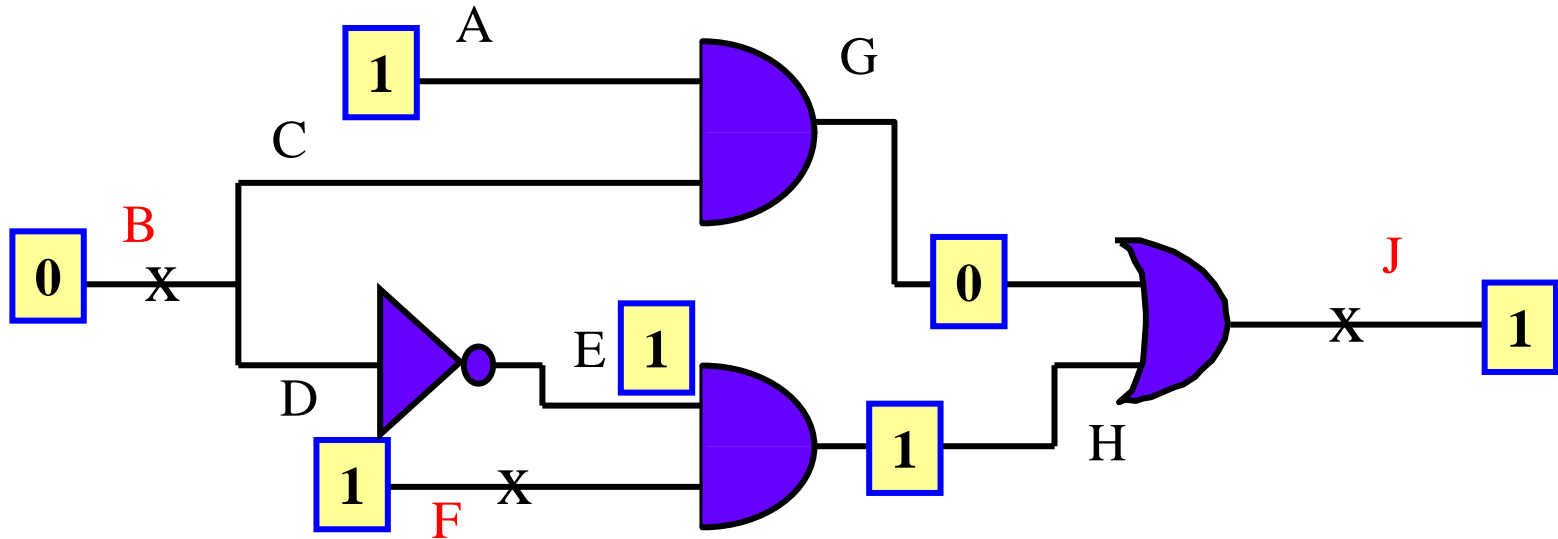

$LG = \{10\_0, B/1:11\_1\}$      $LE = \{0\_1, B/1:1\_0\}$


$LH = \{11\_1, B/1:01\_0, F/0:10\_0\}$

$LJ = \{01\_1, B/1:10\_1, F/0:00\_0, J/0:01\_0\}$



## Example: Concurrent Simulation (4)

- When A changes from 1 to 0

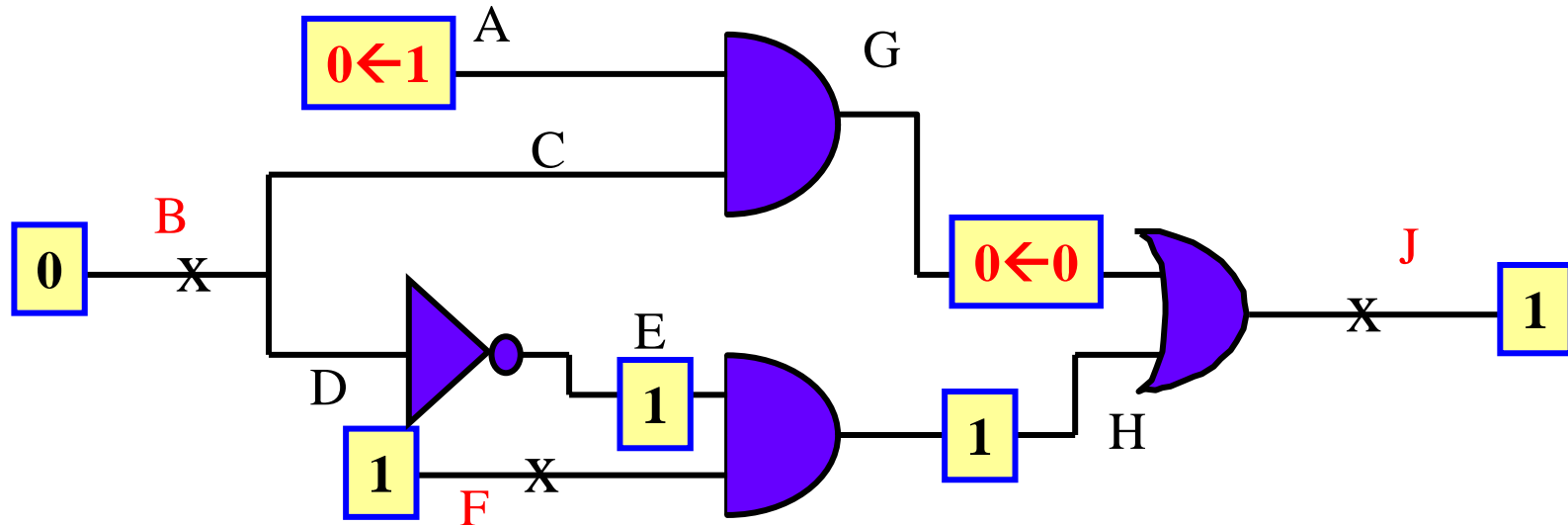


$LG = \{00\_0, B/1:01\_0\}$      $LE = \{0\_1, B/1:1\_0\}$

$LH = \{11\_1, B/1:01\_0, F/0:10\_0\}$



$LJ = \{01\_1, \text{B/1:00\_0}, F/0:00\_0, J/0:01\_0\}$

# Fault List of AND Gate

 
  
# Fault List Propagation

These 2 faults are not propagated after evaluation



# Parallel-Pattern Single-Fault Simulation

---


- Basic Idea:
  - Event Driven + Parallel Simulation
- Parallel-Pattern Simulation
  - Many patterns are simulated in parallel for both fault-free circuit and faulty circuits
  - The number of patterns is a multiple of the computer word-length
- Event-Driven
  - reduction of logic event simulation time
- Simple and Extremely Efficient
  - basis of most modern combinational fault simulators

# Example: Parallel Pattern Simulation


- Consider one fault F/0 and four patterns: P3,P2,P1,P0

Bit-Space: 

P3	P2	P1	P0
----	----	----	----

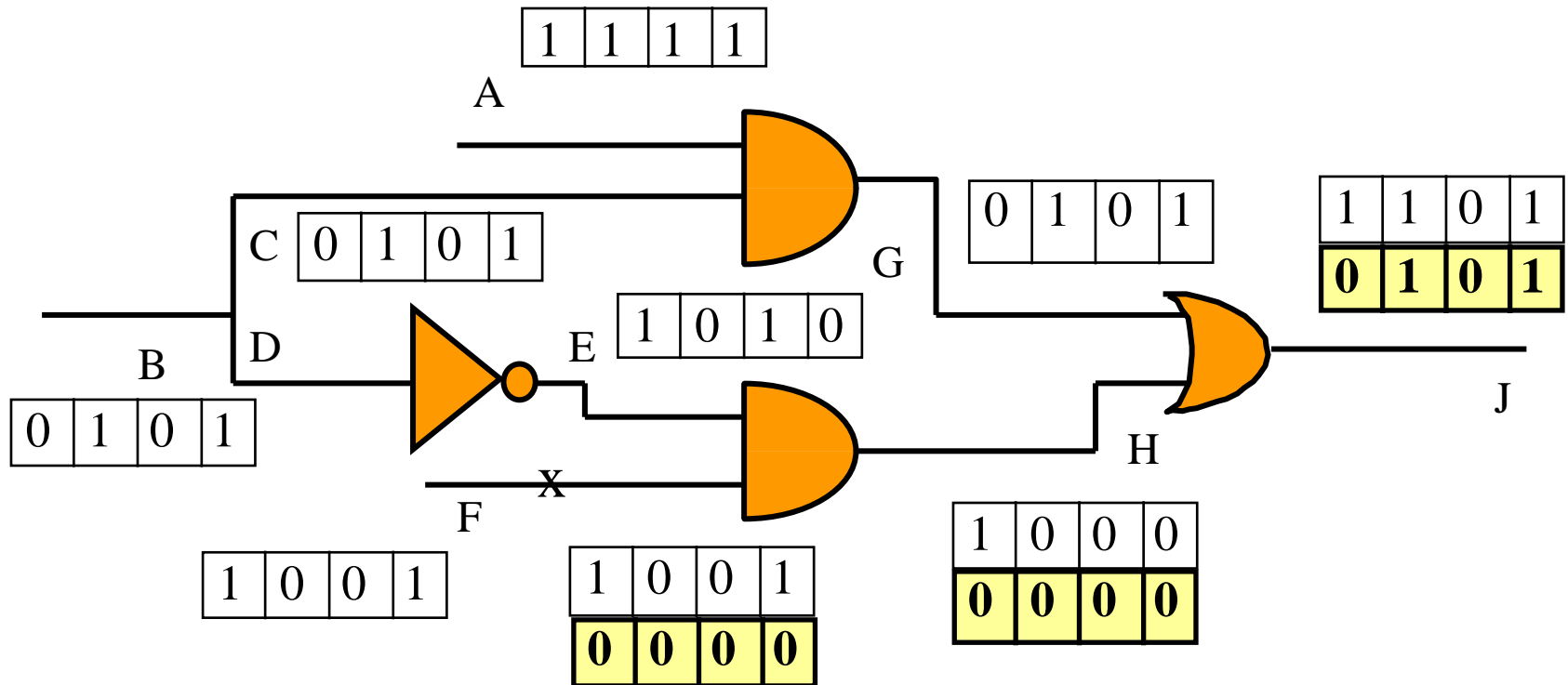


# Sensitive Input and Critical Path

 

- Sensitive Input of a gate:
  - A gate input  $i$  is **sensitive** if complementing the value of  $i$  changes the value of the gate output
- Critical line
  - Assume that the fault-free value of  $w$  is  $v$  in response to  $t$
  - A line  $w$  is **critical** w.r.t. a pattern  $t$  iff  $t$  detects the fault  **$w$  stuck-at  $v$**
- Critical paths
  - Paths consisting of critical lines only

# Basics of Critical Path Tracing

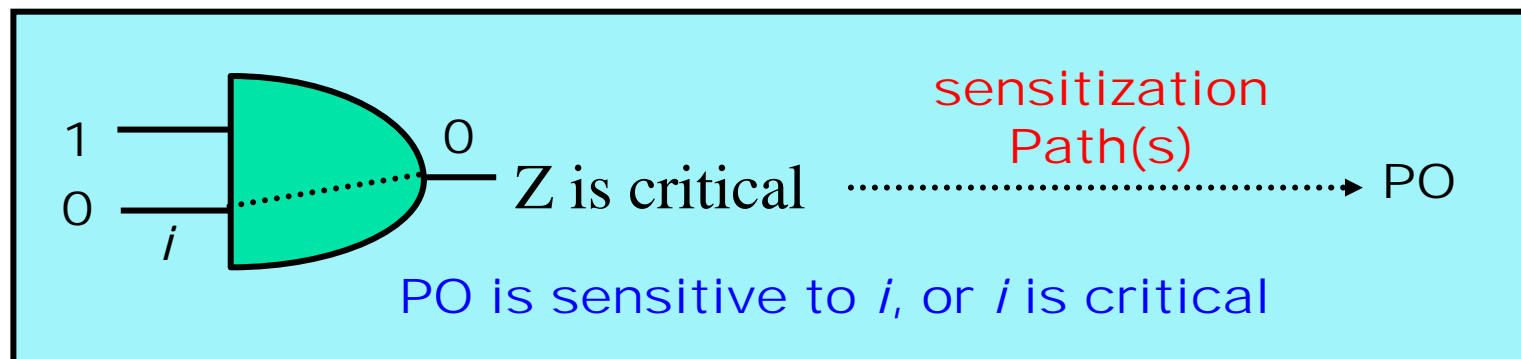

- A gate input  $i$  is critical w.r.t. a pattern  $t$  if
  - (1) the gate output is critical and
  - (2)  $i$  is a sensitive input to  $t$
  - Use recursion to prove that  $i$  is also critical
- In a fanout-free circuit
  - the criticality of a line can be determined by backward traversing the sensitive gate inputs from PO's, in linear time


# Analysis of Critical Path Tracing

---

- Three-step Procedure:
  - Step 1: Fault-free simulation
  - Step 2: Mark the sensitive inputs of each gate
  - Step 3: Identification of the critical lines by backward critical path tracing)
- Complexity is  $O(G)$ 
  - Where  $G$  is the gate count
  - for fanout-free circuits --- very rare in practice
- Application
  - Applied to fanout-free regions, while stem faults are still simulated by parallel-pattern fault simulator.



# Example of Critical Path Tracing

 


**Detected faults in the fanout-free region:**  
**{J/0, H/0, F/0, E/0, D/1}**

**Question: is B stuck-at-1 detected ?**

 
# Anomaly of Critical Path Tracing

- **Stem criticality** is hard to infer from branches.  
E.g. is B/1 detectable by the given pattern?



- It turns out that **B/1 is not detectable** even though both C and D are critical, because their effects cancel out each other at gate J, (i.e., **fault masking problem**)
- There is also a so-called **multiple path sensitization problem**.

# Multiple Path Sensitization

 

Both **C** and **D** are not critical, yet **B is critical** and **B/0** can be **detected at J by multiple path sensitization**.



# Sequential Fault Simulation

---

- Modern Techniques:
  - Fault simulation without restoration
  - Parallel fault simulation
  - Adoption of advanced combinational techniques
  - Management of hypertrophic faults
  - Other techniques:
    - parallel-sequence and parallel-pattern

# Sequential Design Model

## Sequential Circuits

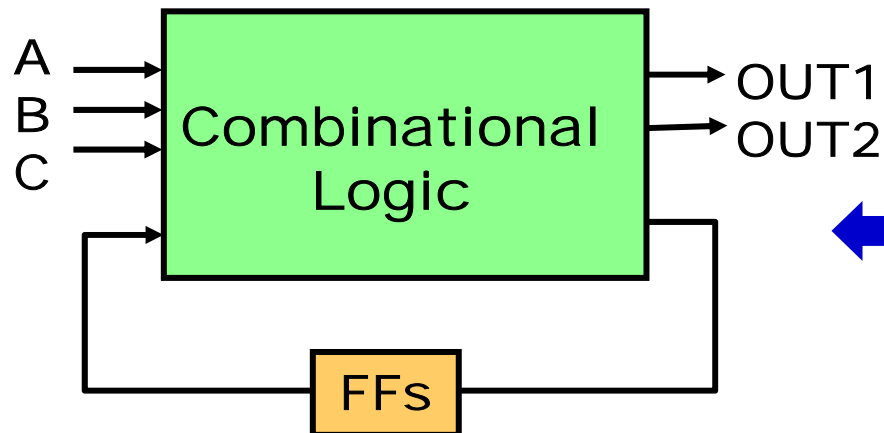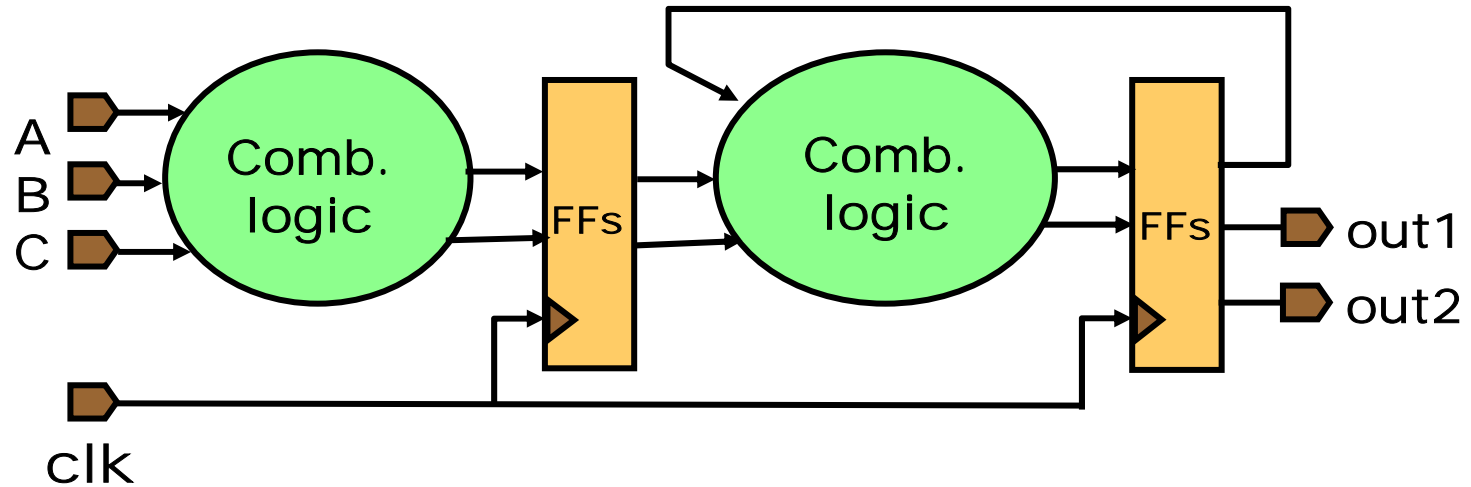


← Hoffman Model
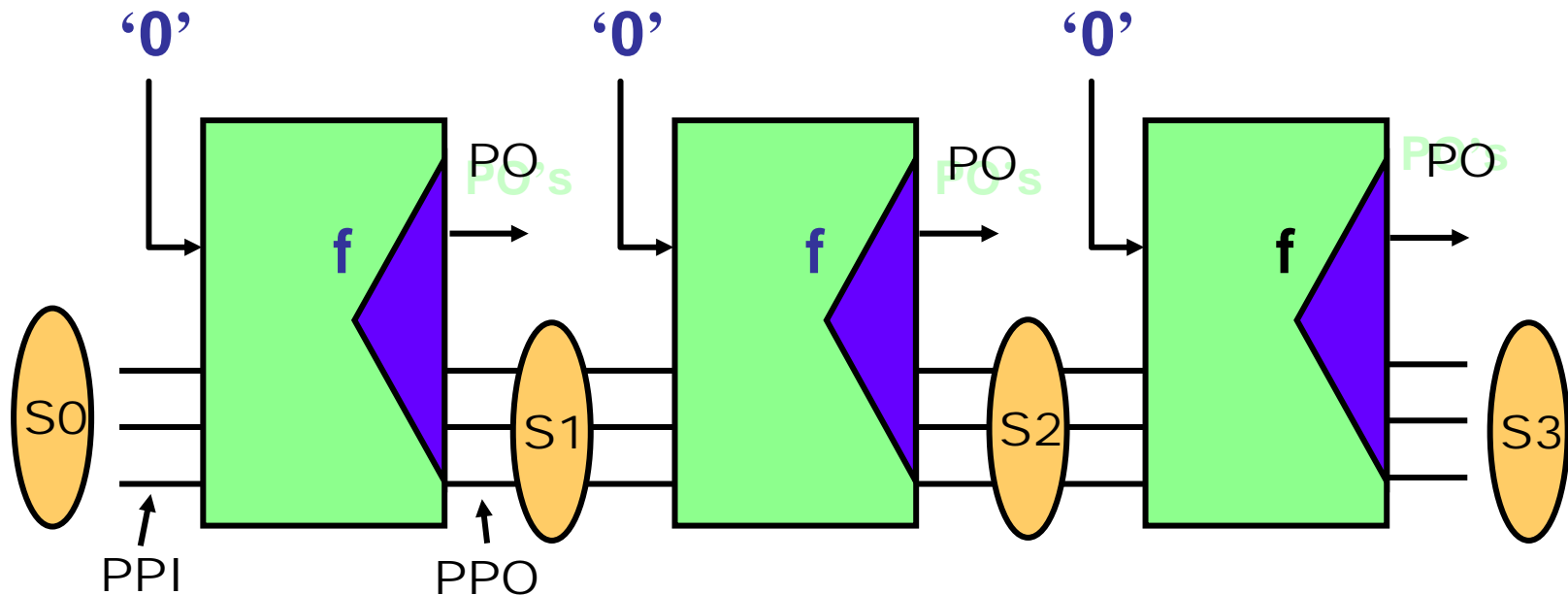
# Time-Frame-Expansion Model

Ex: Input Sequence ('0', '0', '0')

State Sequence ( $S0 \rightarrow S1 \rightarrow S2 \rightarrow S3$ )




Notations: PPI: pseudo primary inputs (I.e., outputs of flip-flops)  
PPO: pseudo primary outputs (I.e., inputs of flip-flops)

**A single fault becomes multiple faults in the time-frame-expansion model**
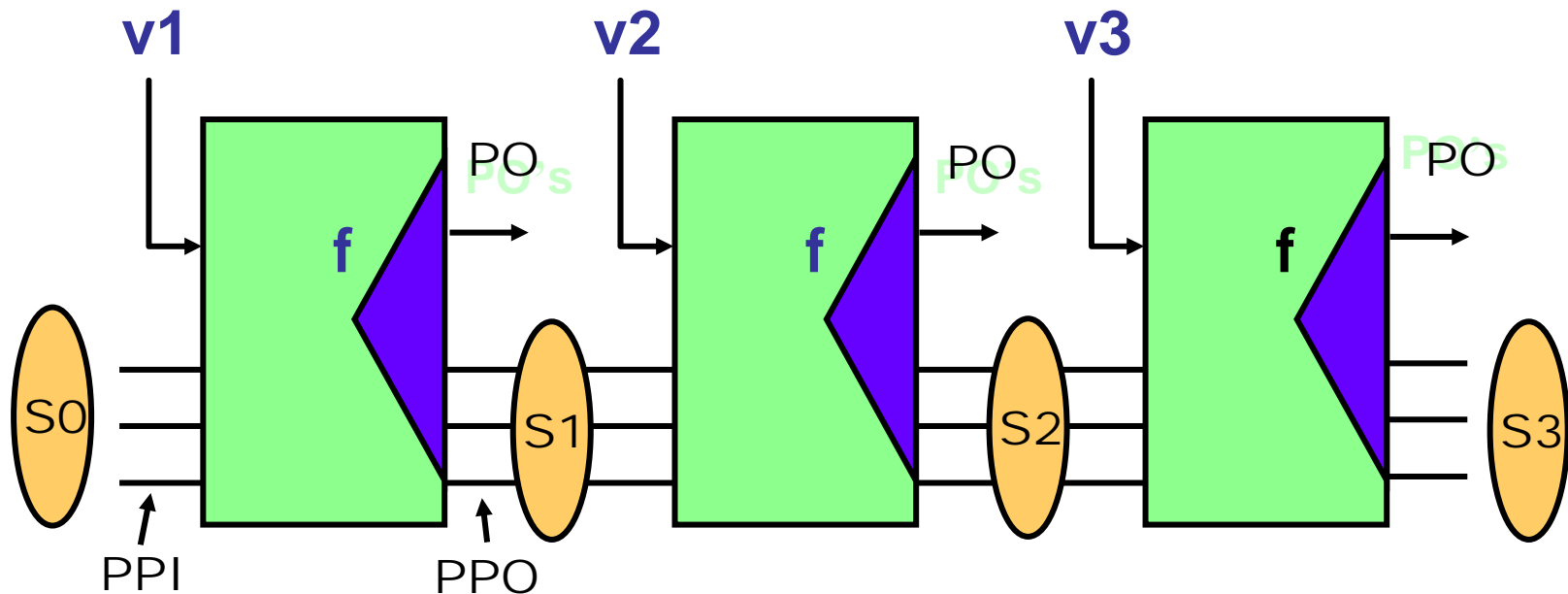
# Parallel Pattern Simulation for Sequential Circuits?

Ex: Input Sequence ( $v1, v2, v3, \dots$ )


State Sequence ( $S0 \rightarrow S1 \rightarrow S2 \rightarrow S3 \rightarrow \dots$ )



If (next-state function) depends on only  $k$  previous input vectors  
→ Then parallel pattern simulation would take  $(k+1)$  passes to converge !

# Outline

---

- Introduction
- Fault Modeling
- Fault Simulation
-  • **Test Generation**
- Design For Testability



# Outline of ATPG (Automatic Test Pattern Generation)

---

- Test Generation (TG) Methods
  - Based on Truth Table
  - Based on Boolean Equation
  - Based on Structural Analysis
  - D-algorithm [Roth 1967]
  - 9-Valued D-algorithm [Cha 1978]
  - PODEM [Goel 1981]
  - FAN [Fujiwara 1983]

# General ATPG Flow

---

- ATPG (Automatic Test Pattern Generation)
  - Generate a set of vectors for a set of target faults
- Basic flow
  - Initialize the vector set to NULL**
  - Repeat**
    - Generate a new test vector**
    - Evaluate fault coverage for the test vector**
    - If the test vector is acceptable, then add it to the vector set**
  - Until required fault coverage is obtained**
- To accelerate the ATPG
  - **Random patterns** are often generated first to detect easy-to-detect faults, then a deterministic TG is performed to generate tests for the remaining faults


# Combinational ATPG

---


- Test Generation (TG) Methods
  - Based on Truth Table
  - Based on Boolean Equation
  - Based on Structural Analysis
- Milestone Structural ATPG Algorithms
  - D-algorithm [Roth 1967]
  - 9-Valued D-algorithm [Cha 1978]
  - PODEM [Goel 1981]
  - FAN [Fujiwara 1983]
 
# A Test Pattern

A Fully Specified Test Pattern  
(every PI is either 0 or 1)



 
A Partially Specified Test Pattern  
(certain PI's could be **undefined**)



# Test Generation Methods

## (From Truth Table)

 **Ex: How to generate tests for the stuck-at 0 fault (fault  $\alpha$ )?**



abc	f	$f\alpha$
000	0	0
001	0	0
010	0	0
011	0	0
100	0	0
101	1	1
110	1	0
111	1	1

# Test Generation Methods

## (Using Boolean Equation)

$$f = ab + ac, f_{\alpha} = ac$$

$T_{\alpha}$  = the set of all tests for fault  $\alpha$


$$= \text{ON\_set}(f \oplus f_{\alpha})$$

$$= \text{ON\_set}(f) * \text{OFF\_set}(f_{\alpha}) + \text{OFF\_set}(f) * \text{ON\_set}(f_{\alpha})$$

$$= \{(a,b,c) \mid (ab+ac)(ac)' + (ab+ac)'(ac) = 1\} \leftarrow \text{Boolean equation}$$

$$= \{(a,b,c) \mid abc' = 1\}$$

$$= \{(110)\}.$$

 

High complexity !!

Since it needs to compute the **faulty function** for each fault.

\* **ON\_set(f)**: All input combinations to which f evaluates to 1.

**OFF\_set(f)**: All input combinations to which f evaluates to 0.

Note: a **function** is characterized by its **ON\_SET**

# Boolean Difference

- Physical Meaning of Boolean Difference
  - For a logic function  $F(X)=F(x_1, \dots, x_i, \dots, x_n)$ , find **all the input combinations** that make a value-change at  $x_i$  also cause a value-change at  $F$ .
- Logic Operation of Boolean Difference
  - The Boolean difference of  $F(X)$  w.r.t. input  $x_i$  is



$$dF(x)/dx_i = F_i(0) \oplus F_i(1) = F_i(0) \cdot F_i(1)' + F_i(0)' \cdot F_i(1)$$

Where


$$F_i(0) = F(x_1, \dots, 0, \dots, x_n)$$

$$F_i(1) = F(x_1, \dots, 1, \dots, x_n)$$

## Illustrations of Boolean Difference

  

# Chain Rule

 

$$\begin{array}{l} f = AB \\ G = f + CD \end{array} \quad \rightarrow \quad \begin{array}{l} dG/df = (C' + D') \\ df/dA = B \end{array}$$


$$\rightarrow dG/dA = (dG/df) \cdot (df/dA) = (C' + D') \cdot B$$

An Input vector  $v$  sensitizes a fault effect from **A to G**  
Iff  $v$  sensitizes the effect from **A to f** and from **f to G**



 
# Boolean Difference (con't)

- Boolean Difference
  - With respect to an **internal signal**,  $w$ , Boolean difference represents the set of **input combinations that sensitize** a fault effect from  $w$  to the primary output  $F$
- Calculation
  - **Step 1**: convert the function  $F$  into a new one  $G$  that takes the **signal  $w$  as an extra primary input**
  - **Step 2**:  $dF(x_1, \dots, x_n)/dw = dG(x_1, \dots, x_n, w)/dw$



# Test Gen. By Boolean Difference

Case 1: Faults are present at PIs.

 

Fault Sensitization Requirement:

$$dF/da = F(a=0) \oplus F(a=1) = 0 \oplus (b+c) = (b+c)$$

Test-set for  $a$  s-a-1 =  $\{(a,b,c) \mid \underline{a'} \cdot (b+c)=1\} = \{(01x), (0x1)\}$ .

Test-set for  $a$  s-a-0 =  $\{(a,b,c) \mid \underline{a} \cdot (b+c)=1\} = \{(11x), (1x1)\}$ .


No need to compute  
The faulty function !!

Fault activation  
requirement

Fault sensitization  
requirement

# Test Generation By Boolean Difference (con't)

 **Case 2: Faults are present at internal lines.**



$$G(\text{i.e., } F \text{ with } h \text{ floating}) = h + ac$$
$$dG/dh = G(h=0) \oplus G(h=1) = (ac \oplus 1) = (a' + c')$$

Test-set for  $h$  s-a-1 is

$$\{(a,b,c) \mid h' \cdot (a' + c') = 1\} = \{(a,b,c) \mid (a' + b') \cdot (a' + c') = 1\} = \{(0xx), (x00)\}.$$


Test-set for  $h$  s-a-0 is

$$\{(a,b,c) \mid \underline{h} \cdot \underline{(a' + c')} = 1\} = \{(110)\}.$$

For fault activation      For fault sensitization


# Outline of ATPG (Automatic Test Pattern Generation)

---

- Test Generation (TG) Methods
  - Based on Truth Table
  - Based on Boolean Equation
  - Based on Structural Analysis
  -  – D-algorithm [Roth 1967]
  - 9-Valued D-algorithm [Cha 1978]
  - PODEM [Goel 1981]
  - FAN [Fujiwara 1983]
 
# Test Generation Method (From Circuit Structure)


- Two basic goals
  - (1) **Fault activation** (FA)
  - (2) **Fault propagation** (FP)
  - Both of which requires **Line Justification** (LJ), i.e., finding input combinations that force certain signals to their desired values
- Notations:
  - **1/0** is denoted as **D**, meaning that good-value is 1 while faulty value is 0
  - Similarly, **0/1** is denoted as **D'**
  - Both D and D' are called fault effects (FE)




 
# Common Concepts for Structural TG

- Fault activation
  - Setting the faulty signal to either 0 or 1 is a Line Justification problem
- Fault propagation
  - (1) select a path to a PO → decisions
  - (2) Once the path is selected → a set of line justification (LJ) problems are to be solved
- Line Justification
  - Involves decisions or implications
  - Incorrect decisions: need backtracking

To justify  $c=1 \rightarrow a=1$  and  $b=1$  (implication)  
To justify  $c=0 \rightarrow a=0$  or  $b=0$  (decision)



# Ex: Decision on Fault Propagation

  

decision tree


- Fault activation
  - $G1=0 \rightarrow \{ a=1, b=1, c=1 \} \rightarrow \{ G3=0 \}$
- Fault propagation: through **G5** or **G6**
- Decision through **G5**:
  - $G2=1 \rightarrow \{ d=0, a=0 \} \rightarrow$  inconsistency at  $a \rightarrow$  backtrack !!
- Decision through **G6**:
  - $\rightarrow G4=1 \rightarrow e=0 \rightarrow$  done !! The resulting test is (111x0)

**D-frontiers**: are the gates whose output value is  $x$ , while one or more Inputs are  $D$  or  $D'$ . For example, initially, the D-frontier is  $\{ G5, G6 \}$ .
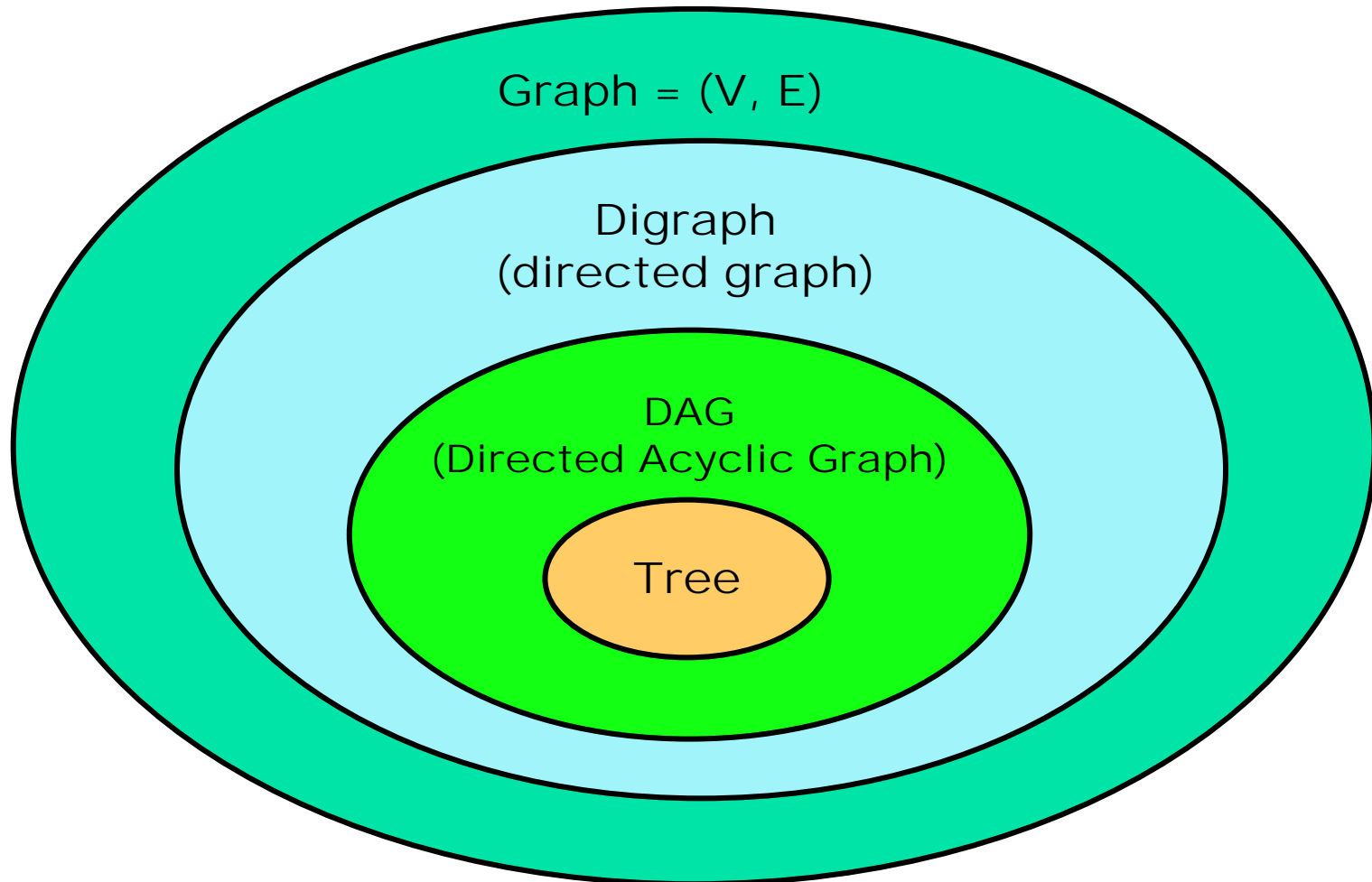
# Various Graphs



---

A **Combinational Circuit**: is usually modeled as a **DAG**, but not **tree**





# Ex: Decisions On Line Justification

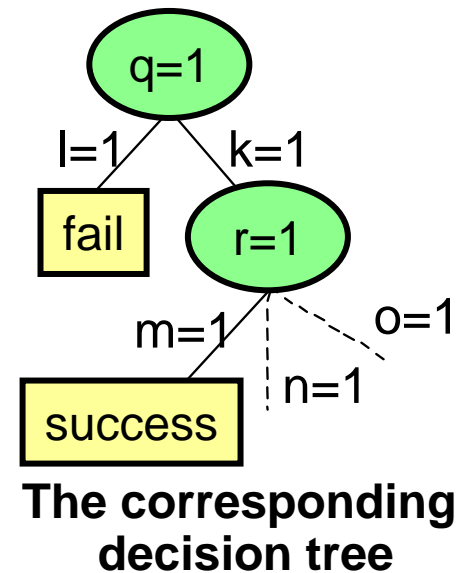 

**J-frontier:** is the set of gates whose output value is known (i.e., 0 or 1), but is not implied by its input values.  
 Ex: initially, J-frontier is  $\{q=1, r=1\}$

- FA  $\rightarrow$  set h to 0
- FP  $\rightarrow e=1, f=1 (\rightarrow o=0)$  ; FP  $\rightarrow q=1, r=1$
- To justify  $q=1 \rightarrow l=1$  or  $k=1$  Decision point
- Decision:  $l=1 \rightarrow c=1, d=1 \rightarrow m=0, n=0 \rightarrow r=0 \rightarrow$  inconsistency at r  $\rightarrow$  backtrack !
- Decision:  $k=1 \rightarrow a=1, b=1$
- To justify  $r=1 \rightarrow m=1$  or  $n=1 (\rightarrow c=0$  or  $d=0) \rightarrow$  Done ! (J-frontier is  $\phi$ )

# Branch-and-Bound Search

---

- Test Generation
  - Is a branch-and-bound search
  - Every decision point is a branching point
  - If a set of decisions lead to a conflict (or bound), a backtrack is taken to explore other decisions
  - A test is found when
    - (1) fault effect is propagated to a PO
    - (2) all internal lines are justified
  - No test is found after all possible decisions are tried → Then, target fault is undetectable
  - Since the search is exhaustive, it will find a test if one exists

For a combinational circuit, an undetectable fault is also a redundant fault → Can be used to simplify circuit.




# Implications

---


- Implications
  - Computation of the values that can be uniquely determined
    - **Local implication**: propagation of values from one line to its immediate successors or predecessors
    - **Global implication**: the propagation involving a larger area of the circuit and re-convergent fanout
- Maximum Implication Principle
  - Perform as many implications as possible
  - It helps to either reduce the number of problems that need decisions or to **reach an inconsistency sooner**

# Local Implications (Forward)

Before

 
 
 


J-frontier={ ...,a }

 


D-frontier={ ...,a }

After

   





J-frontier={ ... }

 





D-frontier={ ... }

# Local Implications (Backward)


Before

    

After

    

# Global Implications

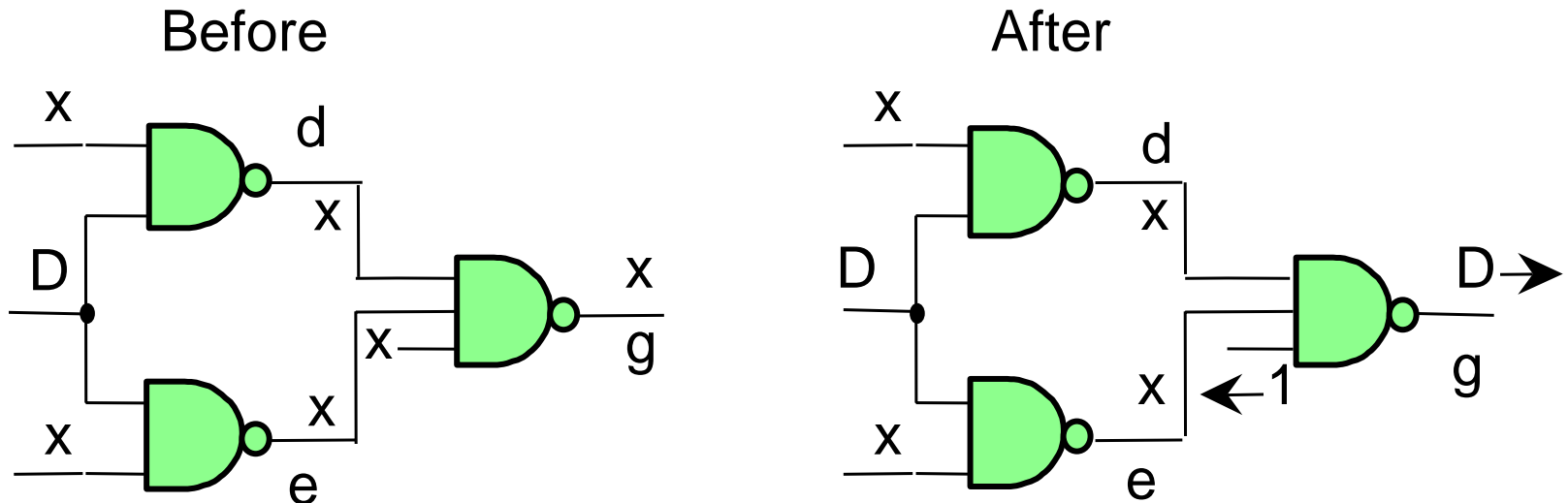

- Unique D-Drive Implication

- Suppose D-frontier (or D-drive) is  $\{d, e\}$ ,  $\rightarrow$  g is a **dominator** for both d and e, hence a **unique D-drive** is at g


**g is called a dominator of d:**

**because every path from d to an PO passes through g**

 
# Learning for Global Implication

- Static Learning
  - Global implication derived by **contraposition law**
  - Learn static (i.e., **input independent**) signal implications
- Dynamic Learning
  - **Contraposition law + other signal values**
  - Is input pattern dependent

$$A \rightarrow B \Rightarrow \sim B \rightarrow \sim A$$



 
F=1 implies B=1  
Because  $B=0 \rightarrow F=0$   
(Static Learning)



F=0 implies B=0 **When A=1**  
Because  $\{B=1, A=1\} \rightarrow F=1$   
(Dynamic Learning)


# Early Detection of Inconsistency

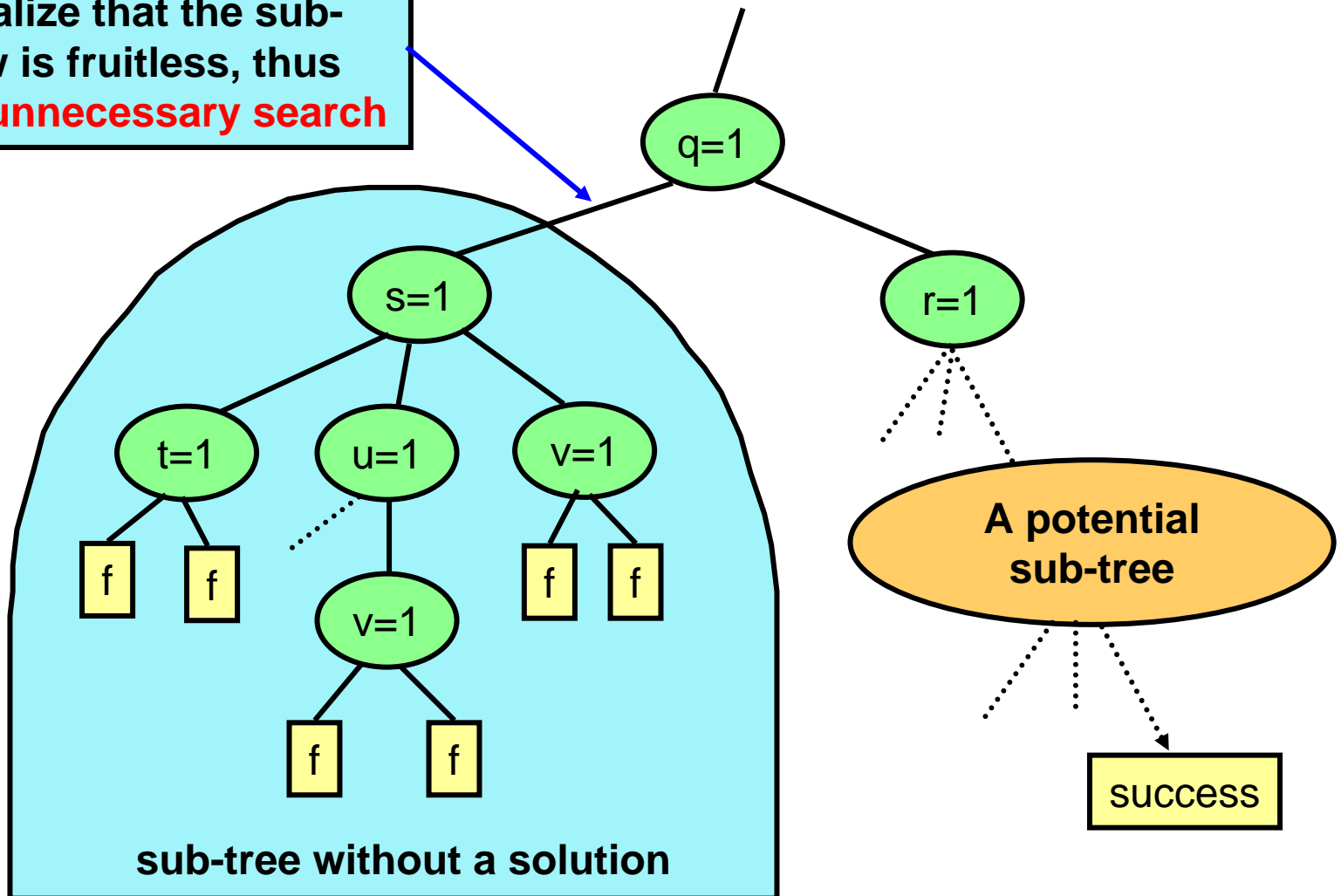**Aggressive implication** may help to realize that the sub-tree below is fruitless, thus avoiding **unnecessary search**





- $\{0, 1, x, D, D'\}$

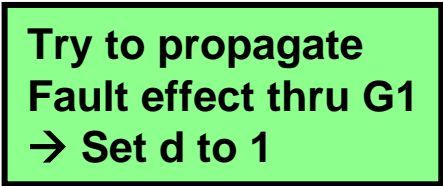


**Try to propagate  
Fault effect thru G2  
→ Set j,k,l,m to 1**




Conflict at k  
→ Backtrack !
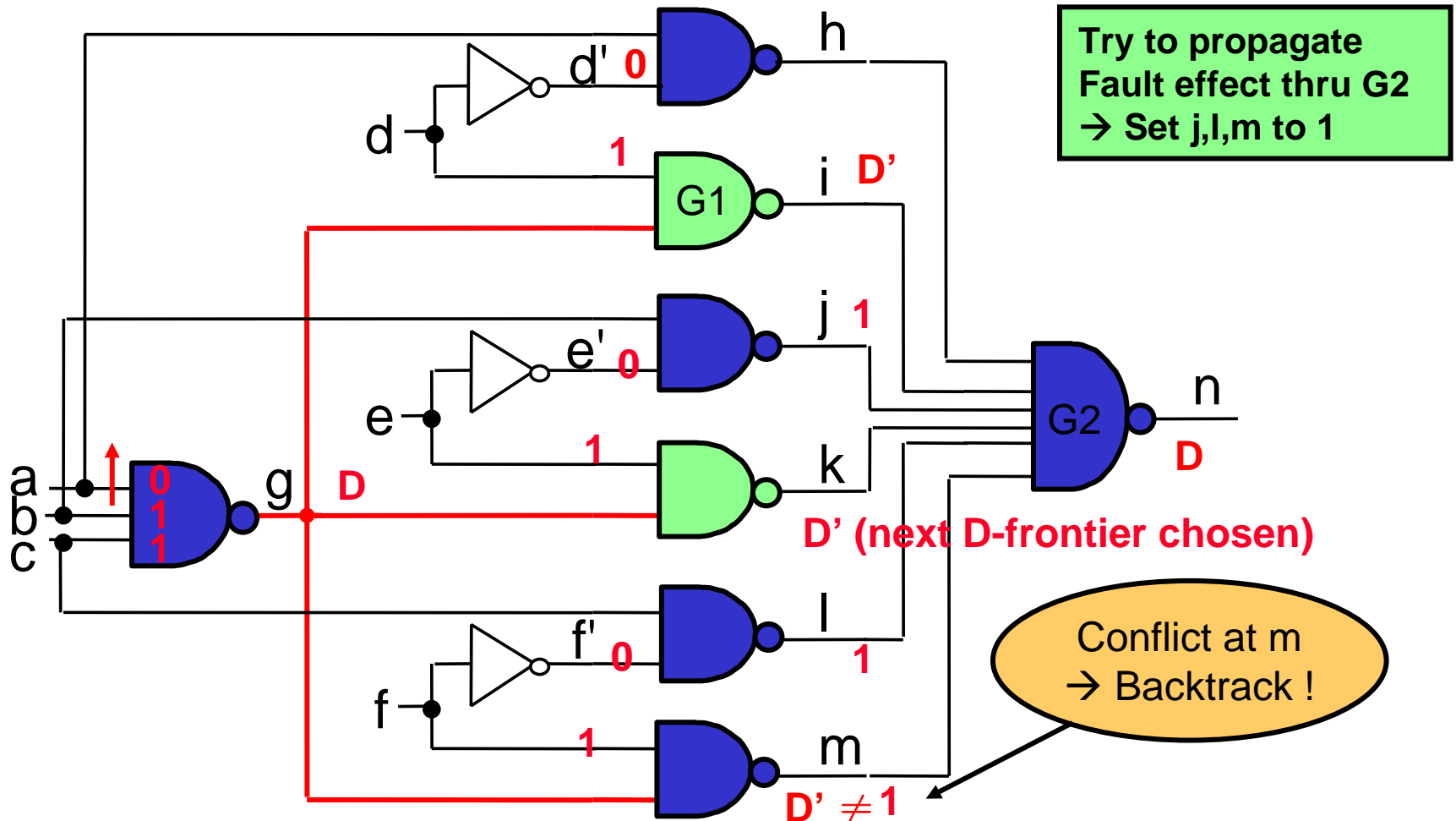
## Ex: D-Algorithm (2/3)

- Five logic values
  - $\{0, 1, x, D, D'\}$



- $\{0, 1, x, D, D'\}$

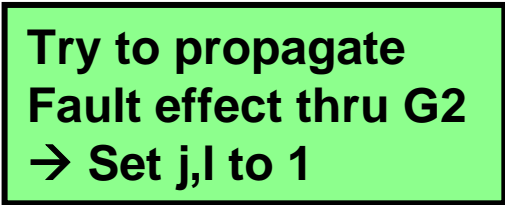



**Fault propagation  
and line justification  
are both complete  
→ A test is found !**

**This is a case of multiple path sensitization !**

e=1	k=D' e'=0 j=1	Propagate via k
l=1 m=1	n=D f'=0 f=1 m=D'	Propagate via n  <b>Contradiction</b>
f=1	m=D' f'=0 l=1 n=D	Propagate via m
 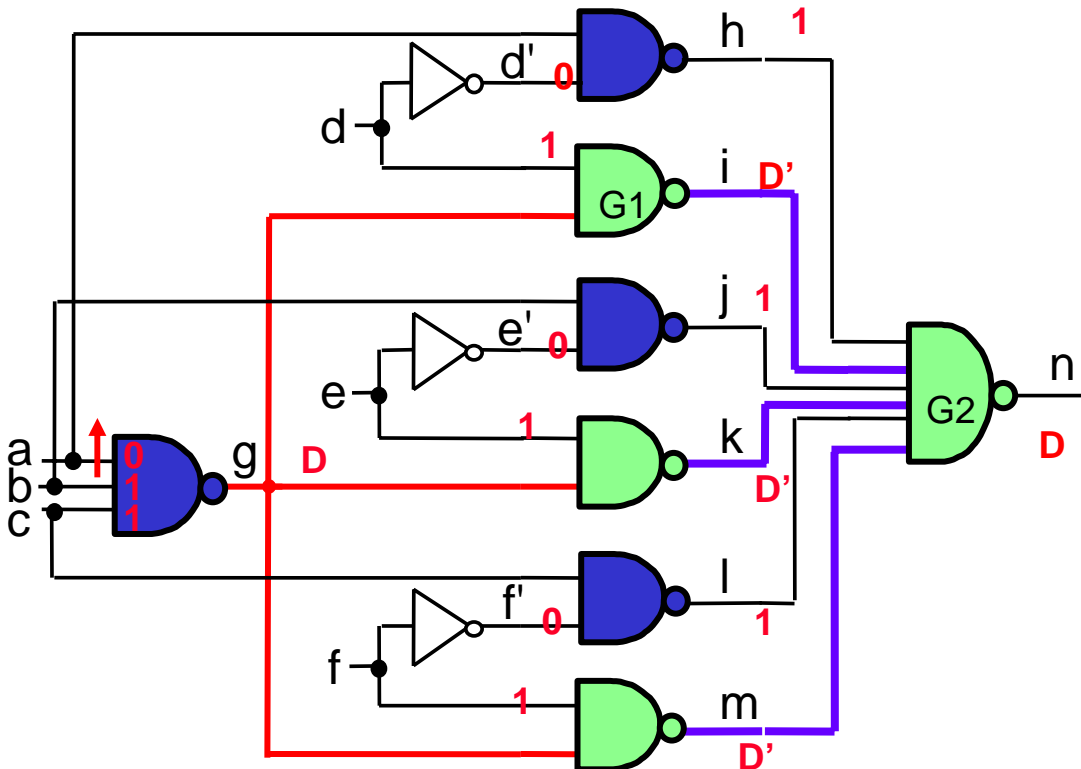
# Decision Tree on D-Frontier


- The decision tree below
  - Node  $\rightarrow$  D-frontier
  - Branch  $\rightarrow$  Decision Taken
  - A **Depth-First-Search** (DFS) strategy is often used


 
## 9-Value D-Algorithm

---

- Logic values (fault-free / faulty)
  - $\{0/0, 0/1, 0/u, 1/0, 1/1, 1/u, u/0, u/1, u/u\}$ ,
  - where  $0/u=\{0,D'\}$ ,  $1/u=\{D,1\}$ ,  $u/0=\{0,D\}$ ,  $u/1=\{D',1\}$ ,  $u/u=\{0,1,D,D'\}$ .
- Advantage:
  - Automatically considers **multiple-path sensitization**, thus reducing the amount of search in D-algorithm
  - The speed-up is **NOT** very significant in practice because **most faults are detected through single-path sensitization**



# Final Step of 9-Value D-Algorithm

---

- To derive the test vector
  - $A = (0/1) \rightarrow 0$  (take the fault-free one)
  - $B = (1/u) \rightarrow 1$
  - $C = (1/u) \rightarrow 1$
  - $D = (u/1) \rightarrow 1$
  - $E = (u/1) \rightarrow 1$
  - $F = (u/1) \rightarrow 1$
- The final vector
  - $(A,B,C,D,E,F) = (0, 1, 1, 1, 1, 1)$



# Outline of ATPG (Automatic Test Pattern Generation)

---

- Test Generation (TG) Methods

- Based on Truth Table
- Based on Boolean Equation
- Based on Structural Analysis
- D-algorithm [Roth 1967]
- 9-Valued D-algorithm [Cha 1978]
- PODEM [Goel 1981]
- FAN [Fujiiwara 1983]




# PODEM: Path-Oriented DEcision Making

---

- Fault Activation (FA) and Propagation (FP)
  - lead to sets of Line Justification (LJ) problems. The LJ problems can be solved via value assignments.
- In D-algorithm
  - TG is done through indirect signal assignment for FA, FP, and LJ, that eventually maps into assignments at PI's
  - The decision points are at internal lines
  - The worst-case number of backtracks is exponential in terms of the number of decision points (e.g., at least  $2^k$  for  $k$  decision nodes)
- In PODEM
  - The test generation is done through a sequence of direct assignments at PI's
  - Decision points are at PIs, thus the number of backtracking might be fewer
 
# Search Space of PODEM

- Complete Search Space
  - A binary tree with  $2^n$  leaf nodes, where  $n$  is the number of PI's
- Fast Test Generation
  - Need to find a path leading to a SUCCESS terminal **quickly**



# Objective() and Backtrace()

---

- PODEM
  - Also aims at establishing a sensitization path based on **fault activation and propagation** like D-algorithm
  - Instead of **justifying** the signal values required for sensitizing the selected path, **objectives** are setup to guide the **decision process at PI's**
- **Objective**
  - is a **signal-value pair** ( $w, v_w$ )
- **Backtrace**
  - Backtrace maps a desired objective into a PI assignment that is likely to contribute to the achievement of the objective
  - Is a process that traverses the circuit back from the objective signal to PI's
  - The result is a **PI signal-value pair** ( $x, v_x$ )
  - No signal value is actually assigned during backtrace

往輸入端追蹤

# Objective Routine

- Objective Routine Involves
  - The selection of a **D-frontier**, **G**
  - The selection of an **unspecified input gate** of **G**

```
Objective() {  
    /* The target fault is w s-a-v */  
    /* Let variable obj be a signal-value pair */  
    if (the value of w is x)      obj = ( w, v' ); ← fault activation  
    else {  
        select a gate (G) from the D-frontier; ← fault propagation  
        select an input (j) of G with value x;  
        c = controlling value of G;  
        obj = (j, c');  
    }  
    return (obj);  
}
```

# Backtrace Routine

- Backtrace Routine
  - Involves finding an **all-x path** from objective site to a PI, i.e., every signal in this path has value x

```
Backtrace(w, vw) {  
    /* Maps objective into a PI assignment */  
    G = w; /* objective node */  
    v = vw; /* objective value */  
    while (G is a gate output) { /* not reached PI yet */  
        inv = inversion of G;  
        select an input (j) of G with value x;  
        G = j; /* new objective node */  
        v = v ⊕ inv; /* new objective value */  
    }  
    /* G is a PI */ return (G, v);  
}
```


# Example: Backtrace

Objective to achieved: (F, 1)


PI assignments:

(1)  $A = 0 \rightarrow \text{fail}$

(2)  $B = 1 \rightarrow \text{succeed}$

 

The first time of backtracing

 

The second time of backtracing

# PI Assignment in PODEM

Assume that: **PI's**: { a, b, c, d }

**Current Assignments**: { a=0 }

**Decision**: b=0 → objective fails


**Reverse decision**: b=1

**Decision**: c=0 → objective fails

**Reverse decision**: c=1


**Decision**: d=0

 
**Failure** means **fault effect cannot be propagated** to any PO under current PI assignments






## Example: PODEM (1/3)

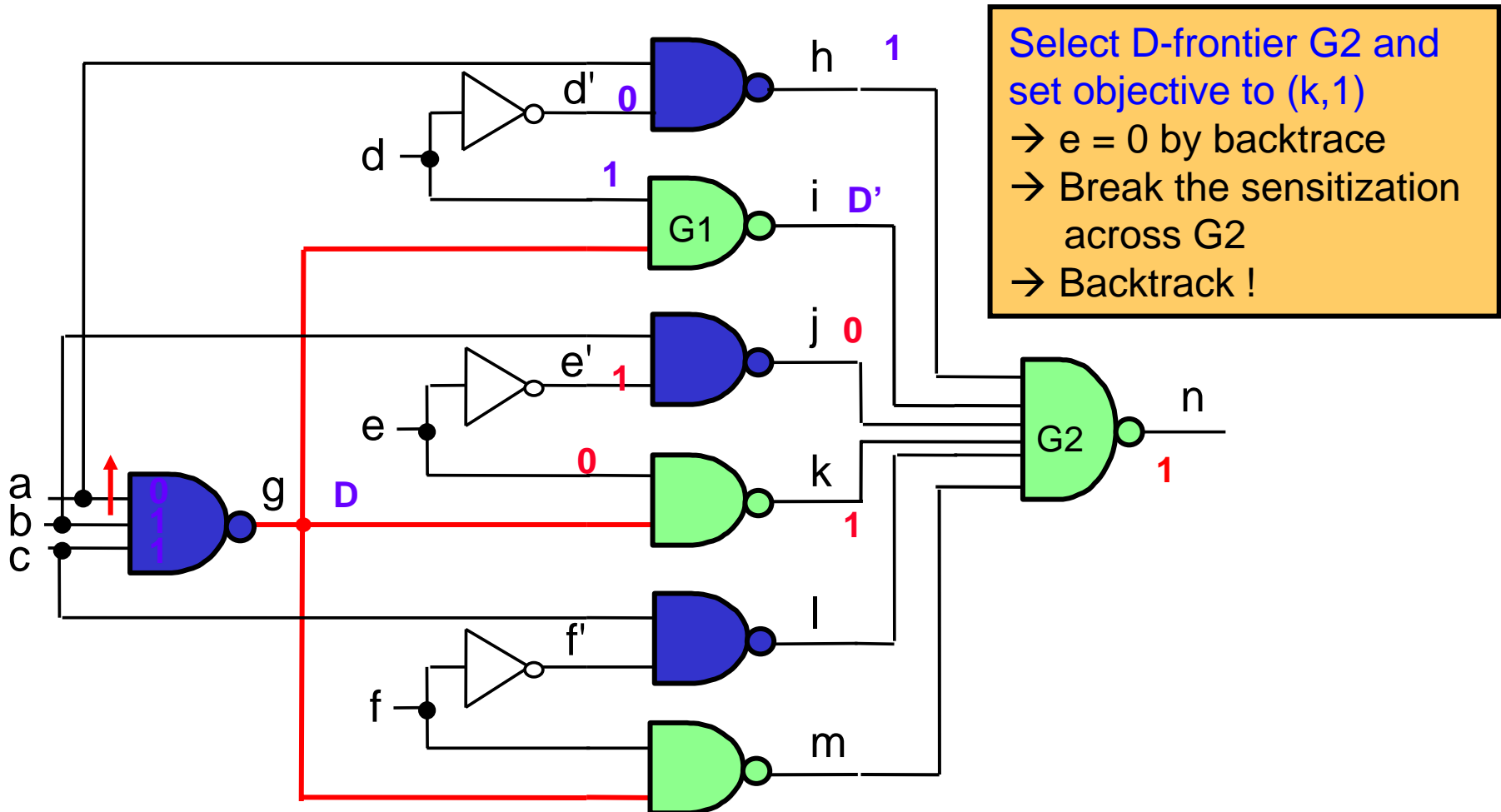

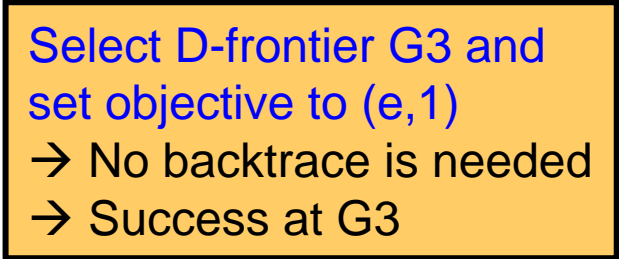


## Example: PODEM (3/3)

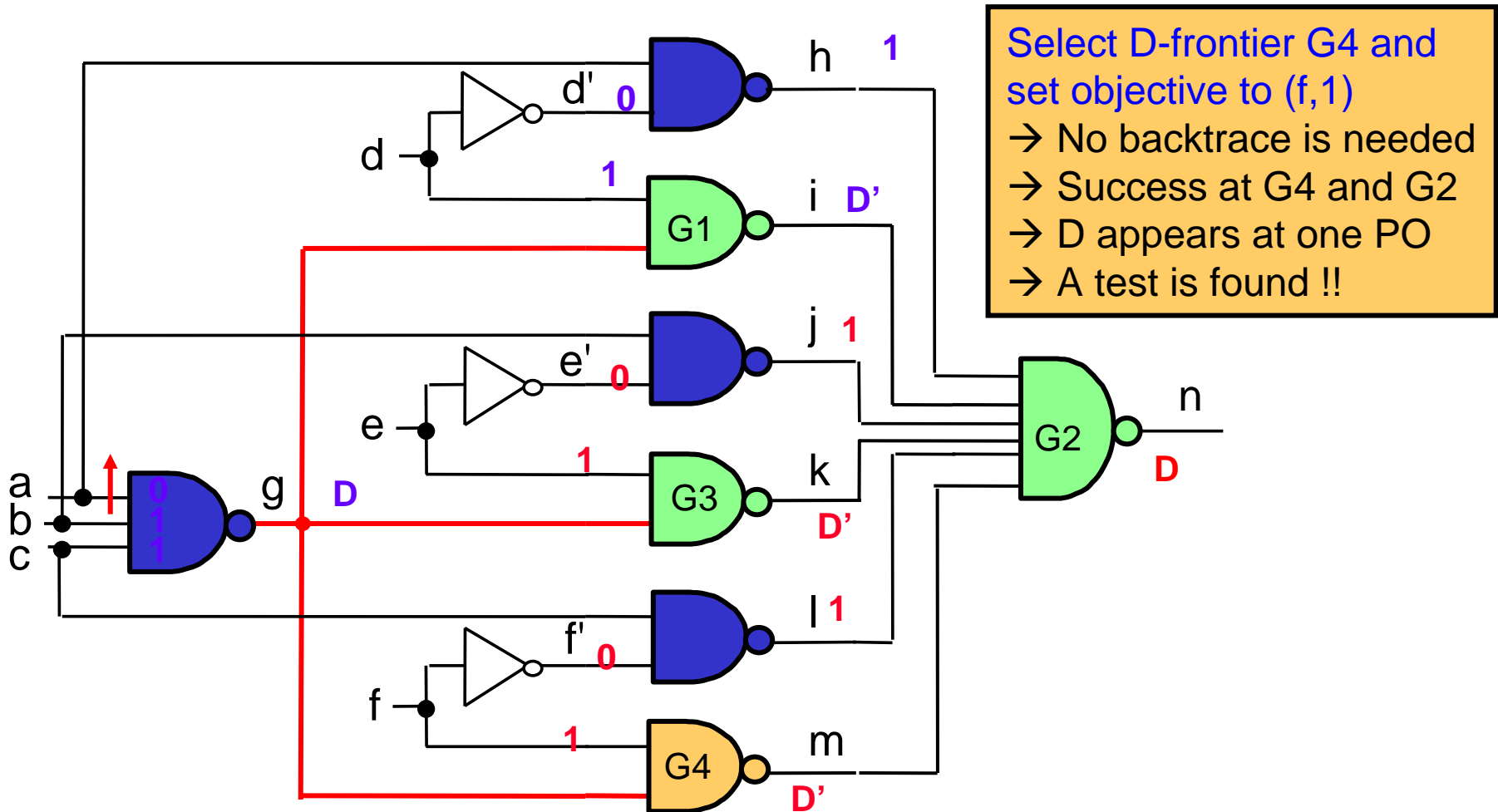


# PODEM: Value Computation

Objective	PI assignment	Implications	D-frontier	Comments
a=0	a=0	h=1	g	
b=1	b=1		g	
c=1	c=1	g=D	i,k,m	
d=1	d=1	d'=0 i=D'	k,m,n	
k=1	e=0	e'=1 j=0 k=1 n=1	m	<div>Assignments need to be reversed during backtracking</div> no solutions ! → backtrack reverse PI assignment
	e=1	e'=0 j=1 k=D'		
l=1	f=1	f'=0 l=1 m=D' n=D		

 

# Decision Tree in PODEM

---

 

- **Decision node**: the PI selected through backtrace for value assignment
- **Branch**: the value assignment to the selected PI

# Terminating Conditions

---

- D-algorithm
  - Success:
    - (1) Fault effect at an output (D-frontier may not be empty)
    - (2) J-frontier is empty
  - Failure:
    - (1) D-frontier is empty (all possible paths are false)
    - (2) J-frontier is not empty
- PODEM
  - Success:
    - Fault effect seen at an output
  - Failure:
    - Every PI assignment leads to failure, in which D-frontier is empty while fault has been activated

# PODEM: Recursive Algorithm

```
PODEM () /* using depth-first-search */
```

```
begin
```

```
  If(error at PO) return(SUCCESS);
```

```
  If(test not possible)      return(FAILURE);
```

```
  (k, vk) = Objective();          /* choose a line to be justified */
```

```
  (j, vj) = Backtrace(k, vk); /* choose the PI to be assigned */
```

```
  Imply (j, vj);                /* make a decision */
```

```
  If ( PODEM()==SUCCESS )      return (SUCCESS);
```


```
  Imply (j, vj');              /* reverse decision */
```

```
  If ( PODEM()==SUCCESS )      return(SUCCESS);
```

```
  Imply (j, x);
```

```
  Return (FAILURE);
```

```
end
```

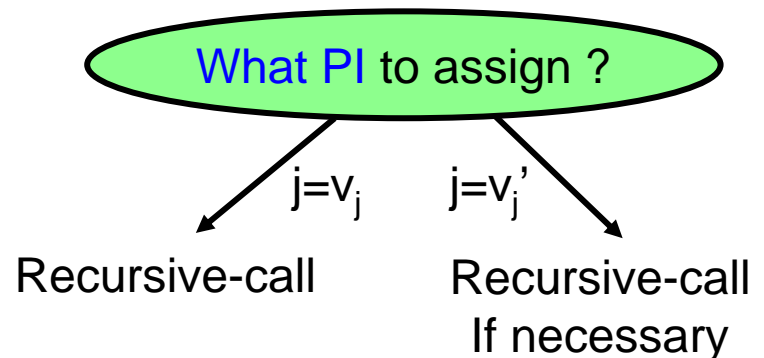

# Overview of PODEM

---



- PODEM
  - examines all possible input patterns **implicitly** but **exhaustively** (branch-and-bound) for finding a test
  - It is **complete** like D-algorithm (i.e., will find one if a test exists)
- Other Key Features
  - **No J-frontier**, since there are no values that require justification
  - **No consistency check**, as conflicts can never occur
  - **No backward implication**, because values are propagated only forward
  - **Backtracking** is implicitly done by simulation rather than by an explicit and time-consuming save/restore process
  - Experimental results show that PODEM is generally faster than the D-algorithm


  
# The Selection Strategy in PODEM

---

- In Objective() and Backtrace()
  - Selections are done **arbitrarily** in original PODEM
  - The algorithm will be more efficient if certain guidance used in the selections of **objective node** and **backtrace path**
- Selection Principle
  - **Principle 1**: Among **several unsolved problems**
    - → Attack the **hardest** one
    - Ex: to justify a '1' at an AND-gate output
  - **Principle 2**: Among **several solutions** for solving a problem
    - → Try the **easiest** one
    - Ex: to justify a '1' at OR-gate output




# Controllability As Guidance

- Controllability of a signal  $w$ 
  - $CY1(w)$ : the probability that line  $w$  has value 1.
  - $CY0(w)$ : the probability that line  $w$  has value 0.
  - Example:
    - $f = ab$
    - Assume  $CY1(a)=CY0(a)=CY1(b)=CY0(b)=0.5$
    - $CY1(f)=CY1(a) \times CY1(b)=0.25$ ,
    - $CY0(f)=CY0(a)+CY0(b)-CY0(a) \times CY0(b)=0.75$
- Example of Smart Backtracing
  - Objective  $(c, 1) \rightarrow$  choose path  $c \rightarrow a$  for backtracing
  - Objective  $(c, 0) \rightarrow$  choose path  $c \rightarrow a$  for backtracing

$$\begin{array}{l} CY1(a) = 0.33 \\ CY0(a) = 0.67 \end{array}$$
 
$$\begin{array}{l} CY1(b) = 0.5 \\ CY0(b) = 0.5 \end{array}$$



# Testability Analysis

---

- Applications
  - To give an early warning about the testing problems that lie ahead
  - To provide guidance in ATPG
- Complexity
  - Should be simpler than ATPG and fault simulation, i.e., need to be linear or almost linear in terms of circuit size
- Topology analysis
  - Only the structure of the circuit is analyzed
  - No test vectors are involved
  - Only approximate, reconvergent fanouts cause inaccuracy

# SCOAP

## (Sandia Controllability/Observability Analysis Program)


---

- Computes six numbers for each node  $N$ 
  - $CC^0(N)$  and  $CC^1(N)$ 
    - Combinational 0 and 1 controllability of a node  $N$
  - $SC^0(N)$  and  $SC^1(N)$ 
    - Sequential 0 and 1 controllability of a node  $N$
  - $CO(N)$ 
    - Combinational observability
  - $SO(N)$ 
    - Sequential observability
 
# General Characteristic of Controllability and Observability


Controllability calculation: sweeping the circuit from PI to PO

Observability calculation: sweeping the circuit from PO to PI


 
# Controllability Measures

- $CC^0(N)$  and  $CC^1(N)$ 
  - The number of combinational nodes that must be assigned values to justify a 0 or 1 at node N
- $SC^0(N)$  and  $SC^1(N)$ 
  - The number of sequential nodes that must be assigned values to justify a 0 or 1 at node N



$$CC^0(Y) = \min [CC^0(x1), CC^0(x2)] + 1$$


$$CC^1(Y) = CC^1(x1) + CC^1(x2) + 1$$

$$SC^0(Y) = \min [SC^0(x1), SC^0(x2)]$$

$$SC^1(Y) = SC^1(x1) + SC^1(x2)$$
 
# Controllability Measure (con't)

- $CC^0(N)$  and  $CC^1(N)$ 
  - The number of combinational nodes that must be assigned values to justify a 0 or 1 at node N
- $SC^0(N)$  and  $SC^1(N)$ 
  - The number of sequential nodes that must be assigned values to justify a 0 or 1 at node N




$$\begin{aligned} CC^0(Y) &= CC^0(x1) + CC^0(x2) + CC^0(x3) + 1 \\ CC^1(Y) &= \min [ CC^1(x1), CC^1(x2), CC^1(x3) ] + 1 \\ SC^0(Y) &= SC^0(x1) + SC^0(x2) + SC^0(x3) \\ SC^1(Y) &= \min [ SC^1(x1), SC^1(x2), SC^1(x3) ] \end{aligned}$$

# Observability Measure

---
 
## – CO(N) and SO(N)

- The observability of a node N is a function of the output observability and of the cost of holding all other inputs at non-controlling values



$$\begin{aligned} \text{CO}(\mathbf{x1}) &= \text{CO}(\mathbf{Y}) + \text{CC}^0(\mathbf{x2}) + \text{CC}^0(\mathbf{x3}) + 1 \\ \text{SO}(\mathbf{x1}) &= \text{SO}(\mathbf{Y}) + \text{SC}^0(\mathbf{x2}) + \text{SC}^0(\mathbf{x3}) \end{aligned}$$



## PODEM: Example 2 (1/3)


**Initial objective=(G5,1).**

G5 is an AND gate → Choose the hardest-1

→ **Current objective=(G1,1).**


G1 is an AND gate → Choose the hardest-1

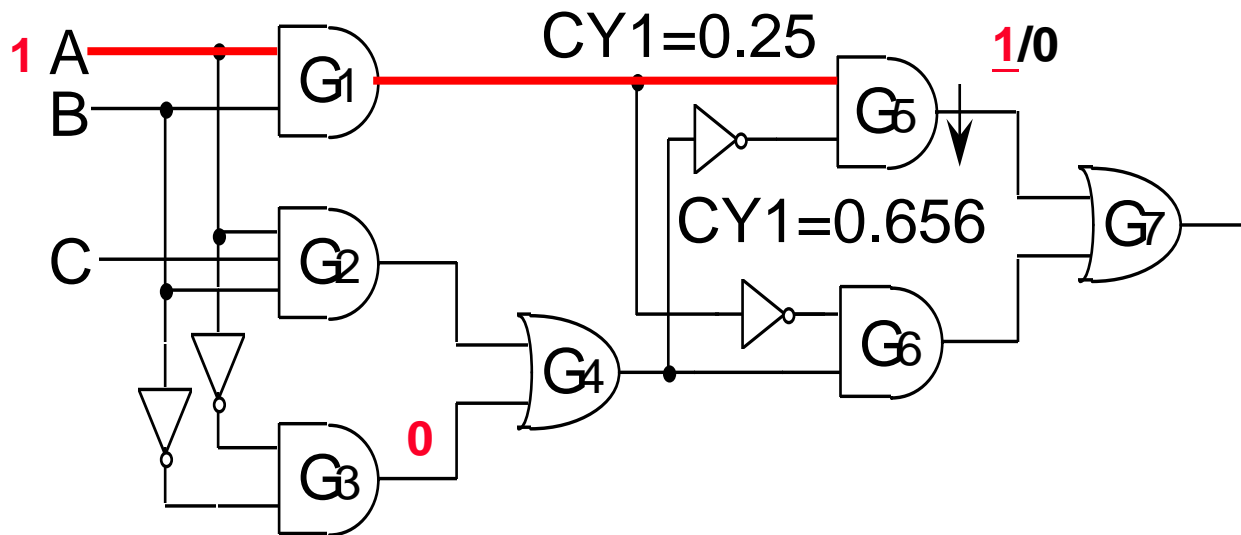→ Arbitrarily, **Current objective=(A,1).** A is a PI → Implication → G3=0.


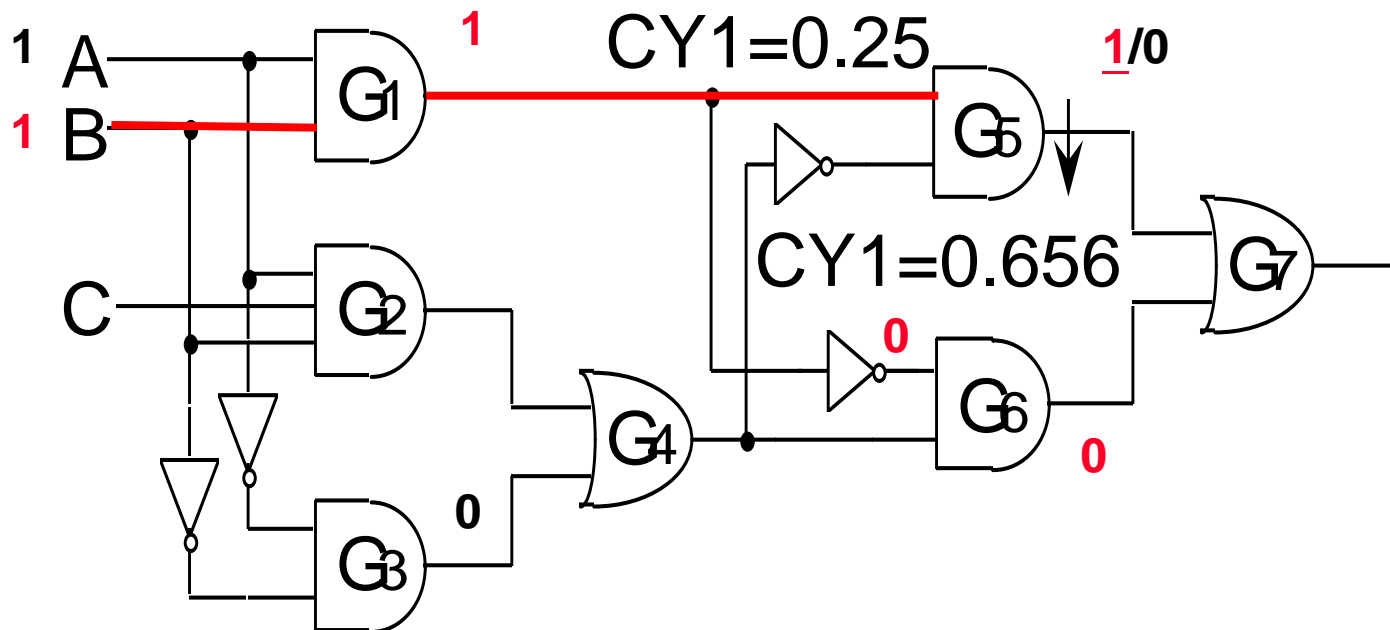
## PODEM: Example 2 (2/3)

The initial objective satisfied? No! → **Current objective=(G5,1).**  
G5 is an AND gate → Choose the hardest-1 → **Current objective=(G1,1).**  
G1 is an AND gate → Choose the hardest-1  
→ Arbitrarily, **Current objective=(B,1).** B is a PI → Implication → G1=1, G6=0.



## PODEM: Example 2 (3/3)


The initial objective satisfied? No! → **Current objective=(G5,1).**

The value of G1 is known → **Current objective=(G4,0).**

The value of G3 is known → **Current objective=(G2,0).**

A, B is known → **Current objective=(C,0).**

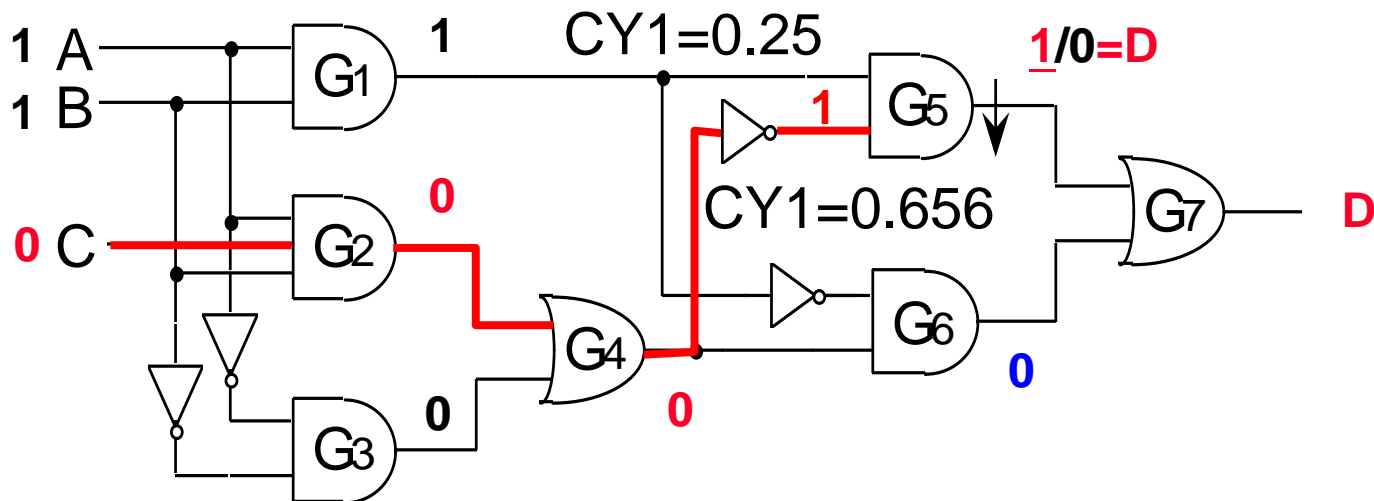C is a PI → Implication →  $G2=0$ ,  $G4=0$ ,  $G5=D$ ,  $G7=D$ .



**No backtracking !!**


# If The Backtracing Is Not Guided (1/3)

Initial objective=(G5,1).

Choose path G5-G4-G2-A → **A=0**.

Implication for A=0 → G1=0, G5=0 → **Backtracking to A=1**.

Implication for A=1 → G3=0.

 


## If The Backtracing Is Not Guided (2/3)

The initial objective satisfied? No! → **Current objective=(G5,1).**

Choose path G5-G4-G2-B → **B=0.**



Implication for B=0 → G1=0, G5=0 → **Backtracking to B=1.**

Implication for B=1 → G1=1, G6=0.

 
 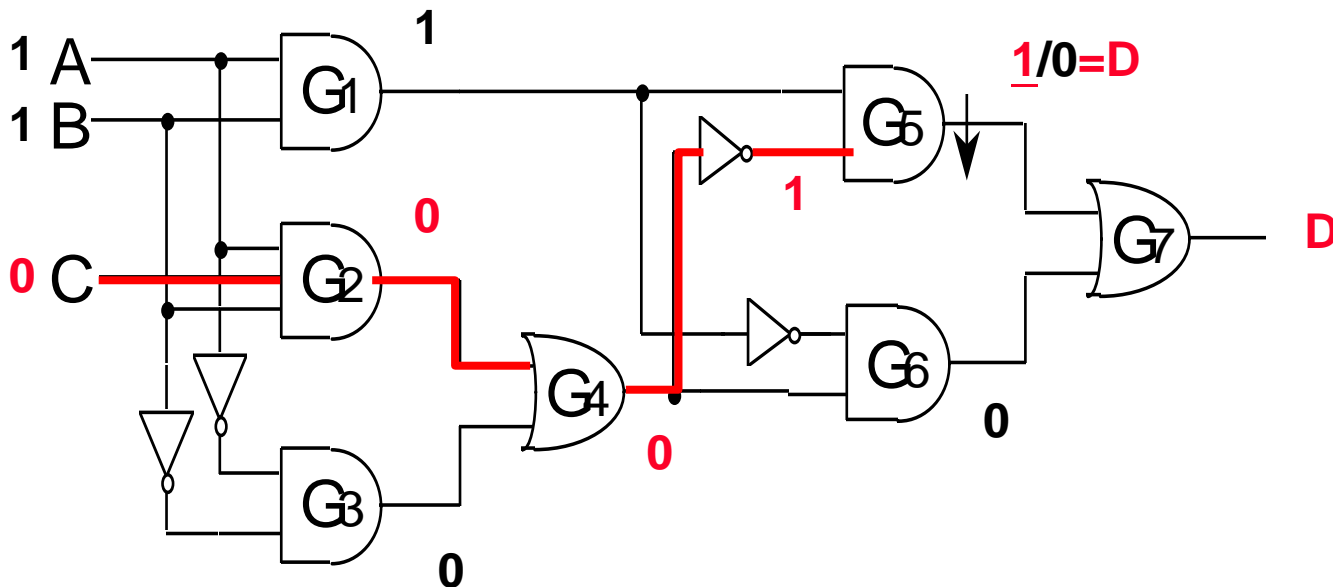
# If The Backtracing Is Not Guided (3/3)

The initial objective satisfied? No!  $\rightarrow$  Current objective=(G5,1).  
Choose path G5-G4-G2-C  $\rightarrow$  **C=0**.  
Implication for **C=0**  $\rightarrow$  G2=0, G4=0, G5=D, G7=D.



**Two times of backtracking !!**

# Outline of ATPG (Automatic Test Pattern Generation)

---

- Test Generation (TG) Methods

- Based on Truth Table
- Based on Boolean Equation
- Based on Structural Analysis
- D-algorithm [Roth 1967]
- 9-Valued D-algorithm [Cha 1978]
- PODEM [Goel 1981]
- FAN [Fujiwara 1983]



# FAN (Fanout Oriented) Algorithm


---

- FAN
  - Introduces two major extensions to PODEM's backtracing algorithm
- 1st extension
  - Rather than stopping at PI's, backtracing in FAN may **stop at an internal lines**
- 2nd extension
  - FAN uses **multiple backtrace** procedure, which attempts to satisfy a set of objectives simultaneously



 
# Headlines and Bound Lines


- Bound line
  - A line reachable from at least one **stem**
- Free line
  - A line that is NOT bound line
- Head line
  - A free line that directly feeds a bound line




# Decision Tree (PODEM v.s. FAN)

 

Assume that:  
Objective is (J, 0)

 

 J is a head line  
→ Backtrace stops at J  
→ Avoid unnecessary search



# Why Stops at Head Lines ?


---

- Head lines are mutually independent
  - Hence, for each given value combination at head lines, there always exists an input combination to realize it.
- FAN has two-steps
  - Step 1: PODEM using headlines as pseudo-PI's
  - Step 2: Generate real input pattern to realize the value combination at head lines.

 
# Why Multiple Backtrace ?

- Drawback of Single Backtrace
  - A PI assignment satisfying one objective  $\rightarrow$  may preclude achieving another one, and this leads to backtracking
- Multiple Backtrace
  - Starts from a **set of objectives** (Current\_objectives)
  - Maps these multiple objectives into a **head-line assignment**  $k=v_k$  that is likely to
    - Contribute to the **achievement of a subset** of the objectives
    - Or show that some subset of the original objectives **cannot be simultaneously achieved**

**Multiple objectives  
May have conflicting  
Requirements at a stem**



# Example: Multiple Backtrace

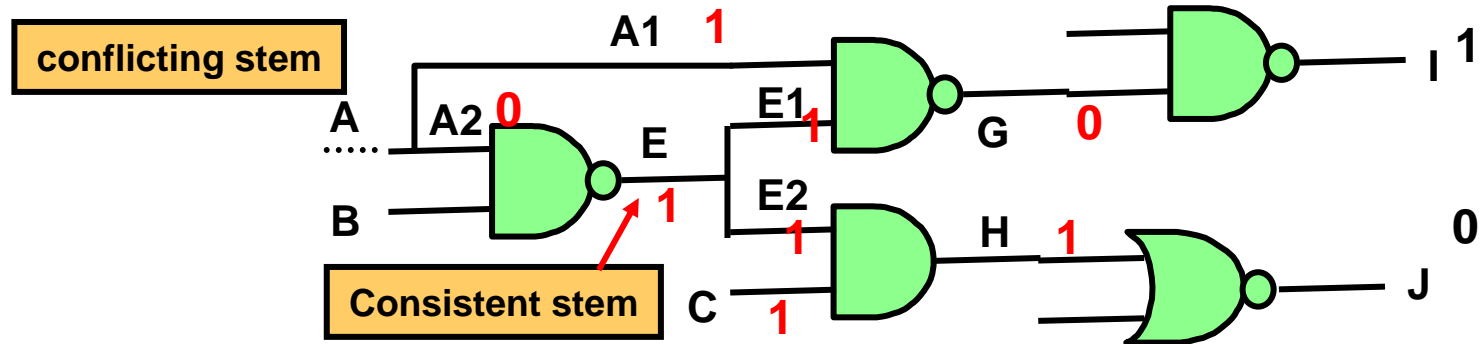

Current_objectives	Processed entry	Stem_objectives	Head_objectives
(I,1), (J,0)	(I,1)		
(J,0), (G,0)	(J,0)		
(G,0), (H,1)	(G,0)		
(H,1), (A1,1), (E1,1)	(H,1)		
(A1,1), (E1,1), (E2,1), (C,1)	(A1,1)	A	
(E1,1), (E2,1), (C,1)	(E1,1)	A,E	
(E2,1), (C,1)	(E2,1)	A,E	
(C,1)	(C,1)	A,E	C
Empty → restart from (E,1)		A	C
(E,1)	(E,1)	A	C
(A2,0)	(A2,0)	A	C
empty		A	C

# References For ATPG

---

- [1] Sellers et al., "Analyzing errors with the Boolean difference", IEEE Trans. Computers, pp. 676-683, 1968.
- [2] J. P. Roth, "Diagnosis of Automata Failures: A Calculus and a Method", IBM Journal of Research and Development, pp. 278-291, July, 1966.
- [2'] J. P. Roth et al., "[Programmed Algorithms to Compute Tests to Detect and Distinguish Between Failures in Logic Circuits](#)", IEEE Trans. Electronic Computers, pp. 567-579, Oct. 1967.
- [3] C. W. Cha et al, "9-V Algorithm for Test Pattern Generation of Combinational Digital Circuits", IEEE TC, pp. 193-200, March, 1978.
- [4] P. Goel, "[An Implicit Enumeration Algorithm to Generate Tests for Combinational Logic Circuits](#)", IEEE Trans. Computers, pp. 215-222, March, 1981.
- [5] H. Fujiwara and T. Shimono, "[On the Acceleration of Test Generation Algorithms](#)", IEEE TC, pp. 1137-1144, Dec. 1983.
- [6] M. H. Schulz et al., "SOCRATES: A Highly Efficient Automatic Test Pattern Generation System", IEEE Trans. on CAD, pp. 126-137, 1988.
- [6'] M. H. Schulz and E. Auth, "Improved Deterministic Test Pattern Generation with Applications to Redundancy Identification", IEEE Trans CAD, pp. 811-816, 1989.

# Outline

---

- Introduction
- Fault Modeling
- Fault Simulation
- Test Generation
- ➔ • Design For Testability

# Why DFT ?

---

- Direct Testing is Way Too Difficult !
  - Large number of FFs
  - Embedded memory blocks
  - Embedded analog blocks
- Design For Testability is inevitable
  - Like death and tax



# Design For Testability

---

- Definition
  - Design For Testability (DFT) refers to those **design techniques** that make test generation and testing cost-effective
- DFT Methods
  - Ad-hoc methods
  - Scan, full and partial
  - Built-In Self-Test (BIST)
  - Boundary scan
- Cost of DFT
  - Pin count, area, performance, design-time, test-time


# Important Factors

---

- Controllability
  - Measure the ease of controlling a line
- Observability
  - Measure the ease of observing a line at PO
- Predictability
  - Measure the ease of predicting output values
- DFT deals with ways of improving
  - Controllability
  - Observability
  - Predictability

 
# Test Point Insertion

- Employ test points to enhance
  - **Controllability**
  - **Observability**
- CP: Control Points
  - **Primary inputs used to enhance controllability**
- OP: Observability Points
  - **Primary outputs used to enhance observability**


 
# 0/1 Injection Circuitry

- Normal operation  
When  $CP\_enable = 0$
- Inject 0
  - Set  $CP\_enable = 1$  and  $CP = 0$
- Inject 1
  - Set  $CP\_enable = 1$  and  $CP = 1$



Inserted circuit for controlling line w


# Control Point Selection

---

- Impact
  - The **controllability** of the fanout-cone of the added point is improved
- Common selections
  - Control, address, and data buses
  - Enable / Hold inputs
  - Enable and read/write inputs to memory
  - **Clock** and **preset/clear** signals of flip-flops
  - Data select inputs to multiplexers and demultiplexers

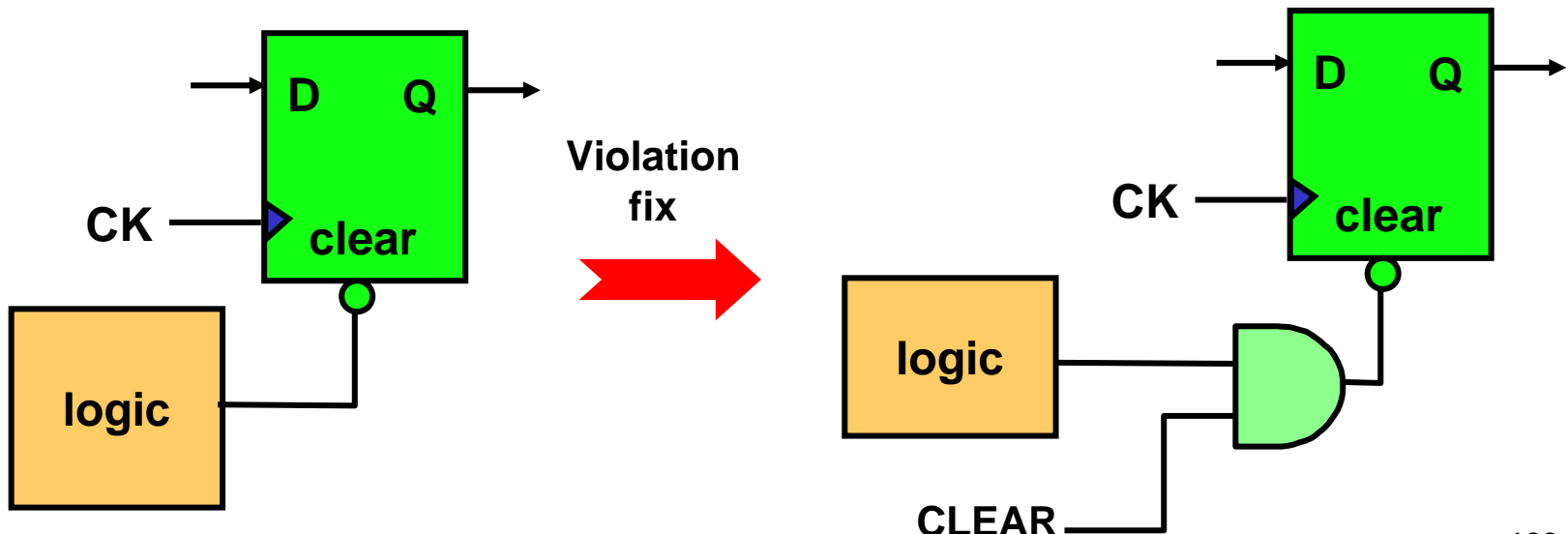
# Example: Use CP to Fix DFT Rule Violation

- DFT rule violations
  - The **set/clear** signal of a flip-flop is generated by other logic, instead of directly controlled by an input pin
  - **Gated clock** signals
- Violation Fix
  - Add a control point to the **set/clear signal** or clock signals


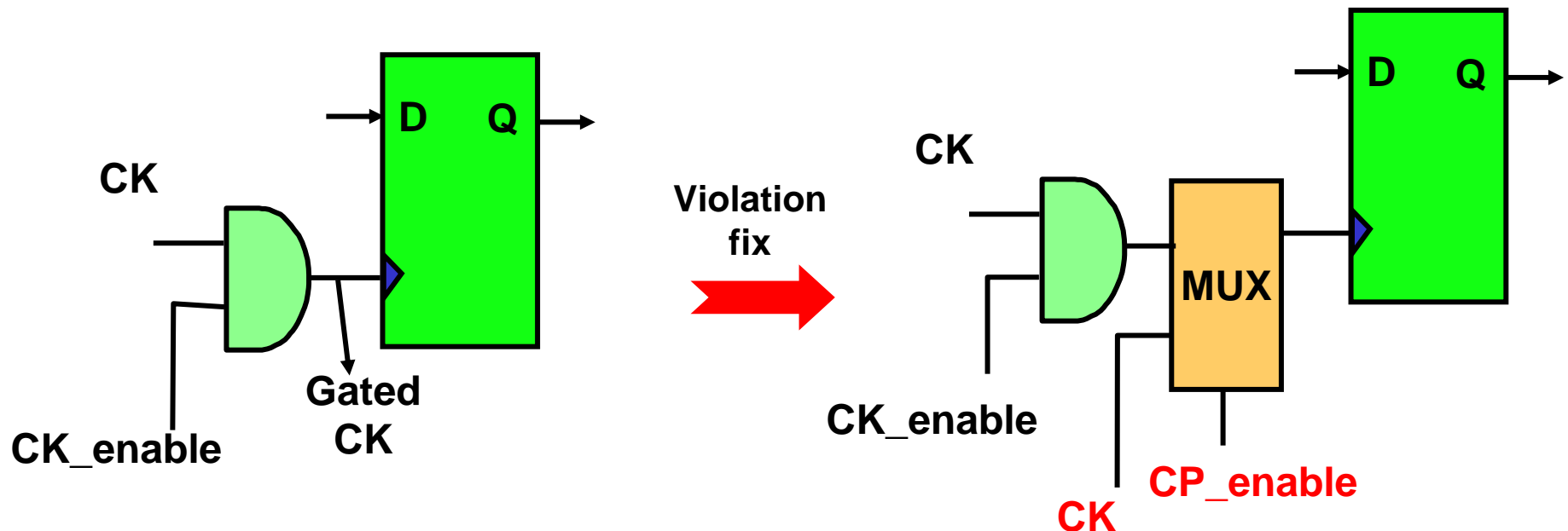
# Example: Fixing Gated Clock

- Gated Clocks
  - **Advantage:** power dissipation of a logic design can thus reduced
  - **Drawback:** the design's testability is also reduced
- Testability Fix




# Example: Fixing Tri-State Bus Contention

---


- Bus Contention
  - A stuck-at-fault at the tri-state enable line may cause bus contention – **multiple active drivers** connect to the bus simultaneously
- Fix
  - Add CP's to **turn off tri-state devices** during testing

Enable line stuck-at-1

 

Unpredicted voltage on bus may cause fault to go unnoticed

Enable line active

 




# Observation Point Selection

---

- Impact
  - The **observability** of the transitive fanins of the added point is improved
- Common choice
  - Stem lines having **high fanout**
  - Global feedback paths
  - Redundant signal lines
  - Output of logic devices having many inputs
    - MUX, XOR trees
  - **Output from state devices**
  - Address, control and data buses
 
# Problems of CP & OP

- Large number of I/O pins
  - Add MUX's to reduce the number of I/O pins
  - Serially shift CP values by shift-registers
- Larger test time




# What Is Scan ?


---

- Objective
  - To provide controllability and observability at **internal state variables** for testing
- Method
  - Add **test mode** control signal(s) to circuit
  - Connect **flip-flops to form shift registers** in test mode
  - Make inputs/outputs of the flip-flops in the shift register controllable and observable
- Types
  - Internal scan
    - **Full scan, Partial scan, Random access**
  - Boundary scan

# The Scan Concept

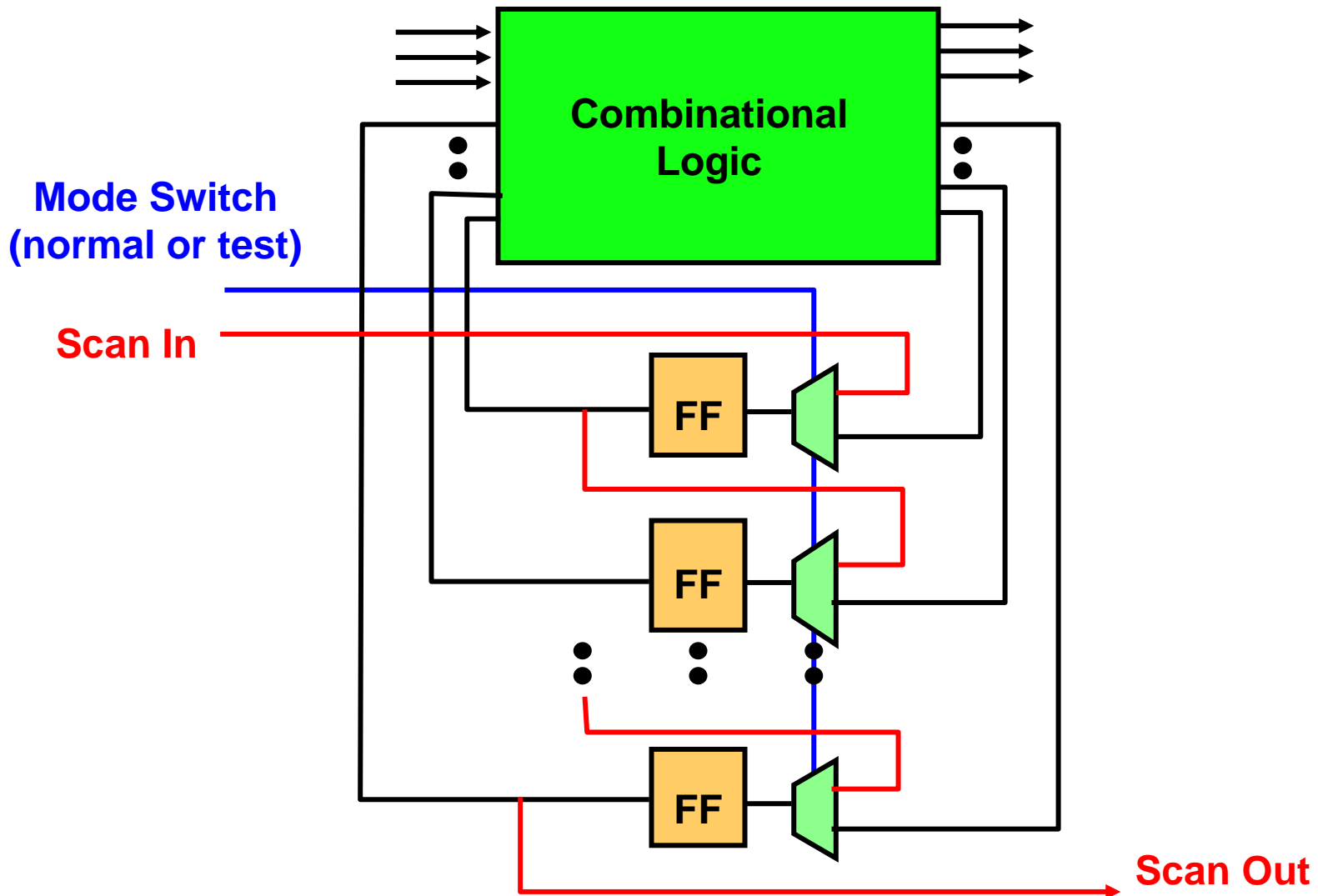


# A Logic Design Before Scan Insertion

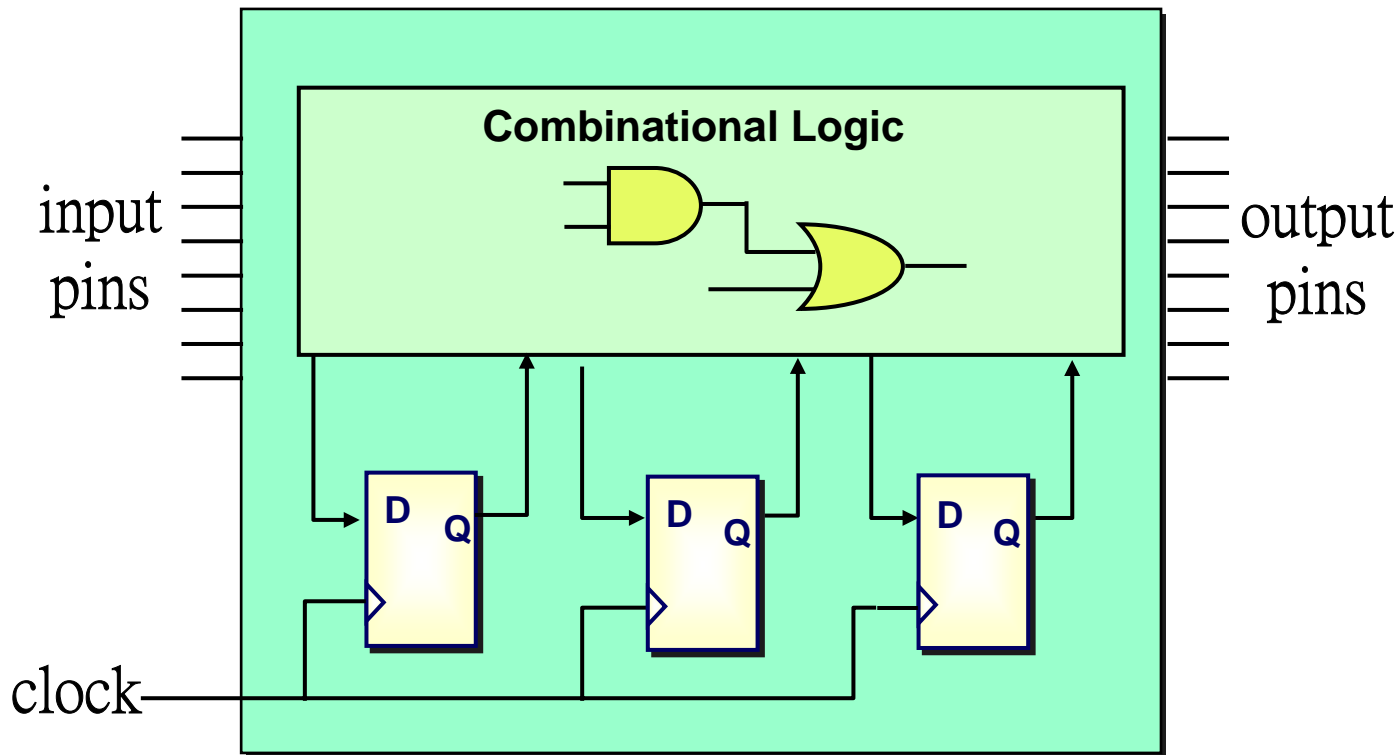


Sequential ATPG is extremely difficult:  
due to the lack of controllability and observability at flip-flops.

# Example: A 3-stage Counter

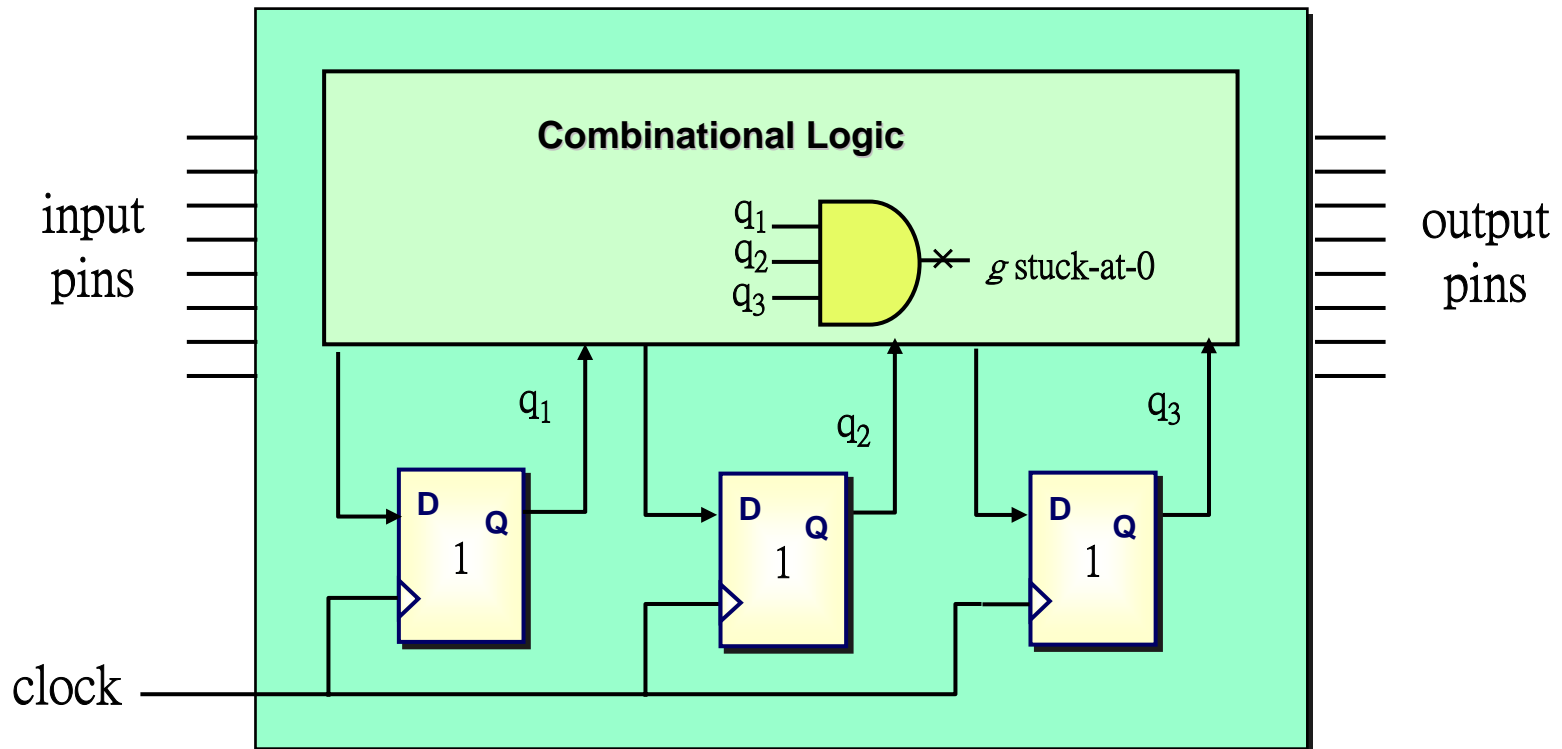

It takes 8 clock cycles to set the flip-flops to be (1, 1, 1),  
for detecting the target fault  $g$  stuck-at-0 fault  
( $2^{20}$  cycles for a 20-stage counter !)

# A Logic Design After Scan Insertion

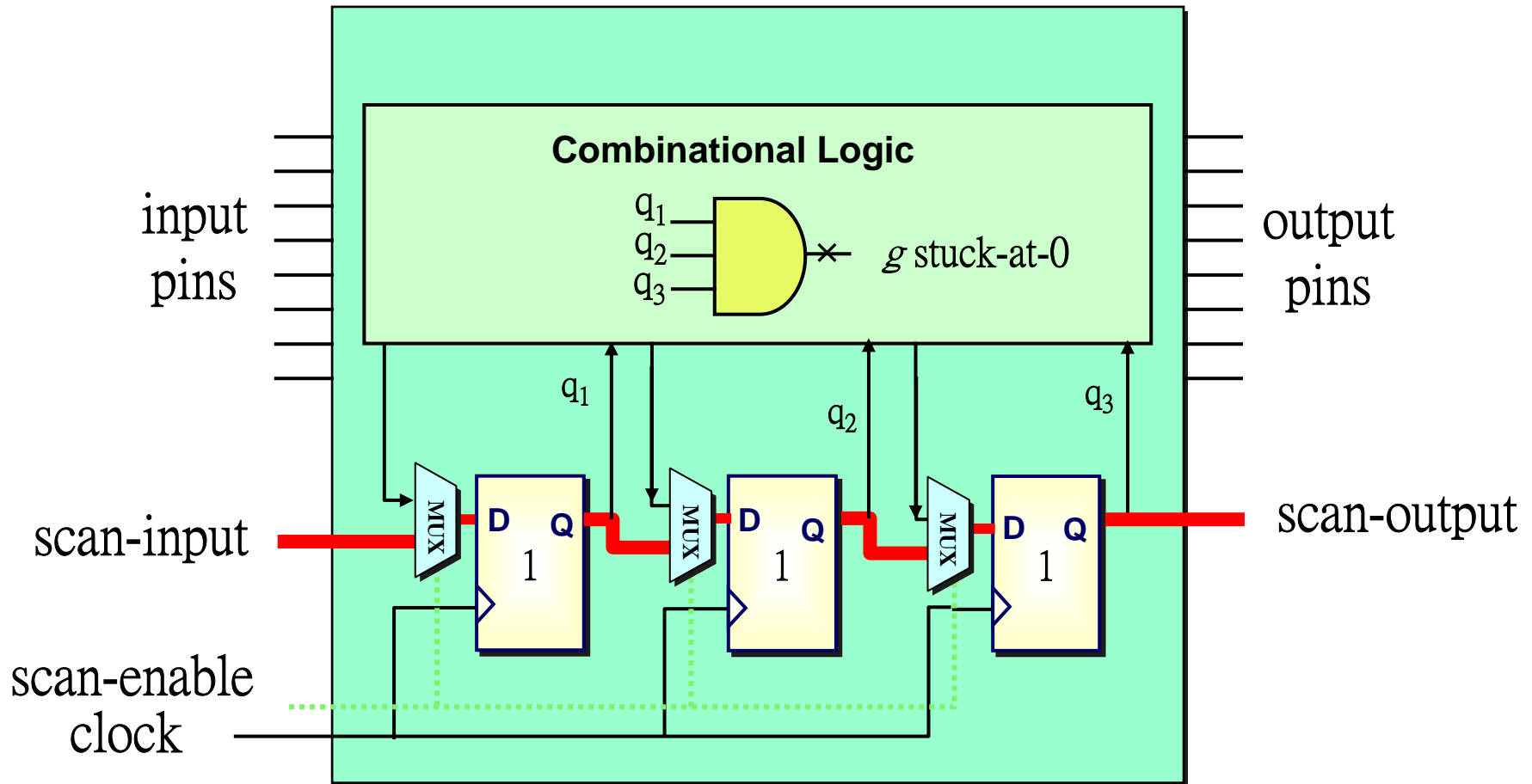

Scan Chain provides an **easy access** to flip-flops  
→ Pattern Generation is much easier !!


# Procedure Of Applying Test Patterns

- Notation

- Test vectors  $\mathbf{T} = \langle t_i^I, t_i^F \rangle i= 1, 2, \dots$
- Output Response  $\mathbf{R} = \langle r_i^O, r_i^F \rangle i= 1, 2, \dots$

- Test Application

 - (1)  $i = 1$ ;
- (2) Scan-in  $t_1^F$  /\* scan-in the first state vector for PPI's \*/
- (3) Apply  $t_i^I$  /\* apply current input vector at PI's \*/
- (4) Observe  $r_i^O$  /\* observe current output response at PO's \*/
- (5) **Parallely load register** /\* load-in the next vector at PPO's \*/
  - (I.e., set Mode to 'Normal')
- (6) Scan-out  $r_i^F$  while scanning-in  $t_{i+1}^F$  /\* overlap scan-in and scan-out \*/
- (7)  $i = i+1$ ; Goto step (3)






# Testing Scan Chain ?

---


- Common practice
  - Scan chain is often **first tested** before testing core logic by pumping-in and pumping-out **random vectors**
- Procedure
  - (1)  $i = 0$ ;
  - (2) Scan-in 1<sup>st</sup> random vector to flip-flops
  - (3) Scan-out  $(i)^{\text{th}}$  random vector while scanning-in  $(i+1)^{\text{th}}$  vector for flip-flops.
    - The  $(i)^{\text{th}}$  scan-out vector should be identical to  $(i)^{\text{th}}$  vector scanned in earlier, otherwise scan-chain is mal-functioning
  - (4) If necessary  $i = i+1$ , goto step (3)
 
# MUXed Scan Flip-Flop

- Only **D-type master-slave flip-flops** are used
- One extra primary input **pin** available for test
- All flip-flop clocks controlled from primary inputs
  - No **gated clock** allowed
- Clocks must not feed data inputs of flip-flops
- Most popularly supported in standard cell libraries




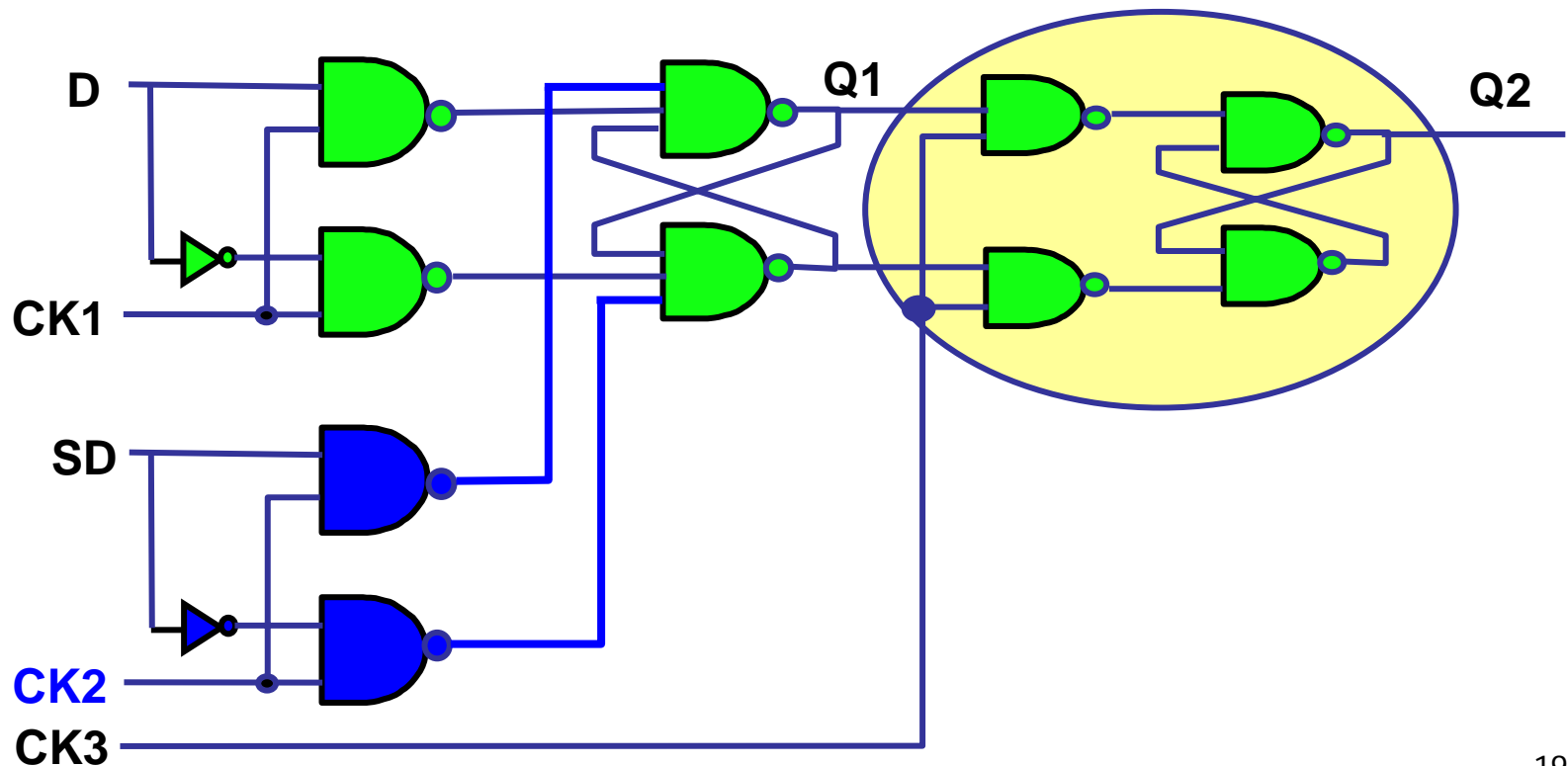- LSSD: Level Sensitive Scan Design
  - Less performance degradation than MUXed scan FF
- Clocking
  - Normal operation: non-overlapping CK1=1 → CK3=1
  - Scan operation: non-overlapping CK2=1 → CK3=1





# Symbol of LSSD Scan FF

---

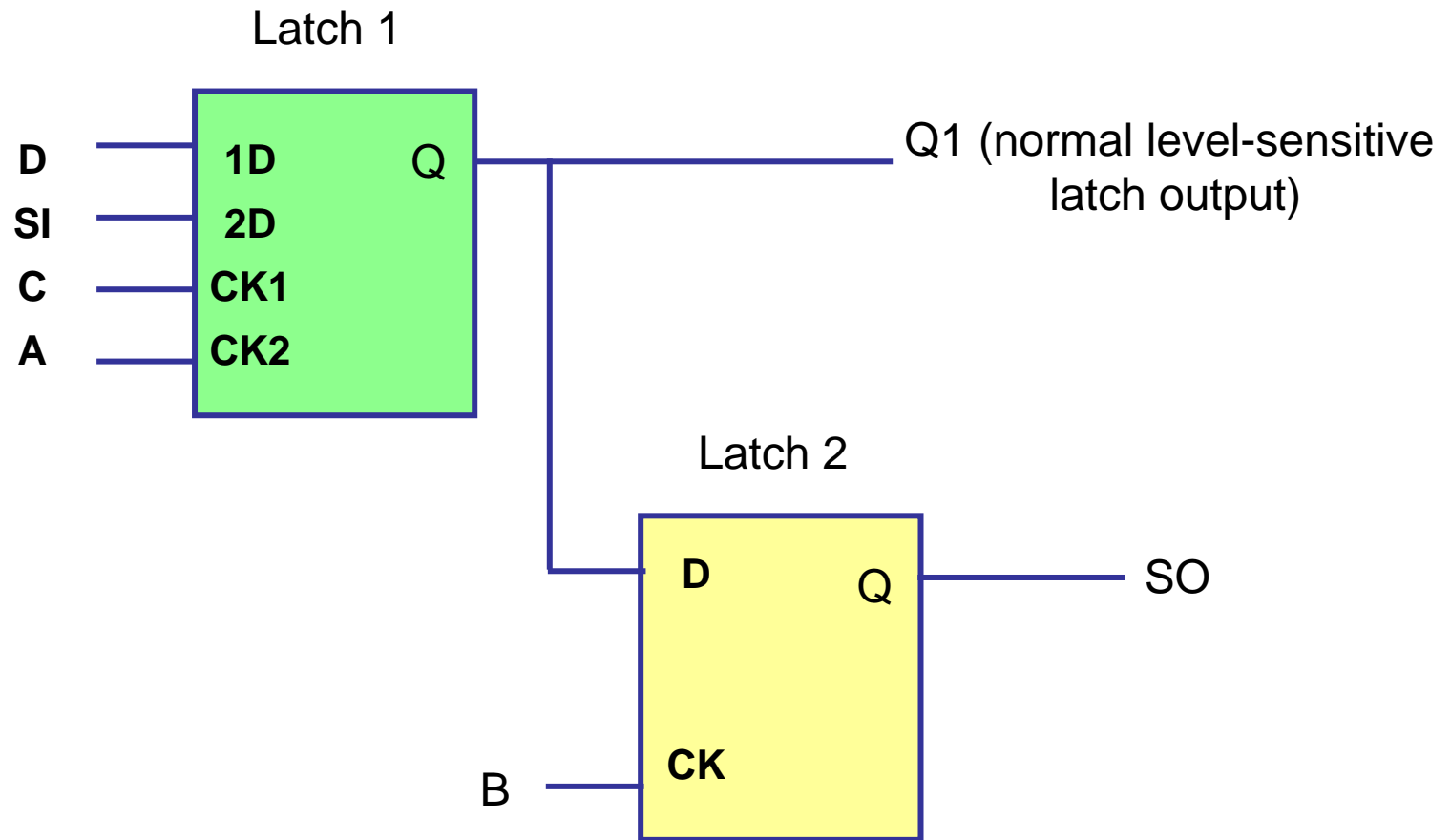

# Scan Rule Violation Example

 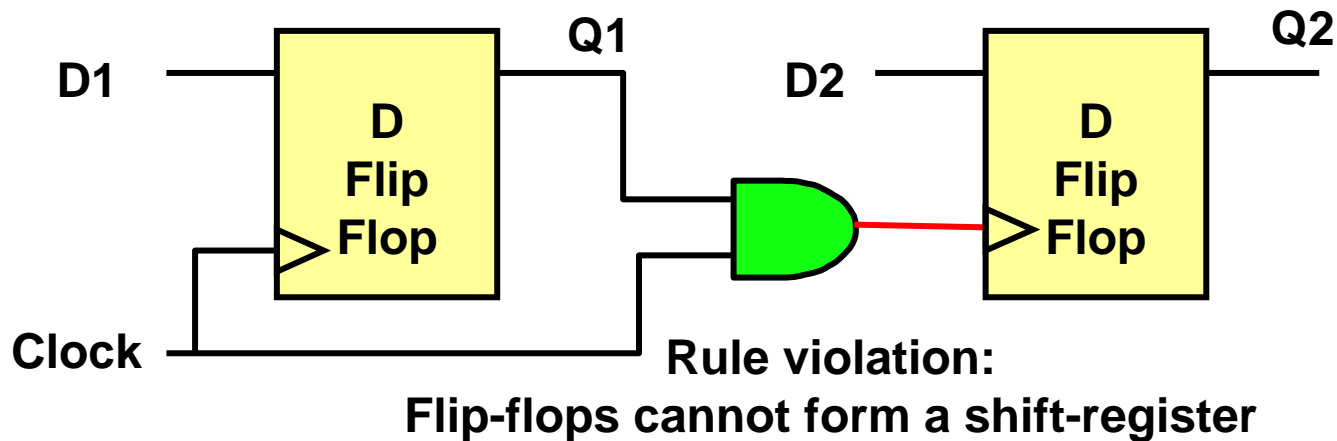

**All FFs are triggered by the same clock edge  
Set or reset signals are not controlled by any internal signals**

# Some Problems With Full Scan

---

## Major Commercial Test Tool Companies

Synopsys

Mentor-Graphics

SynTest (華騰科技)

LogicVision

- Problems
  - Area overhead
  - Possible performance degradation
  - High test application time
  - Power dissipation
- Features of Commercial Tools
  - Scan-rule violation check (e.g., DFT rule check)
  - Scan insertion (convert a FF to its scan version)
  - ATPG (both combinational and sequential)
  - Scan chain reordering after layout


# Performance Overhead

---


- The increase of delay along the normal data paths include:
  - Extra gate delay due to the multiplexer
  - Extra delay due to the capacitive loading of the scan-wiring at each flip-flop's output
- Timing-driven partial scan
  - Try to avoid scan flip-flops that belong to the timing critical paths
  - The flip-flop selection algorithm for partial scan can take this into consideration to reduce the timing impact of scan to the design
 
# Scan-Chain Reordering

- Scan-chain order is often decided at gate-level **without knowing the cell placement**
- Scan-chain consumes a lot of **routing resources**, and could be minimized by **re-ordering the flip-flops** in the chain after layout is done



Layout of a cell-based design

 

A better scan-chain order



# Overhead of Scan Design


---

- No. of CMOS gates = 2000
- Fraction of flip-flops = 0.478
- Fraction of normal routing = 0.471

Scan implementation	Predicted overhead	Actual area overhead	Normalized operating frequency
None	0	0	1.0
Hierarchical	14.05%	16.93%	0.87
Optimized	14.05%	11.9%	0.91
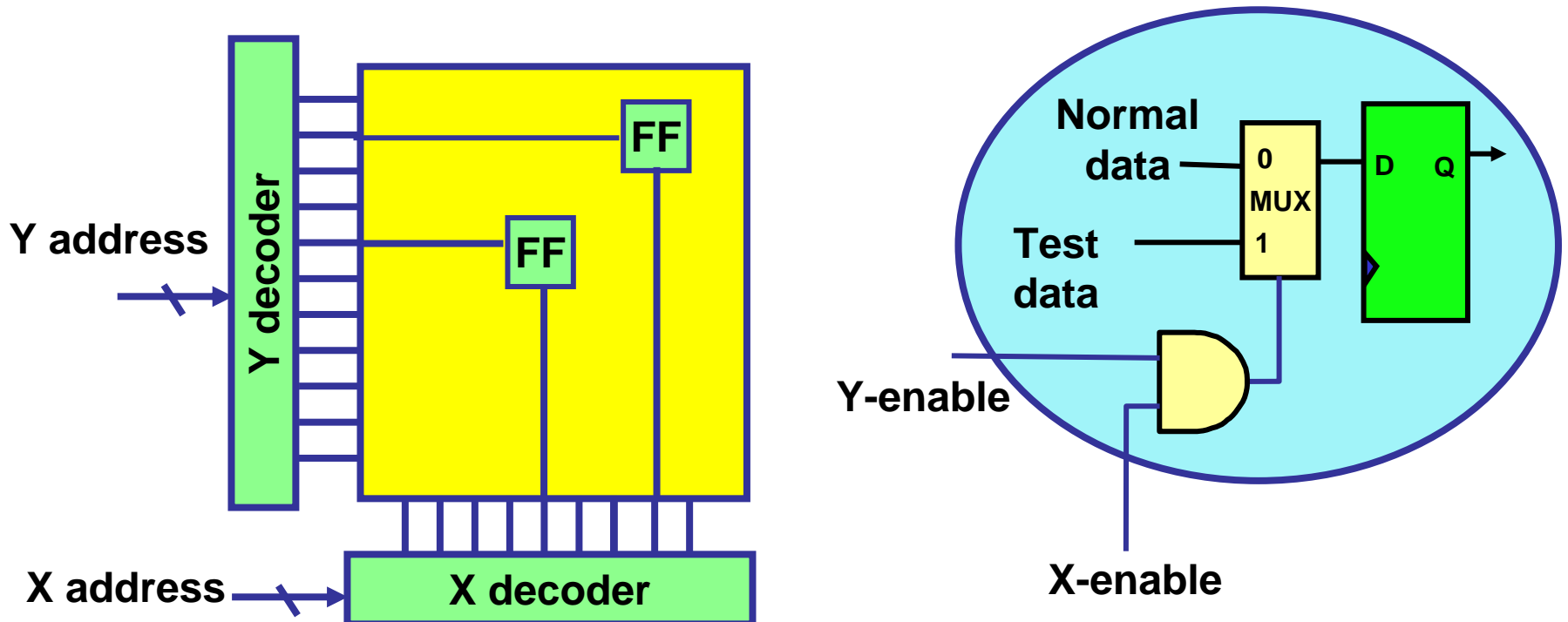
# Random Access Scan

- Comparison with Scan-Chain
  - More flexible – any FF can be accessed in constant time
  - Test time could be reduced
  - More hardware and routing overhead




# Parameters

---

- link\_library
  - The ASIC vendor library where your design is initially represented
- target\_library
  - Usually the same as your link\_library, unless you are translating a design between technologies
- test\_default\_scan\_style
  - multiplexed\_flip\_flop, clocked\_scan, aux\_clock\_lssd
  - Note that: the cell library incorporated should support these scan cells

# Typical Flat Design Flow

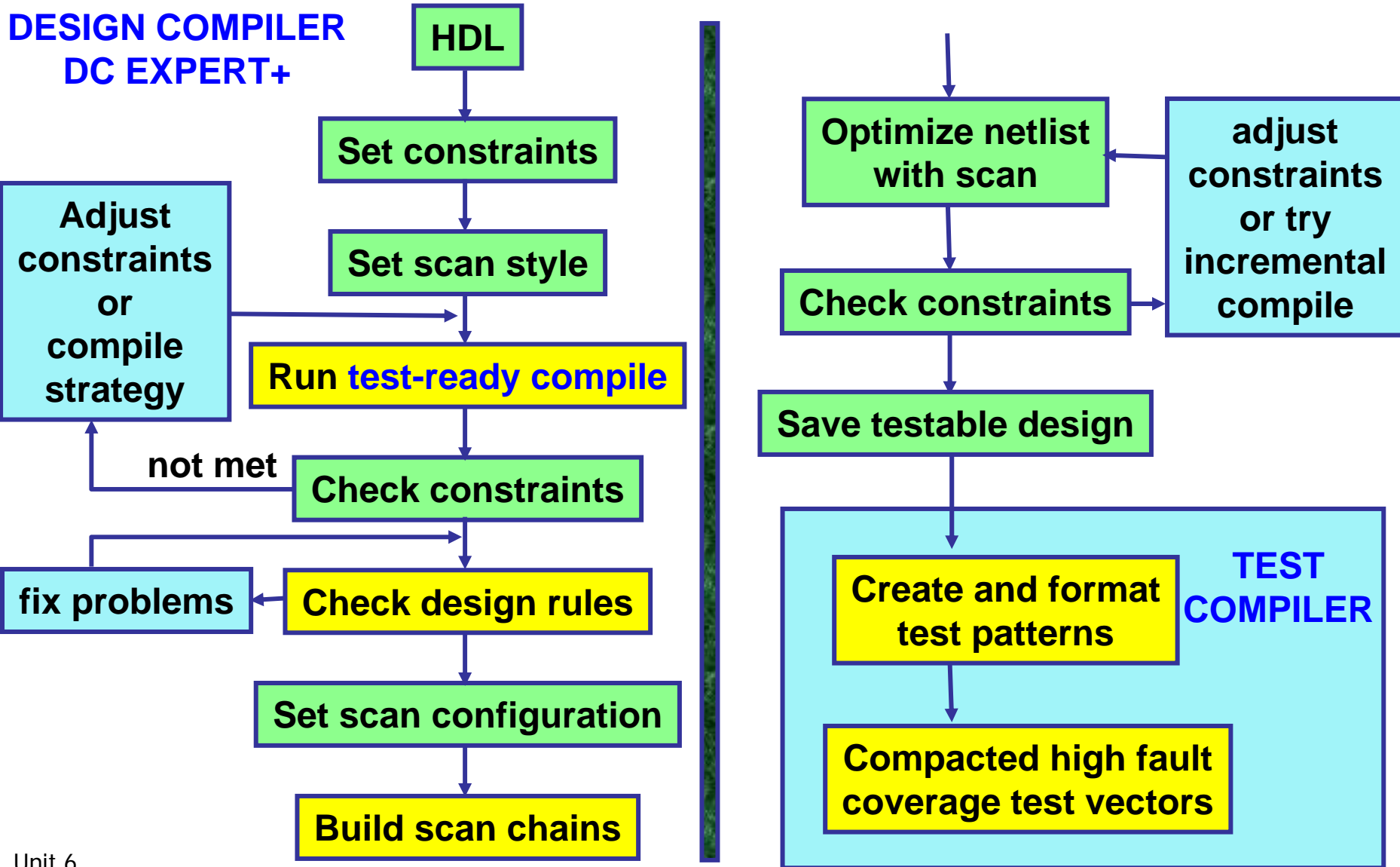

# Synthesizing The Design

---

- Read in HDL code

```
dc_shell > read -format verilog design_name.v
```

- Set target\_library

```
dc_shell > target_library = asic_vendor.db
```

- Constraint the design

```
dc_shell > max_area 1000
```

```
dc_shell > create_clock clock_port -period 20 -waveform {10,15}
```

- Declare the test methodology

```
dc_shell > set_scan_configuration -methodology partial_scan
```

- Select scan style

```
dc_shell > test_default_scan_style = multiplexed_flip_flop
```

- Compilation

```
dc_shell > compile -scan
```

# Synthesizing The Design (con't)

---

- Check constraints

`dc_shell > report_constraint -all_violators`

- Save design

`dc_shell > write -format db -out design_test_ready.db`

- Check design rules

`dc_shell > check_test`

# Building Scan Chains

---

- Declare Scan Enable Signal

```
dc_shell > set_scan_signal test_scan_enable -port SE
```

```
dc_shell > set_drive 2 SE
```

- Set Min. Fault Coverage If Partial Scan

```
dc_shell > set_min_fault_coverage 95
```

- No Scan Replacement

```
dc_shell > set_scan_configuration -replace false
```

- Build the Scan Chains

```
dc_shell > insert_scan
```

- Check the Design Rules Again

```
dc_shell > check_test
```

# Generating Test Patterns

---

- Generate Test Report

dc\_shell > report\_test –scan\_path

- Write out Scan Design

dc\_shell > write –format db –hierarchy –out design.db

- Generate The Test

dc\_shell > create\_test\_patterns –compact\_effort high

- Write Out Test Patterns

dc\_shell > write\_test –out test\_vectors –format WGL

- WGL (Waveform Generation Language)

– Is a format supported by Summit Design Software




# Partial Scan

---

- Basic idea
  - Select a subset of flip-flops for scan
  - Lower overhead (area and speed)
  - Relaxed design rules
- Cycle-breaking technique
  - Cheng & Agrawal, IEEE Trans. On Computers, April 1990
  - Select scan flip-flops to simplify sequential ATPG
  - Overhead is about 25% off than full scan
- Timing-driven partial scan
  - Jou & Cheng, ICCAD, Nov. 1991
  - Allow optimization of area, timing, and testability simultaneously

# Full Scan vs. Partial Scan


---

 


every flip-flop is a scan-FF   NOT every flip-flop is a scan-FF

test time	longer	shorter
hardware overhead	more	less
fault coverage	~100%	unpredictable
ease-of-use	easier	harder

# Partial Scan Design

 

 Scan Flip-Flops: {2, 5}  
Non-Scan FFs: {1, 3, 4, 6}



# Cycle Breaking Algorithm

---


- Algorithm 1
  - Select nodes in a digraph  $G=(V,E)$  to cut all cycles of length greater than one
- Step 1
  - Find all the **non-trivial SCCs**  $G_i=(V_i, E_i)$ , where  $1 \leq i \leq r$
  - If no non-trivial SCC stop
- Step 2
  - (1) Delete a node  $v$  using one of the **heuristics H1, H2, H3** (to be discussed later)
  - (2) **Delete node  $v$  from  $V_i$**  and delete all incoming and outgoing edges of  $v$
  - (3) Let the resulting graph be  $G_i'=(V_i', E_i')$ 
    - Execute Algorithm 1 recursively with  $G_i'$  as input graph

# Reducing the Length of Consecutive Self-Loop Paths

---

- Definition
  - A graph has a **consecutive self-loop path of length K** if there exists a directed path of exactly K vertices, each having a self-loop
- Observation
  - Circuits with consecutive self-loop paths, such as counters, need longer test generation time
- Solution
  - Reduce the length of consecutive self-loop paths by **scanning some of the flip-flops with self-loops**
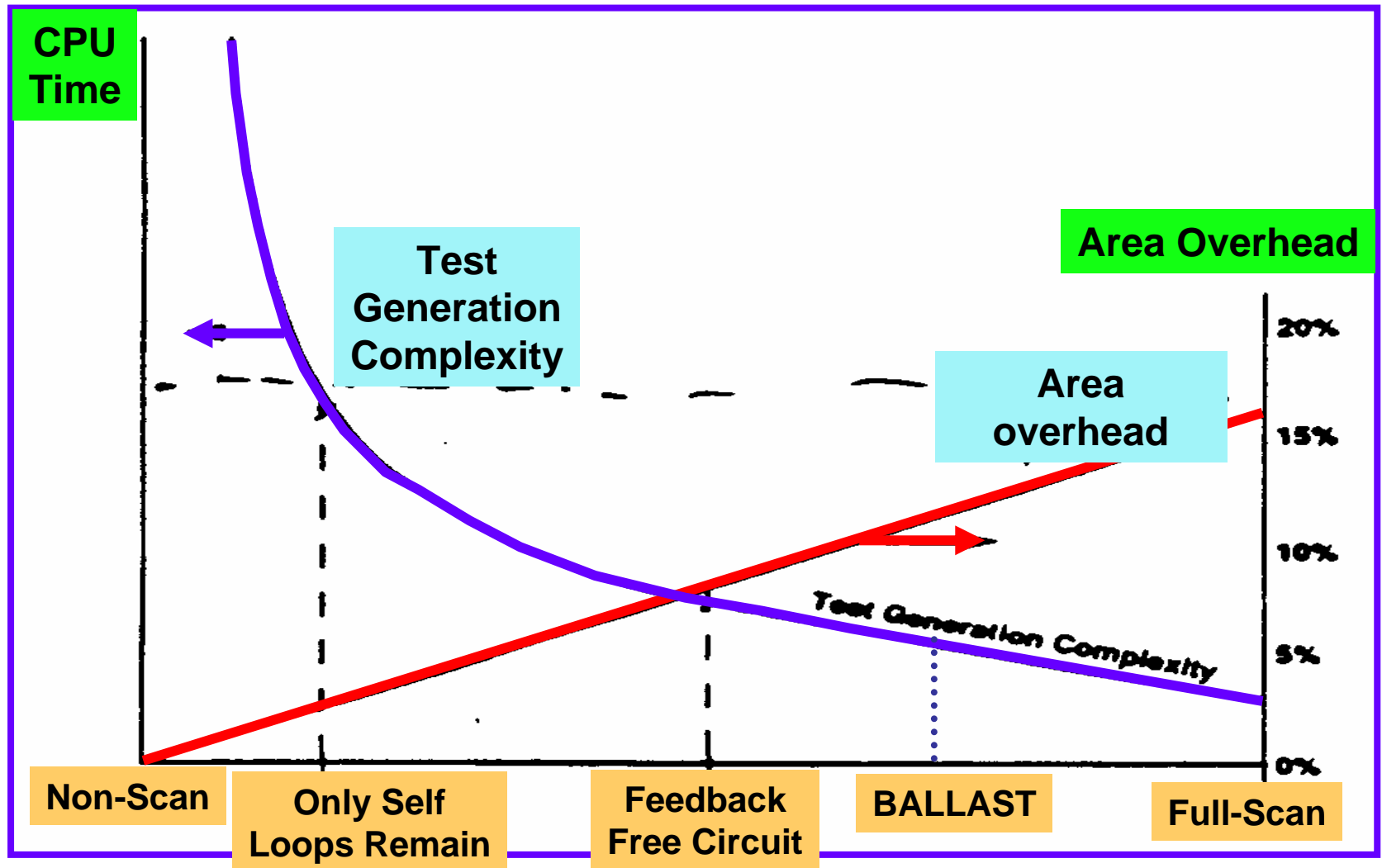
# Trade-Off of Area Overhead v.s. Test Generation Effort



# Conclusions

---

- Testing
  - Conducted after manufacturing
  - Must be considered during the design process
- Major Fault Models
  - Stuck-At, Bridging, Stuck-Open, Delay Fault, ...
- Major Tools Needed
  - Design-For-Testability
    - By Scan Chain Insertion or Built-In Self-Test
  - Fault Simulation
  - Automatic Test Pattern Generation
- Other Applications in CAD
  - ATPG is a way of Boolean Reasoning, applicable to many logic-domain CAD problems